

EENG 426/CPSC 459/ENAS 876 Silicon Compilation

Transistors and Switching Networks

Computer Systems Lab
<http://csl.yale.edu/~rajit>

Fall 2018

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

1 / 32

Feature size

We are going to be using abstract geometry.

- Dimensions will be in integer units of λ
- Manufacturing rules specified in λ
- Examples:
 - Minimum width of a wire $\geq 3\lambda$
 - Minimum spacing between two wires $\geq 3\lambda$
- $F = .6\mu m$, the *feature size*, determined by the smallest transistor that can be manufactured
- $\lambda = 0.3\mu m$, or $F/2$
 \Rightarrow minimum transistor width is usually 2λ

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

2 / 32

Capacitors

- Charge \propto Voltage
- $Q = CV$

Normally,

$$I = C \frac{dV}{dT}$$

Units: Farads (F)

Order of magnitude in $0.6\mu m$ CMOS: $1fF/\mu m^2$

Yale

AVLSI


Manohar

EENG 426: Silicon Compilation

Fall 2018

3 / 32

Capacitors

 

Electrostatics: $\nabla \cdot \mathbb{E} = \frac{\rho}{\epsilon_0}$

$$\begin{aligned} Q &= \sigma A & \epsilon_0 &= 8.85 \times 10^{-12} F/m \\ \text{So: } E &= \frac{\sigma}{\epsilon} & \epsilon &= k\epsilon_0 \\ \text{So: } V &= \frac{\sigma d}{\epsilon} \\ \text{So: } Q &= \frac{\epsilon_0 A}{d} V \end{aligned}$$

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

4 / 32

Capacitors

Capacitance $C = \epsilon A/d$

When we draw geometry, we control A

So for us $C = (\epsilon/d)A \approx 0.1fF/\square$



Series/parallel combination of capacitors:

- $C_{\parallel} = C_1 + C_2$
- $\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2}$

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

5 / 32

Resistors

- $I = V/R$, or $I = GV$, or $V = IR$

Units: Ohms (Ω)

Order of magnitude in $0.5\mu m$ CMOS: $0.1\Omega/\square$

Resistance $R = \rho \frac{l}{A}$

$A = w \times t$, t : thickness of wire

So for us $R = (\rho/t) \frac{l}{w}$

$$\frac{1}{R_{\parallel}} = \frac{1}{R_1} + \frac{1}{R_2} \quad R_s = R_1 + R_2$$

Yale

AVLSI


Manohar

EENG 426: Silicon Compilation

Fall 2018

6 / 32

Transistors

 

- Green: "ndiffusion" ("ndiff")
- Brown: "pdiffusion" ("pdiff")
- Red: "polysilicon" ("poly")

The intersection defines the gate region.

- width W , length L

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

7 / 32

Simplified transistor equations

$V_{GS} - V_T \leq 0 < V_{DS}$ (subthreshold):

$$I_{DS} \approx 0$$

$0 < V_{GS} - V_T < V_{DS}$ (saturation):

$$I_{DS} = \mu C_{ox} \frac{W}{L} \frac{(V_{GS} - V_T)^2}{2}$$

$0 < V_{DS} < V_{GS} - V_T$ (linear):

$$I_{DS} = \mu C_{ox} \frac{W}{L} [(V_{GS} - V_T)V_{DS} - V_{DS}^2/2]$$

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

8 / 32

Digital abstraction

We will simplify all this to:

- If $V(g) > \min(V(s), V(d)) + v_{tn}$, current flows between s and d until $V(s) = V(d)$; otherwise no current flows.
- If $V(g) < \max(V(s), V(d)) + v_{tp}$, current flows between s and d until $V(s) = V(d)$; otherwise no current flows.

Note: $v_{tp} < 0, v_{tn} > 0$ for standard MOSFETs.

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018 9 / 32

Digital abstraction

Drawing transistors:



nFET: if $V(g)$ is “high” long enough, then $V(s) = V(d)$

pFET: if $V(g)$ is “low” long enough, then $V(s) = V(d)$

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018 10 / 32

Digital abstraction

Using an nFET:



Remember: current flows when

$$V(g) > \min(V(s), V(d)) + v_{tn}$$

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018 11 / 32

Digital abstraction

Using a pFET:



Remember: current flows when

$$V(g) < \max(V(s), V(d)) + v_{tp}$$

Yale

AVLSI


Manohar

EENG 426: Silicon Compilation

Fall 2018 12 / 32

Switching networks

In general, we have something like:

 

We only use pFETs in the pull-up and nFETs in the pull-down.

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

13 / 32

Production rules

$G \mapsto S$ is called a *production rule*

- S is $x \uparrow$ or $x \downarrow$
- G is a Boolean expression, called the *guard*

$$x \wedge y \mapsto z \uparrow$$

$$\neg x \mapsto u \downarrow$$

$$\neg x \mapsto u \downarrow$$

$$\neg x \mapsto v \uparrow$$

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

14 / 32

Inverting logic

CMOS is said to be “inverting.”

Given a one-stage circuit \mathcal{C} computing

$$y = \mathcal{C}(\mathbf{x})$$

where \mathbf{x} is a Boolean vector of inputs, we know that if any component of \mathbf{x} changes from *false* to *true*, the output changes from *true* to *false* or remains unchanged.

Why?

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

15 / 32

Production rules

What can we say about a CMOS gate represented by a production rule?

- $x \wedge y \mapsto u \uparrow$

- $x \wedge y \mapsto u \downarrow$

- $\neg(a \vee b) \mapsto c \uparrow$

Yale

AVLSI



Manohar

EENG 426: Silicon Compilation

Fall 2018

16 / 32

Ratioless logic

 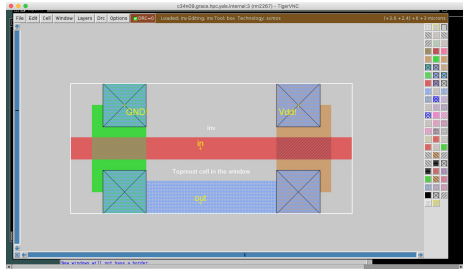

in	out
0	1
1	0

$$R_{on} \approx 10^4 \Omega$$

$$R_{off} \approx 10^9 \Omega$$

Yale

AVLSI


Manohar

EENG 426: Silicon Compilation

Fall 2018

17 / 32

Switches

 

Switch is controlled by $V(c)$.

$$c \Rightarrow (a = b)$$

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

18 / 32

Computing with switches

Use the switches to set nodes to specific voltages.

The voltage could come from:

- Power supply
- Another node

Restoring logic switches power supplies.

Pass gate logic switches other nodes.

Yale

AVLSI


Manohar

EENG 426: Silicon Compilation

Fall 2018

19 / 32

Switches in CMOS

 

A restoring inverter using switches?

NAND? NOR?

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

20 / 32

Pass gates

Pros and Cons:

- Can reduce transistor count
- Can reduce logic stages (non-inverting logic)
- Does not restore signals!
- Unintended “sneak” paths

Yale

AVLSI

Manohar


EENG 426: Silicon Compilation

Fall 2018

21 / 32

Multiplexer

A 2-input MUX:

 

Terrible!

Yale

AVLSI


Manohar

EENG 426: Silicon Compilation

Fall 2018

22 / 32

Restoring multiplexer

 

$$\begin{aligned}(\neg x \wedge c) \vee (\neg y \wedge \neg c) &\mapsto \neg z \uparrow \\(x \wedge c) \vee (y \wedge \neg c) &\mapsto \neg z \downarrow\end{aligned}$$

Yale

AVLSI


Manohar

EENG 426: Silicon Compilation

Fall 2018

23 / 32

Pass gate MUX

 

Simple and fast, but it doesn't restore the quality of the logic signals.

Yale

AVLSI

Manohar


EENG 426: Silicon Compilation

Fall 2018

24 / 32

Pass gate MUX

To restore the pass gate MUX signals:

 

Can we simplify this?

Simple functions: static CMOS

If we want to compute the Boolean function $f(\mathbf{x})$:

- Pull-up switching network: $f(\mathbf{x})$
- Pull-down switching network: $\neg f(\mathbf{x})$

The net result: the output is *always* connected to a power supply.

$$f(\mathbf{x}) \mapsto z \uparrow$$

$$\neg f(\mathbf{x}) \mapsto z \downarrow$$

Production rules

A CMOS gate is of the form:

$$B^+ \mapsto z \uparrow$$

$$B^- \mapsto z \downarrow$$

We require: $\neg(B^+ \wedge B^-)$ **non-interference**

Gates come in two flavors:

- $B^+ \vee B^- \Rightarrow$ the gate is **combinational** or **static**
(This is the same as $B^+ = \neg B^-$)
- $B^+ \neq \neg B^- \Rightarrow$ the gate is **state-holding** or **dynamic**

Production rules

$$b_1 \vee z \mapsto z \uparrow$$


$$b_2 \vee \neg z \mapsto z \downarrow$$

$$b_1 \vee \neg z \mapsto z \uparrow$$

$$b_2 \vee z \mapsto z \downarrow$$


$$z \mapsto \neg z \downarrow$$

$$\neg z \mapsto \neg z \uparrow$$

 

Production rules
 
$$b_1 \vee \neg b_2 \wedge \neg z \mapsto z \uparrow$$
$$b_2 \vee \neg b_1 \wedge z \mapsto z \downarrow$$



Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

29 / 32

Production rules

An *execution* of $G \mapsto S$ is an unbounded sequence of *firings*.

- If G is **true**, the firing amounts to executing S
- If G is **false**, the firing amounts to a **skip**
- If a firing changes the state, it is *effective*; otherwise it is *vacuous*

The execution of a production rule set:

- the parallel composition of the individual production rules in the set
- assumption is “weak fairness”: a specific production rule will get a chance to fire *eventually*

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

30 / 32

Production rules

Stability: an important property of a production rule.

A production rule $G \mapsto x \uparrow$ is *stable* in a computation iff

- G can change from **true** to **false** only if x is **true**
- Alternatively: G can change from **true** to **false** only in states where a firing would be vacuous

(Similar for $G \mapsto x \downarrow$)

What happens in the circuit if a production rule is *unstable*?

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

31 / 32

Production rules

If all production rules in a set are stable, then their execution is equivalent to the following:

- Repeat the following steps forever:
 - 1 Pick one production rule (in a weakly fair fashion) from the production rule set;
 - 2 Fire the selected rule

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

32 / 32