



Physical Implementation: Timing constraints

Rajit Manohar

Asynchronous VLSI and Architecture (AVLSI) Group
Computer Systems Lab, Yale University

<https://cs1.yale.edu/~rajit/>
<https://avlsi.cs1.yale.edu/act>

So far...

- Behavioral modeling
 - ❖ Message-passing programming in CHP
 - ❖ Dataflow graphs
 - ❖ Links and joints
- Gate-level design
 - ❖ Link-joint implementations
 - ❖ Controllers for dataflow components
 - ❖ Syntax-directed translation
- Multiple circuit families!
 - ❖ ... for channels
 - ❖ ... for links
 - ❖ ... for controllers

Why use different circuit families?

- Sufficiently **different costs** in energy, delay, area, and implementation effort
 - ❖ Implementation effort = effort to validate any *timing* requirements
- Basic intuition on the trade-offs
 - ❖ A circuit is robust to large uncertainty in the delay of a signal/gate if some other circuit checks that it has changed
 - ⇒ this has a cost in circuits, and hence area, delay, energy
 - ❖ If we eliminate this cost and the circuit is **not** robust, then we must **check** that the timing requirements are met
- Examples of delay-robustness
 - ❖ Quasi delay-insensitive (QDI) / Speed-independent (SI)
 - ▶ Correct behavior is ***independent*** of gate delay
 - ▶ Some wire forks have a relative delay requirement

Why use different circuit families?

- Example: MOUSETRAP


Timing Analysis

Setup constraint: matched delay

Hold Time constraint:

Data must be safely "captured" by Stage N before new inputs arrive from Stage N-1

 
- Stage N's "self-loop" faster than entire path through previous stage



18

Timing requirements

 - In order of verification complexity...
 - ❖ Local to a small module
 - ❖ Between neighboring modules that exchange data
 - ❖ Paths across multiple modules
- A common approach to describe constraints: **relative timing**
 - ❖ “A signal transition $x+$ must happen before $y-$ ”
 - ❖ “The data must change before the request goes high”




Timing constraints in ACT

- Associate an “iteration counter” with circuit


```
*[ S ] // infinite loop
```

- Each signal transition “x+” / “x-” has an iteration counter attached to it
 - ❖ Some transitions connect iteration “i” to iteration “i+1”
 - ❖ This is determined during logic synthesis

- A timing fork

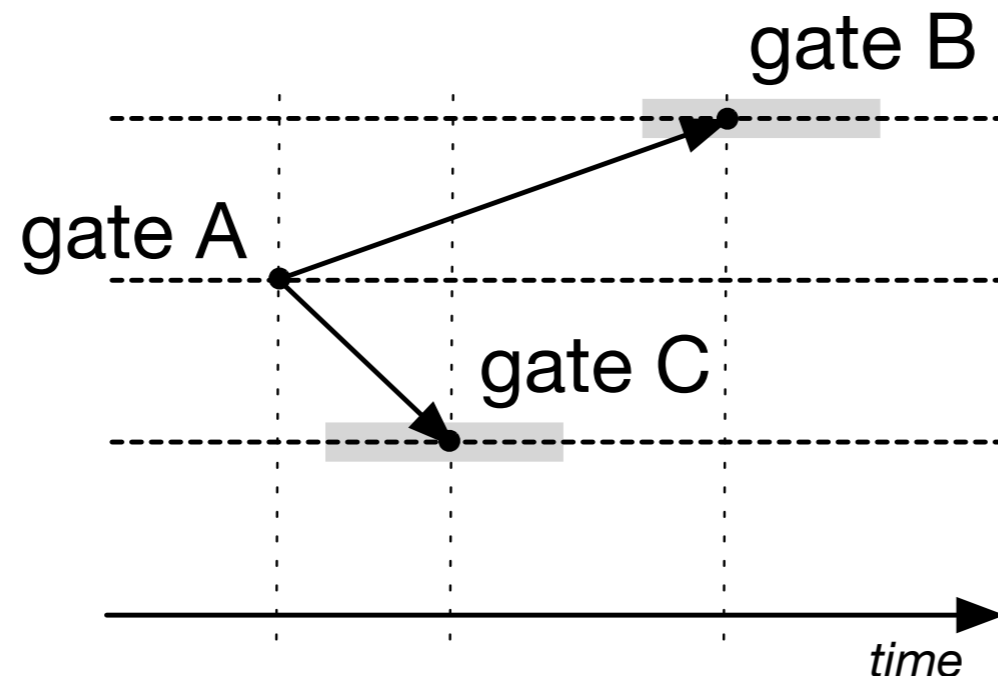

Timing constraints in ACT

 

- **maximum delay** from A to C < **minimum delay** from A to B

```
spec {  
    timing a+ : c+ < b-  
}
```

Timing constraints in ACT

- Example: bundled-data channel

```
template< pint M>
defchan bd (bool d[M]; bool r, a)
{
  spec {
    /* timing fork */
    timing a- : d* < r*+
  }
  ...
}
```

The standard channel definitions in `std::channel` include timing constraints, so those will be automatically included.

`actsim` and `prsim` check constraints during simulation.

Gate level specification

- Circuits specified using production rules
- Timing
 - ❖ Constraints specified in channels and/or controllers
 - ❖ Relation between one iteration to the next also specified
 - ▶ This is determined during logic synthesis
 - ▶ This can also be computed using the chip reset protocol
- Delay annotations for more accurate timing simulation

```
prs {  
    [after=25] a -> b-  
}
```