



ASIC flow: mapping to cells


Rajit Manohar

**Asynchronous VLSI and Architecture (AVLSI) Group
Computer Systems Lab, Yale University**

<https://cs1.yale.edu/~rajit/>
<https://avlsi.cs1.yale.edu/act>

Basic idea

 - Convert entire design into a set of pre-defined blocks (“cells”)
 - ❖ Examples
 - ▶ two-input NAND gate
 - ▶ two-input C-element
 - ▶ inverters with different sizing
 - ▶ ... etc ...
- Each cell is implemented at the transistor-level *once*
 - ❖ Rectangular geometry with input/output connection points (“pins”)



*Example from Skywater 130 library
for synchronous logic*

<https://antmicro-skywater-pdk-docs.readthedocs.io>

Input: gate-level design in ACT

- Gate level design can have
 - ❖ Explicitly instantiated cells
 - ❖ Production rules

- Explicitly instantiated cells
 - ❖ We use your cell instances as specified
 - ❖ Each cell needs a physical implementation
 - ❖ Example:
 - ▶ Mapping arithmetic (e.g. “ $x + y$ ”) using logic synthesis results in a collection of gates selected by the logic synthesis tool
 - ❖ A *technology-independent* cell library for combinational logic is available, based on James Stine’s open-source library in 180nm (“OSU library”)

Input: gate-level design in ACT

- Production rule mapping

```
prs {  
    A & B #> Y-  
  
    Y<30> -> W-  
    ~Y<30> -> W+  
}
```

- Unique cells are identified

```
A & B -> Y-  
~A & ~B -> Y+
```

```
Y<30> -> W-  
~Y<30> -> W+
```

- ACT is re-written to explicitly instantiate these cells
 - ❖ An ACT cell library is generated, consisting of unique production rules across the design
 - ❖ An existing ACT cell library can be re-used, and is extended if necessary

Open-source ACT based on OSU library

```
export defcell NOR2X1 (bool? A, B; bool! Y)
{
  prs {
    A | B => Y-
  }
  sizing { Y {-1} }
}
```

ACT cell

```
.subckt NOR2X1 vdd B gnd Y A
M0 a_9_54# A vdd vdd pfet w=4u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M1 Y B a_9_54# vdd pfet w=4u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M2 Y A gnd Gnd nfet w=1u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M3 gnd B Y Gnd nfet w=1u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
.ends NOR2X1
```

Original
OSU cell

Open-source ACT based on OSU library

```
.subckt HAX1 vdd gnd YC A B YS
M0 vdd A a_2_74# vdd pfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M1 a_2_74# B vdd vdd pfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M2 vdd a_2_74# YC vdd pfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M3 a_41_74# a_2_74# vdd vdd pfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M4 a_49_54# B a_41_74# vdd pfet w=4u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M5 vdd A a_49_54# vdd pfet w=4u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M6 YS a_41_74# vdd vdd pfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M7 a_9_6# A gnd Gnd nfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M8 a_2_74# B a_9_6# Gnd nfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M9 gnd a_2_74# YC Gnd nfet w=1u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M10 a_38_6# a_2_74# gnd Gnd nfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M11 a_41_74# B a_38_6# Gnd nfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M12 a_38_6# A a_41_74# Gnd nfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M13 YS a_41_74# gnd Gnd nfet w=1u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
.ends HAX1
```

Original
OSU cell

Open-source ACT based on OSU library

```
export defcell HAX1 (bool? A, B; bool! YC, YS)
{
  bool __YC, __YS;
  prs {
    A & B ==> __YC-
    __YC ==> YC-

    __YC & (A | B) ==> __YS-
    __YS ==> YS-
  }
  sizing { __YC{-1}; YC{-1}; __YS{-1}; YS{-1} }
}
```

```
.subckt HAX1 vdd gnd YC A B YS
M0 vdd A a_2_74# vdd pfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M1 a_2_74# B vdd vdd pfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M2 vdd a_2_74# YC vdd pfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M3 a_41_74# a_2_74# vdd vdd pfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M4 a_49_54# B a_41_74# vdd pfet w=4u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M5 vdd A a_49_54# vdd pfet w=4u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M6 YS a_41_74# vdd vdd pfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M7 a_9_6# A gnd Gnd nfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M8 a_2_74# B a_9_6# Gnd nfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M9 gnd a_2_74# YC Gnd nfet w=1u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M10 a_38_6# a_2_74# gnd Gnd nfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M11 a_41_74# B a_38_6# Gnd nfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M12 a_38_6# A a_41_74# Gnd nfet w=2u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
M13 YS a_41_74# gnd Gnd nfet w=1u l=0.2u
+ ad=0p pd=0u as=0p ps=0u
.ends HAX1
```

ACT cell

Original
OSU cell

Usage scenarios

- “I have all my cells and they have been instantiated already!”

- ❖ ACT can use your cells as “black box” components

- ❖ For each cell, we will need

- ▶ Black-box: declare cell but do not provide a definition

```
export defcell MY_TWO_INPUT_CELL (bool? A, B; bool! Y);
```

- ▶ LEF, GDS, timing information from .lib (as in a normal cell library)

- Using an existing physical design flow? (e.g. a commercial tool)


- ❖ Map everything to cells

- ❖ Export Verilog netlist or DEF file

- ❖ Use your cell library


Usage scenarios

 - “I don’t have any cells!”
 - ❖ The ACT flow can get you started...
 - ▶ Initial placement of transistors, ready to be wired up
 - ▶ Key requirement: “Skyline” layout



- “I have some cells, but not sure if I have them all”
 - ❖ ACT will let you know if there are any missing cells when mapping to the design

ACT supports *gridded* cells

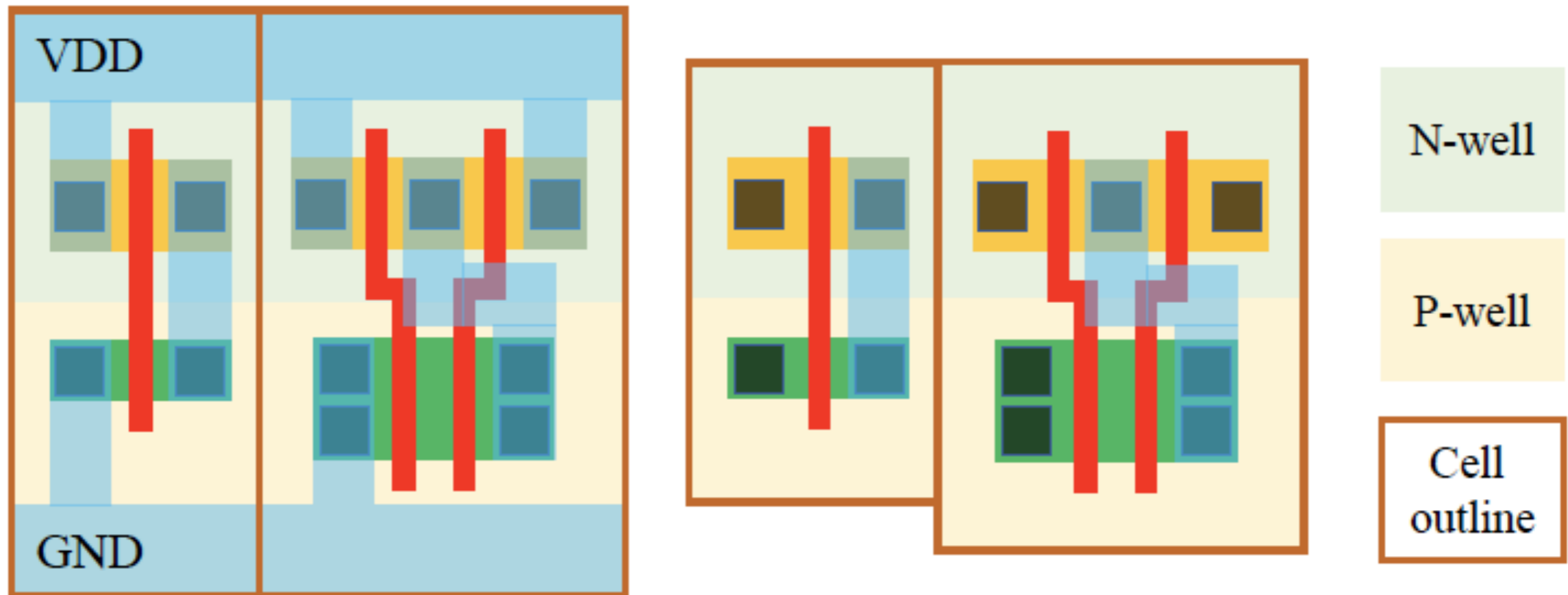

“Standard” cells

most cells are fixed height (e.g. 12 tracks), width is integer multiple of tracks; some “multi-height” cells

“Gridded” cells

cells width and height is integer multiple of tracks; can have “multi-deck” cells