

Custom async circuit design from production rules to netlist

Benjamin Hill

benjamin.hill@intel.com

ASYNC Summer School 2022

Legal Information

Intel does not control or audit third-party data. You should consult other sources to evaluate accuracy.

Your costs and results may vary.

Results have been estimated or simulated

Intel disclaims all express and implied warranties, including without limitation, the implied warranties of merchantability, fitness for a particular purpose, and non-infringement, as well as any warranty arising from course of performance, course of dealing, or usage in trade.

No license (express or implied, by estoppel or otherwise) to any intellectual property rights is granted by this document.

© Intel Corporation. Intel, the Intel logo, and other Intel marks are trademarks of Intel Corporation or its subsidiaries. Other names and brands may be claimed as the property of others.

Implementing custom circuit designs

Our task:



Given a gate-level system expressed as production rule set (PRS),
generate netlist (SPICE) and physical implementation (layout)

Do as little full custom design as possible!



Stay tuned for later sessions describing more automated
parts of the Yale physical implementation flow

Production rule basics

  $\sim a \ \& \ \sim b \ \rightarrow \text{out}+$





$a \ \& \ b \ \rightarrow \text{out}-$

 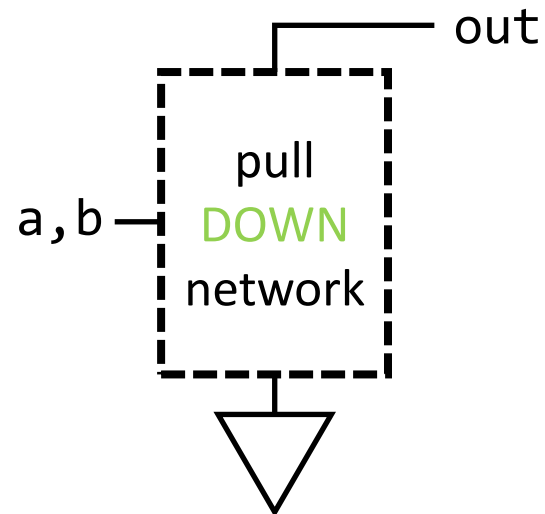


Production rule sets form gates

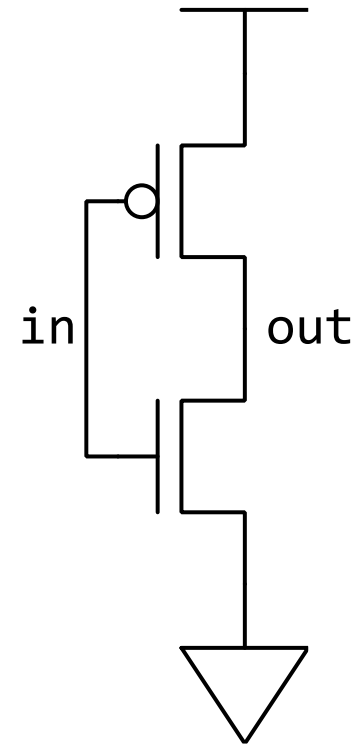 $\sim in \rightarrow out+$
 $in \rightarrow out-$




Custom design flow

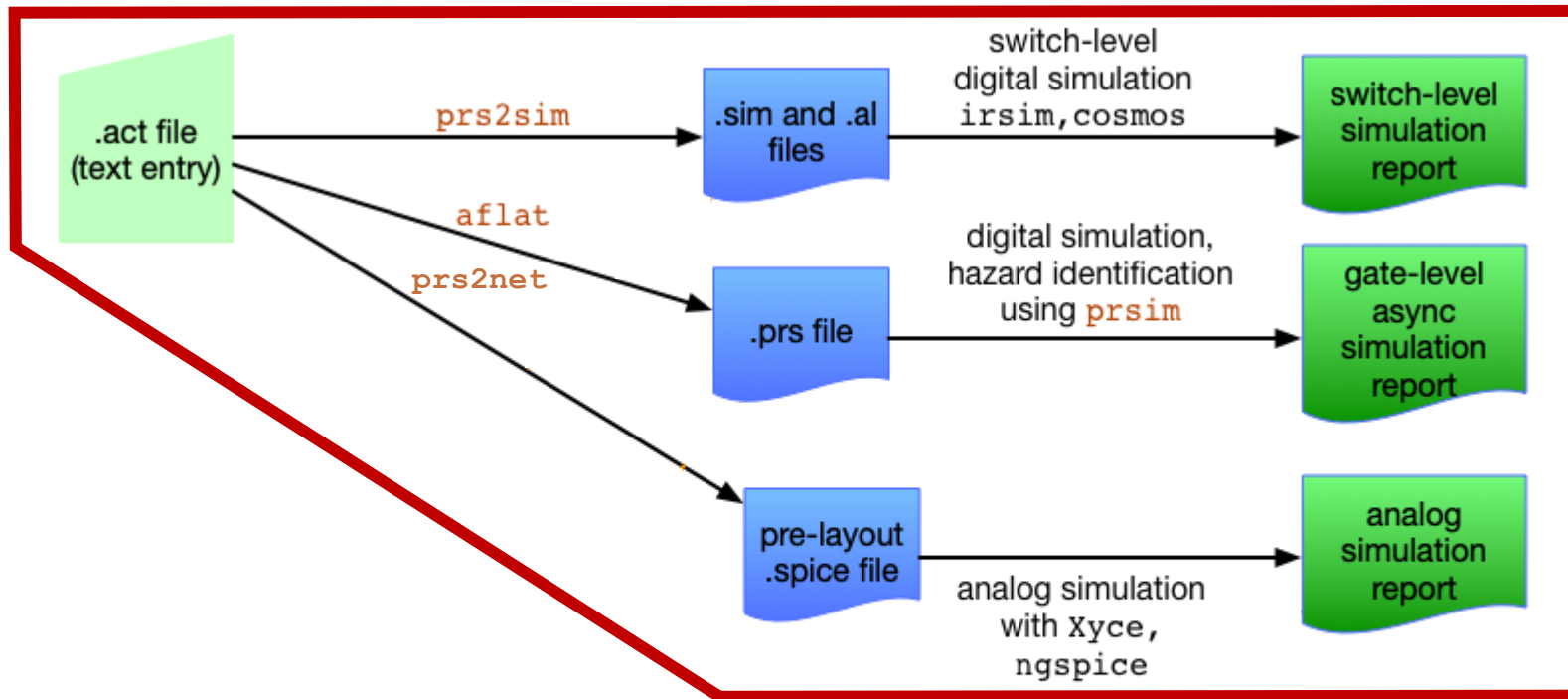

toolname: *existing open-source tools*
toolname: *ACT tools*

CMOS transistors



CMOS transistors

 

PMOS

conducts current
between source and drain
(through P-type channel)
when gate is **LOW**

voltage-controlled

  



NMOS

conducts current
between source and drain
(through N-type channel)
when gate is **HIGH**



PMOS

NMOS


schematic
symbol

  




layout
(top down view)

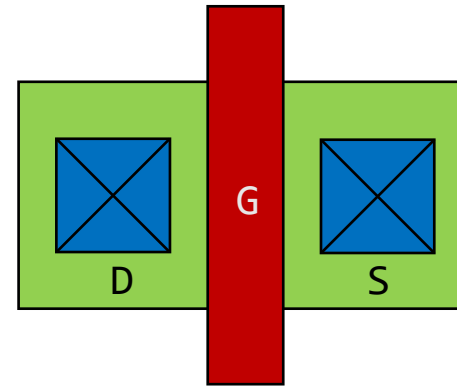 


cross section

 


CMOS transistors

  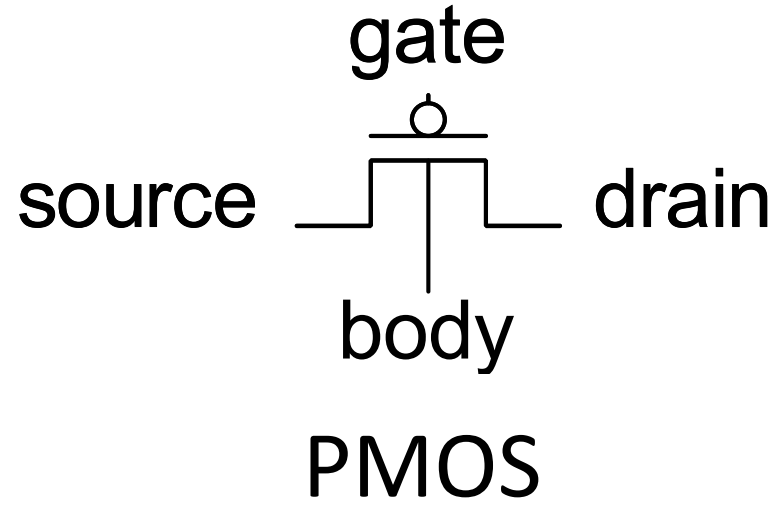


Transistor operation: cutoff

 


PMOS

 


NMOS

 


Transistor operation: channel formation

 


PMOS

 


NMOS

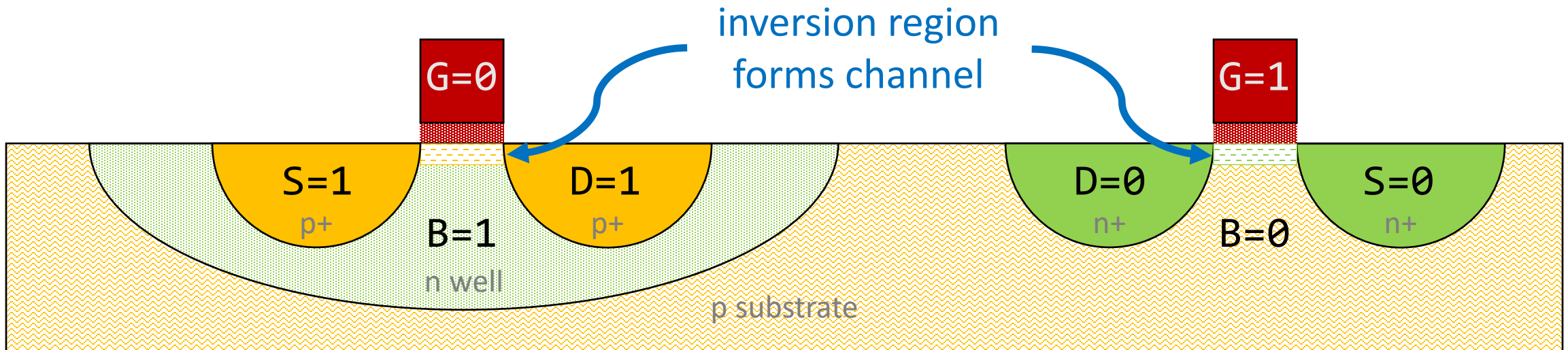


Transistor operation: saturation

 


PMOS

 


NMOS

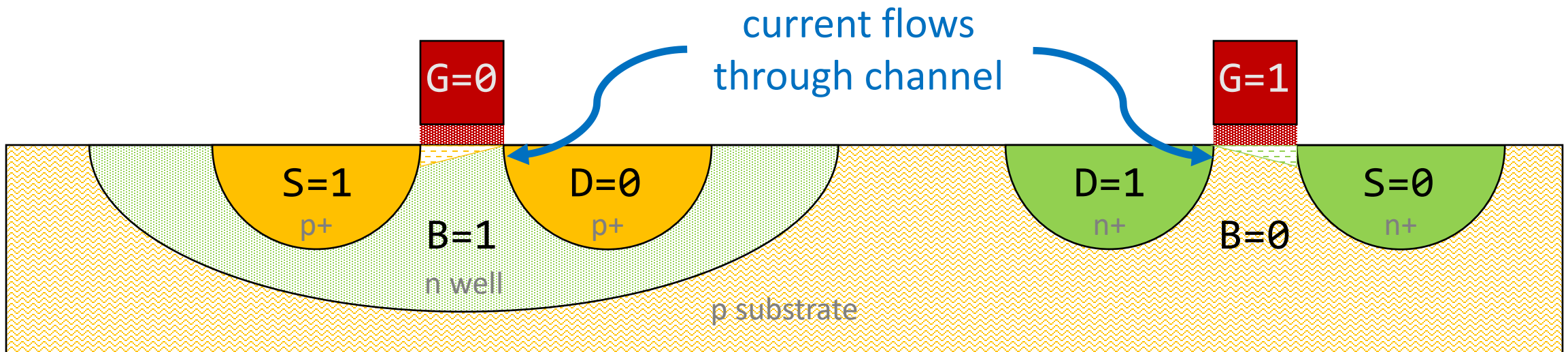


Transistor operation: cutoff

 


PMOS

 

NMOS

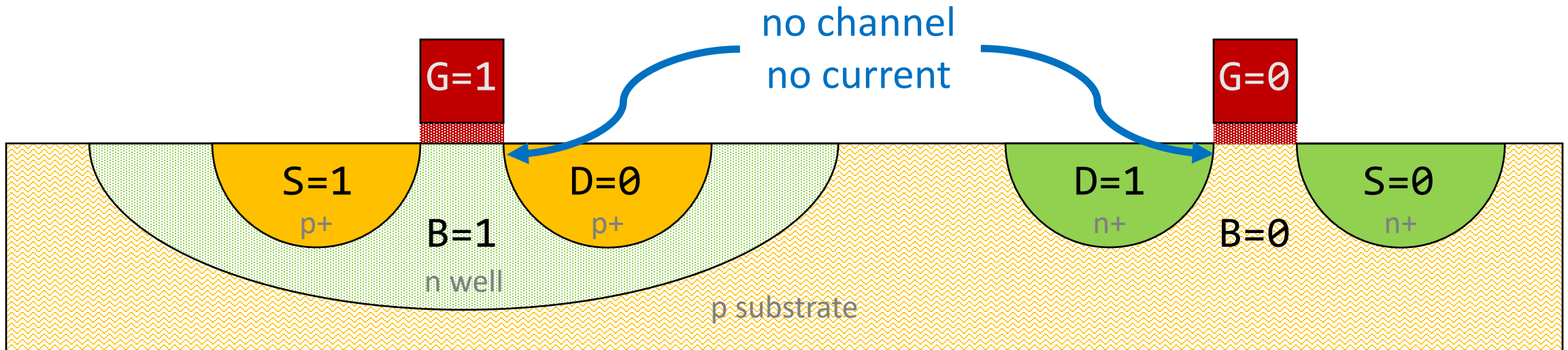


CMOS transistors

 

PMOS

 conducts current
between source and drain
(through P-type channel)
when gate is **LOW**



NMOS

conducts current
between source and drain
(through N-type channel)
when gate is **HIGH**


voltage-controlled

switch





Layout and sizing

Layout example: inverter

 

in	out
0	1
1	0

  


Design rules

set of geometric restrictions intended to yield high probability of correct fabrication, operation, and lifetime

Table 3 Table 2 - Minimum CDs in Design or on Wafer, required by Technology (Core or Periphery)


Layer Name	Feature Size	Space Size	Feature Name	Space Name
Field Oxide	0.14	0.27	FOMCD	FOMCDSP
Deep N-Well	3	6.3	DNMCD	DNMCDSP
P-Well Block Mask	0.84	1.27	PWBMCD	PWBMCDSP
P-Well Drain Extended	0.84	1.27	PWDEMCD	PWDEMCDSP
N-Well	0.84	1.27	NWMCD	NWMCDSP
Metal 1	0.14	0.14	MM1CD	MM1CDSP
Metal 1 - Cu	0.14	0.14	MM1_CuCD	MM1_CuCDSP
Via	0.15	0.17	VIMCD	VIMCDSP
Via - Cu	0.18	0.13	VIM_CuCD	VIM_CuCDSP
Capacitor MIM	2	0.84	CAPMCD	CAPMCDSP
Metal 2	0.14	0.14	MM2CD	MM2CDSP
Metal 2 - Cu	0.14	0.14	MM2_CuCD	MM2_CuCDSP
Via 2-TNV	0.28	0.28	VIM2CD	VIM2CDSP
Via 2-S8TM	0.8	0.8	VIM2CD	VIM2CDSP

 

Transistor sizing

Skywater 130 simplified design rules

λ	75 nm*
L	2λ
W_N	6λ
W_P	10λ

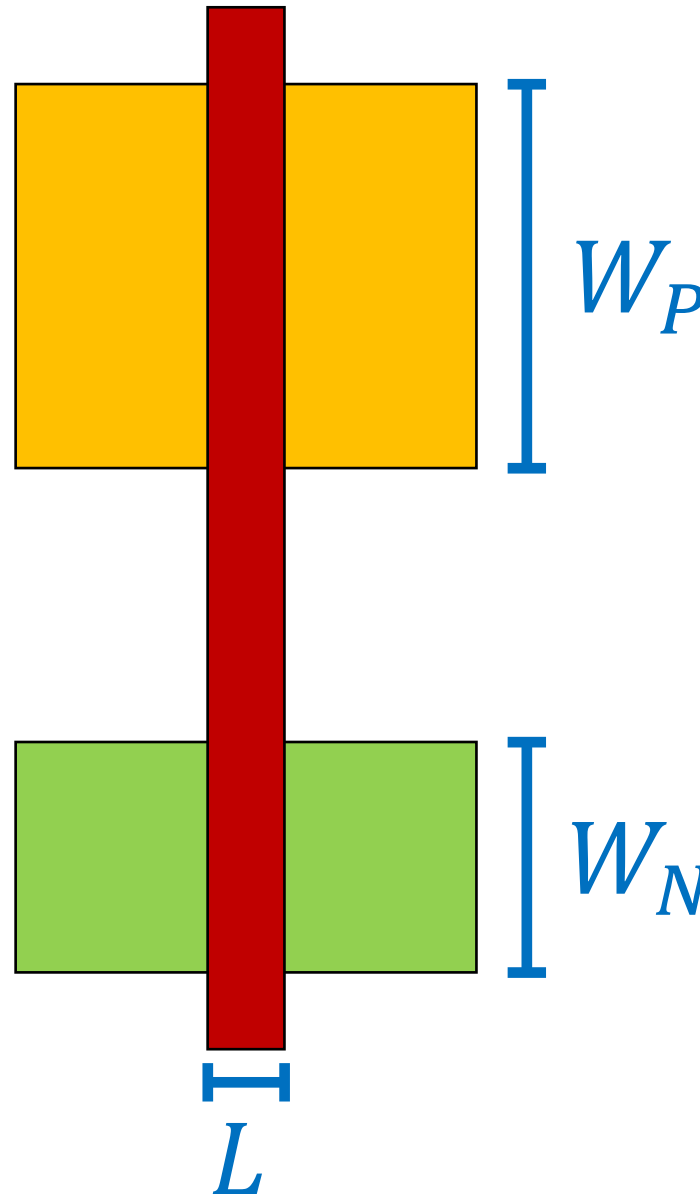

* minimum feature size for Skywater 130
is 150nm transistor gate length


Sizing – how and why

- W, L, lambda
- ACT sizing body, prs body, default config
- Gates drive capacitance: think of simple R-C circuit
- Switching burns energy: charge and discharge capacitor
- Always trading off energy/area/performance

Transistor performance scaling intuition


Transistor device with
width and length parameters

What happens as we vary them?

 


Analogy: resistors

Decreased resistance,
increased current

 
 
$$R_{parallel} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R}{2}$$




$$R_{series} = R_1 + R_2 = 2R$$

current through resistor
(aka “drive strength”)
is inversely proportional to
effective resistance


$$I = \frac{V}{R}$$

Increased resistance, decreased current

Transistor performance scaling intuition

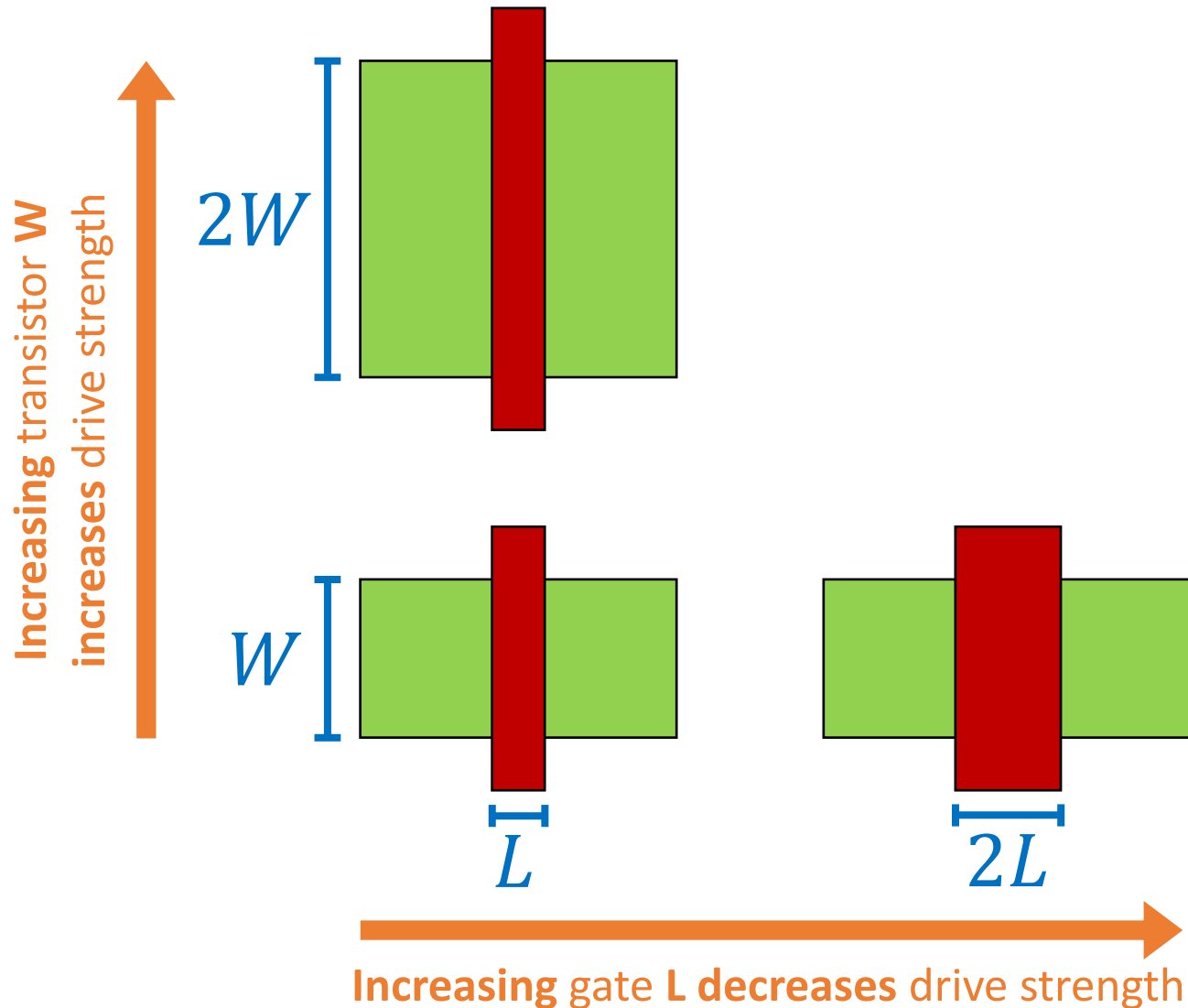

 Key performance metric:
current through transistor
effective resistance
“drive strength”



Digital designer summary

Use NMOS in pull-down network, PMOS in pull-up

⇒ single stage logic is always inverting

Transistor drive strength $\propto \frac{\textit{Width}}{\textit{Length}}$

⇒ use minimum gate length for digital logic (usually)

State-holding gates

Combinational vs state-holding gates

Combinational


- Either **UP** or **DOWN** (but not both) is always conducting

State-holding


- At times neither **UP** nor **DOWN** is conducting
- out is undriven and maintains its previous value

Interfering

 - Both **UP** and **DOWN** conducting simultaneously
- Causes short-circuit/crowbar current through gate, should not be more than transient




 Example state-holding gate: Muller C-element




$a \ \& \ b \ \rightarrow \text{out}+$
 $\sim a \ \& \ \sim b \ \rightarrow \text{out}-$

not CMOS implementable!

 

$a \ \& \ b \ \rightarrow \text{_out}-$
 $\sim a \ \& \ \sim b \ \rightarrow \text{_out}+$
 $\text{_out} \ \rightarrow \text{out}-$
 $\sim \text{_out} \ \rightarrow \text{out}+$

inverting C-element plus inverter

 


$a \ \& \ b \ \# \rightarrow \text{_out}-$
 $\text{_out} \ \Rightarrow \text{out}-$

shorthand syntax


a	b	out
0	0	0
0	1	hold previous state
1	0	hold previous state
1	1	1

Problem: undriven dynamic nodes

 

$a \ \& \ b \ \rightarrow \ _out-$
 $\sim a \ \& \ \sim b \ \rightarrow \ _out+$



a	b	_out
0	0	1
0	1	hold previous state
1	0	hold previous state
1	1	0

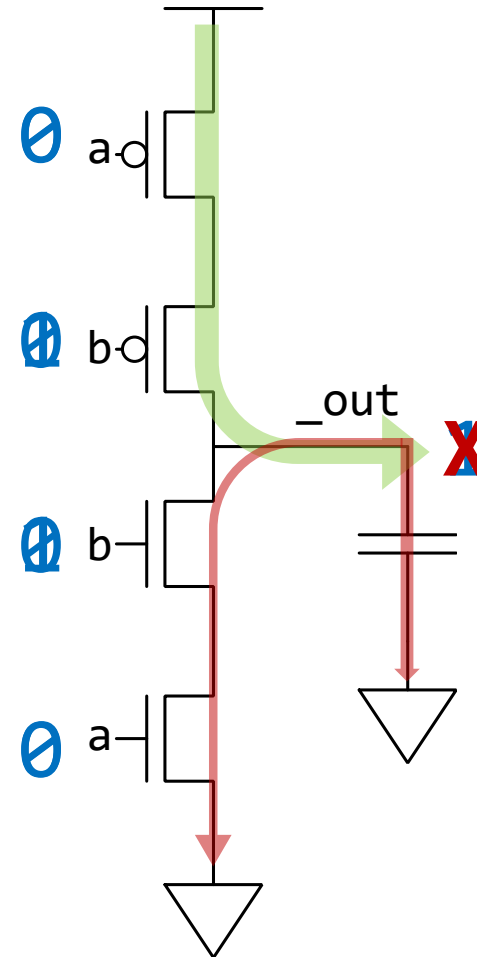

Solution: staticizers

C-element PRS to SPICE example
  
```
defproc celem (bool? a,b; bool! out)
{
  bool _out;
  prs {
    a & b #> _out-
    _out => out-
  }
}
```



SPICE basics

Define new subcircuit (cell):
`.subckt name ports`

Comments begin with *
Metadata generated by prs2net

MOSFET instances:
`Mname D G S B type <param=val>`

End of inv subcircuit:

Instantiate subcircuits hierarchically:
`xname ports cellname`

```
*----- act defproc: inv<> -----
* raw ports:  in out
.subckt inv in out
*.PININFO in:I out:O
*.POWER VDD Vdd
*.POWER GND GND
*.POWER NSUB GND
*.POWER PSUB Vdd
* --- node flags ---
* out (combinational)
* --- end node flags ---
M0_ Vdd in out Vdd p W=1.5U L=0.6U
M1_ GND in out GND n W=0.9U L=0.6U



.ends
*----- end of process: inv<> -----

*----- act defproc: buf<> -----
* raw ports:  in out
.subckt buf in out
xstage1 in __out inv
xstage2 __out out inv
.ends
*----- end of process: buf<> -----
```

C-element PRS to SPICE example



C-element with weak keeper staticizer
  
```
defproc celem (bool? a,b; bool! out)
{
  bool _out;
  prs {
    a & b #> _out-
    _out => out-
  }
}
```



C-element with combinational feedback

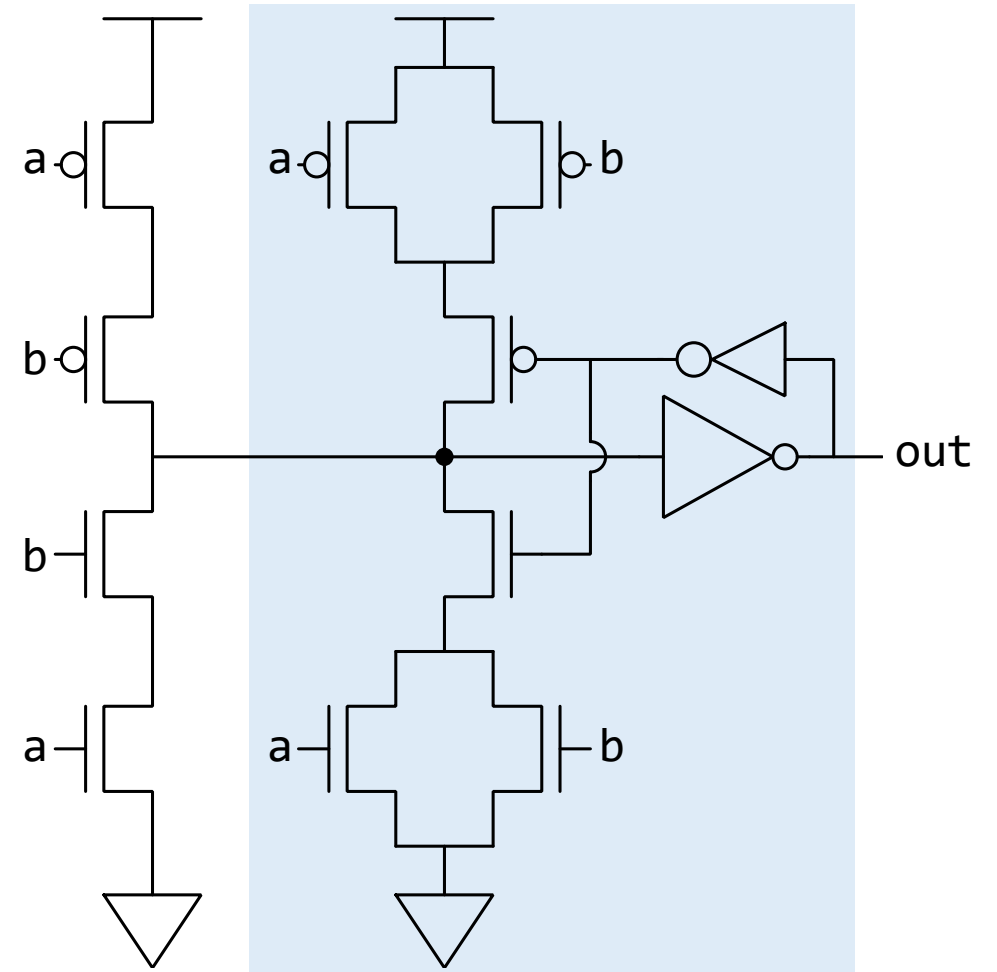
 
```
defproc celem_comb (bool? a,b; bool! out)
{
  bool _out;
  prs {
    [comb=1] a & b #> _out-
    _out => out-
  }
}
```



van Berkel C-element

```
defproc celem_H (bool? a,b; bool! out)
{
  bool _out;
  bool nmid[2], pmid[2];
  prs {
    // N-stack
    [keeper=0] a -> nmid[0]-
    [keeper=0] b -> nmid[1]-
    passn (out, nmid[0], nmid[0])
    passn (b, nmid[0], _out)
    passn (a, nmid[1], _out)

      // Symmetric P-stack, out inverter
    ...
  }
}
```




Simulation options

	Gate level	Switch level	Analog
simulator	prsim, actsim	irsim	Xyce
input	ACT PRS	.sim	SPICE
to generate	write directly or use e.g. chp2prs	prs2sim	prs2net
model	unit delay	RC delay	full analog
fidelity	lowest	medium	highest
speed	fastest	fast	slow

Full custom flow example

Design specification

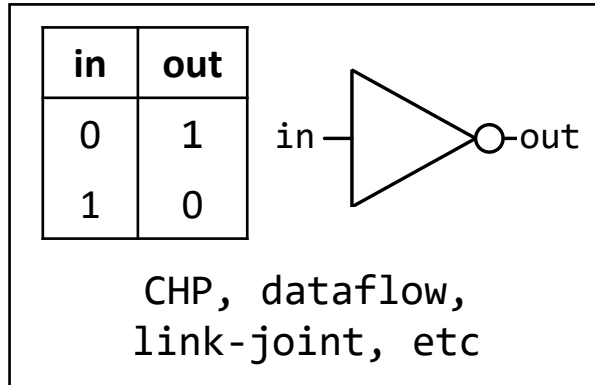

write or
compile

Production rules

```
defproc inv (bool? in; bool! out)
{
  prs { in => out- }
}
```

prs2net
prs2sim


Netlist (SPICE)

```
*---- act defproc: inv<> ----
.subckt inv in out
*.PININFO in:I out:O
*.POWER VDD Vdd
*.POWER GND GND
*.POWER NSUB GND
*.POWER PSUB Vdd
* --- node flags ---
* out (combinational)

M0_ Vdd in out Vdd p W=1.5U L=0.6U
M1_ GND in out GND n W=0.9U L=0.6U

.ends
*---- end of process: inv<> ----
```

Schematic

 

full custom or
semi-automated

extracted
parasitics

Layout

