 


Week 2: Gate-level design



Schedule

9:00 AM	Recap of models; handshake protocols
9:50 AM	<i>break</i>
10:00 AM	Gates and gate-level simulation
10:25 AM	<i>break</i>
10:30 AM	Pipeline example
11:00 AM	<i>break</i>
11:10 AM	Syntax-directed translation to cells
12:15 PM	Non-determinism
12:45 PM	Q&A
1:00 PM	End of Day 2

Recap of previous week: message-passing abstraction

```
defproc buffer(chan?(int) L; chan!(int) R)
{
  int x; // local state

  chp {
    *[ L?x; R!x ]
  }
}
```

```
defproc gcd(chan?(int) X, Y; chan!(int) O)
{
  int x, y; // local state

  chp {
    *[ X?x, Y?y;
      *[ x > y -> x := x - y
        [] y > x -> y := y - x
      ];
      O!x
    ]
  }
}
```



```
defproc alu(chan?(int<2>) cmd;
            chan?(int) X, Y; chan!(int) O)
{
  int x, y; // local state
  int<2> c;

  chp {
    *[ X?x, Y?y, cmd?c;
      [c=0 -> O!(x + y)
        []c=1 -> O!(x - y)
        []c=2 -> O!(x & y)
        []c=3 -> O!(x | y)
      ]
    }
}
```

CHP = Communicating Hardware Processes

Recap of previous week: dataflow abstraction

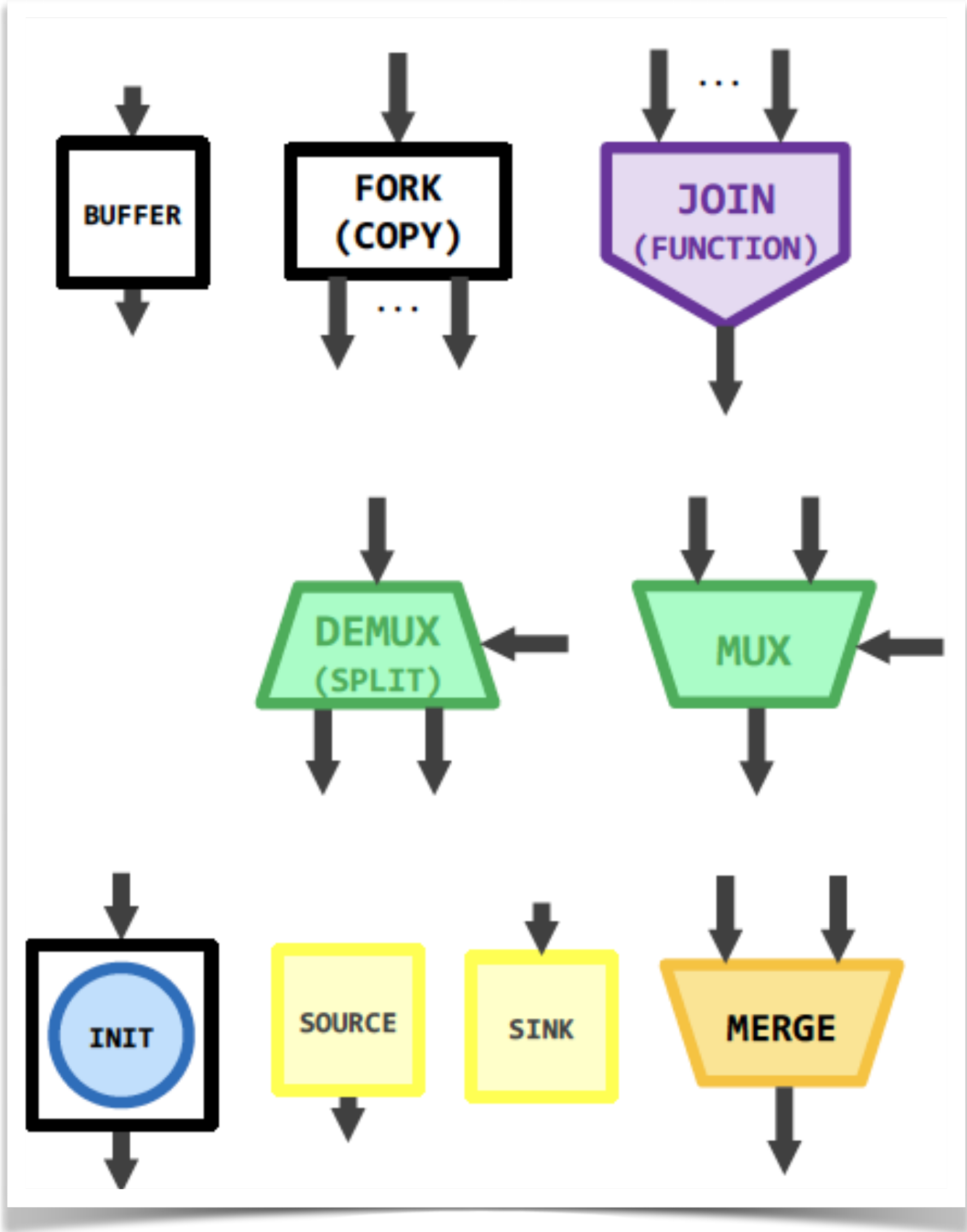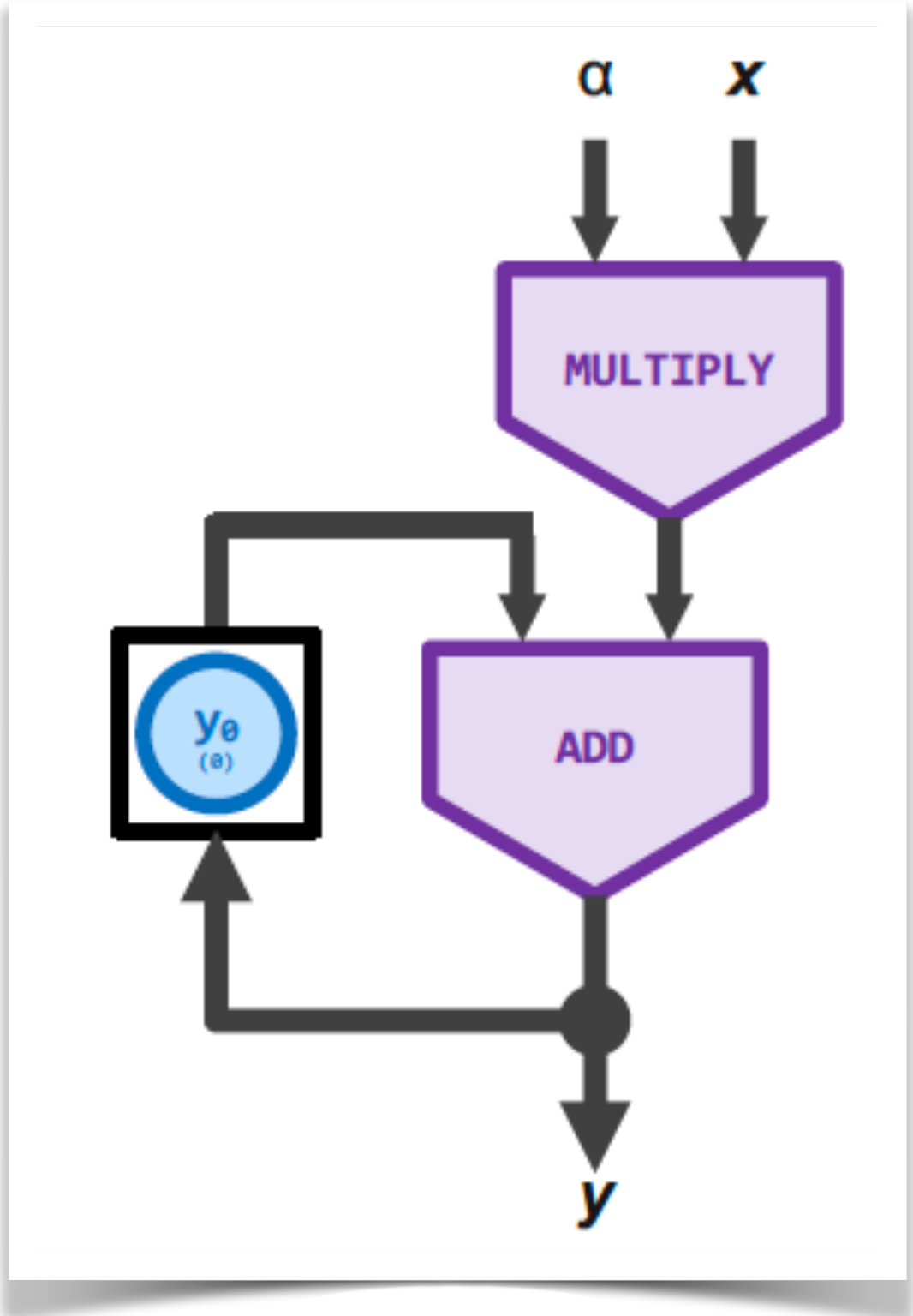- Dataflow model of computation
 - ▶ Tokens flowing through pipelines
 - ▶ Each component operates in parallel
- Each dataflow component can be written as a CHP program




From message-passing to signals


- Variables
 - ❖ Integers can be implemented as an array of signals (bool)
- What about channels?

```
defproc alu(chan?(int<2>) cmd;  
           chan?(int) X, Y; chan!(int) O)  
{  
  int x, y; // local state  
  int<2> c;  
  
  chp {  
    *[ X?x, Y?y, cmd?c;  
      [c=0 -> O!(x + y)  
      [ ]c=1 -> O!(x - y)  
      [ ]c=2 -> O!(x & y)  
      [ ]c=3 -> O!(x | y)  
    ]  
  }  
}
```



Channels

 

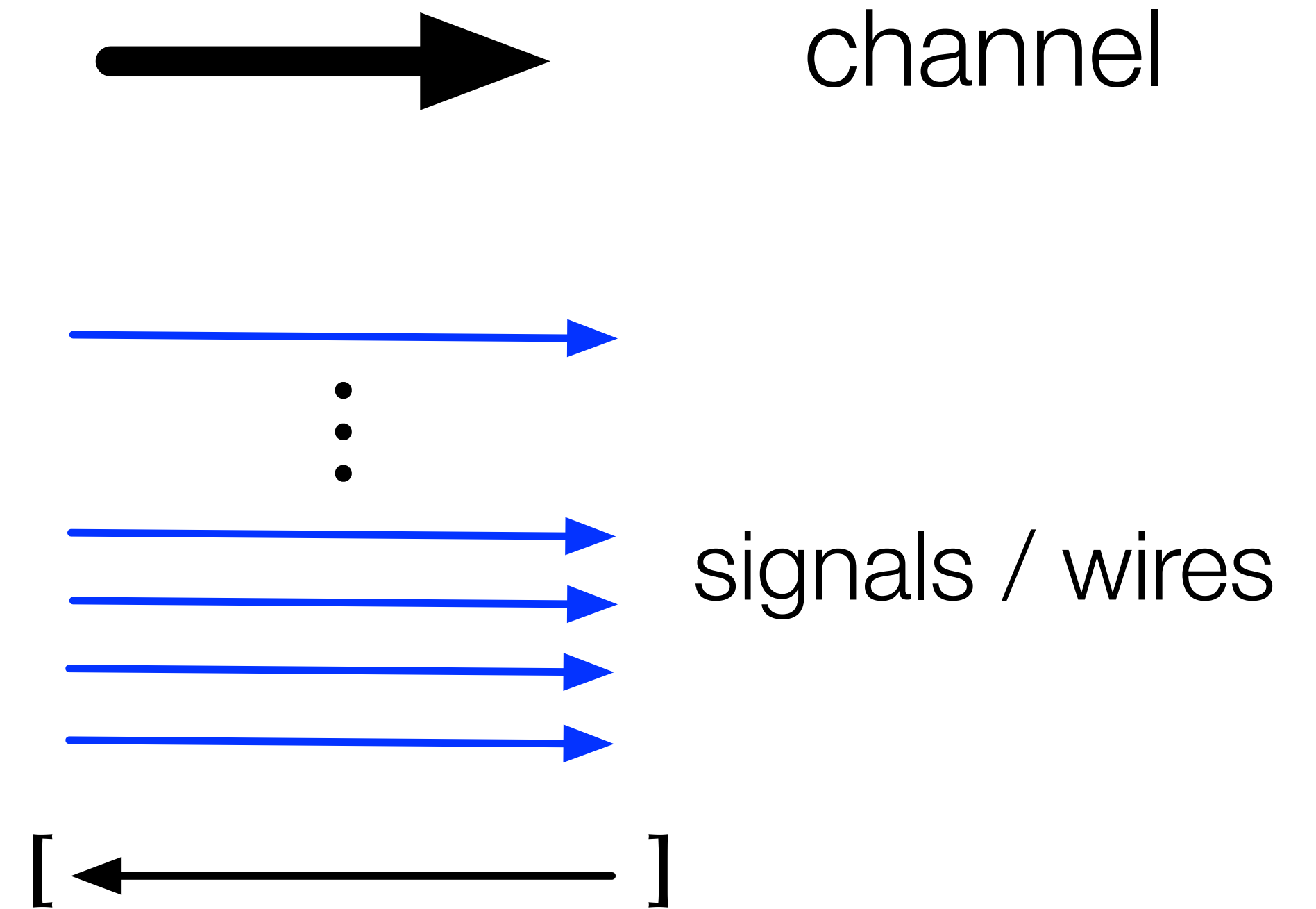- Channels can be implemented in a number of ways
 - ❖ Each channel requires a set of wires
 - ❖ Sender and receiver must follow a communication **protocol**





Dataless channels: two-phase protocol

  

- Two-phase protocol
 - ❖ Also called *transition signaling* protocol
 - ❖ Two wires to implement channel
 - ❖ Two signal changes (“phases”) in sequence
- One end of the channel **initiates** the communication
 - ❖ Called the “**active**” end of the channel (other end is **passive**)

*Either end of the channel
can initiate the communication!*



Dataless channels: four-phase protocol

  

- Four-phase protocol
 - ❖ Two wires to implement channel
 - ❖ Four signal changes (“phases”) in sequence
 - ❖ Sometimes called “return to zero” protocol
- One end of the channel **initiates** the communication
 - ❖ Called the “**active**” end of the channel (other end is **passive**)

*Either end of the channel
can initiate the communication!*



Dataless channels: single track protocol

  

- Two-phase protocol
 - ❖ One wire to implement channel
 - ❖ Two signal changes (“phases”) in sequence
- One end of the channel **initiates** the communication
 - ❖ Called the “**active**” end of the channel (other end is **passive**)



*Either end of the channel
can initiate the communication!*

  Encoding data: bundled data communication





- Protocol on request/acknowledge protocol can be **any** of the ones seen earlier!
 - ❖ Two wires (or one) for the control
 - ❖ N data wires for N-bit data communication
 - ❖ **Timing** requirement (“bundled data timing requirement”)

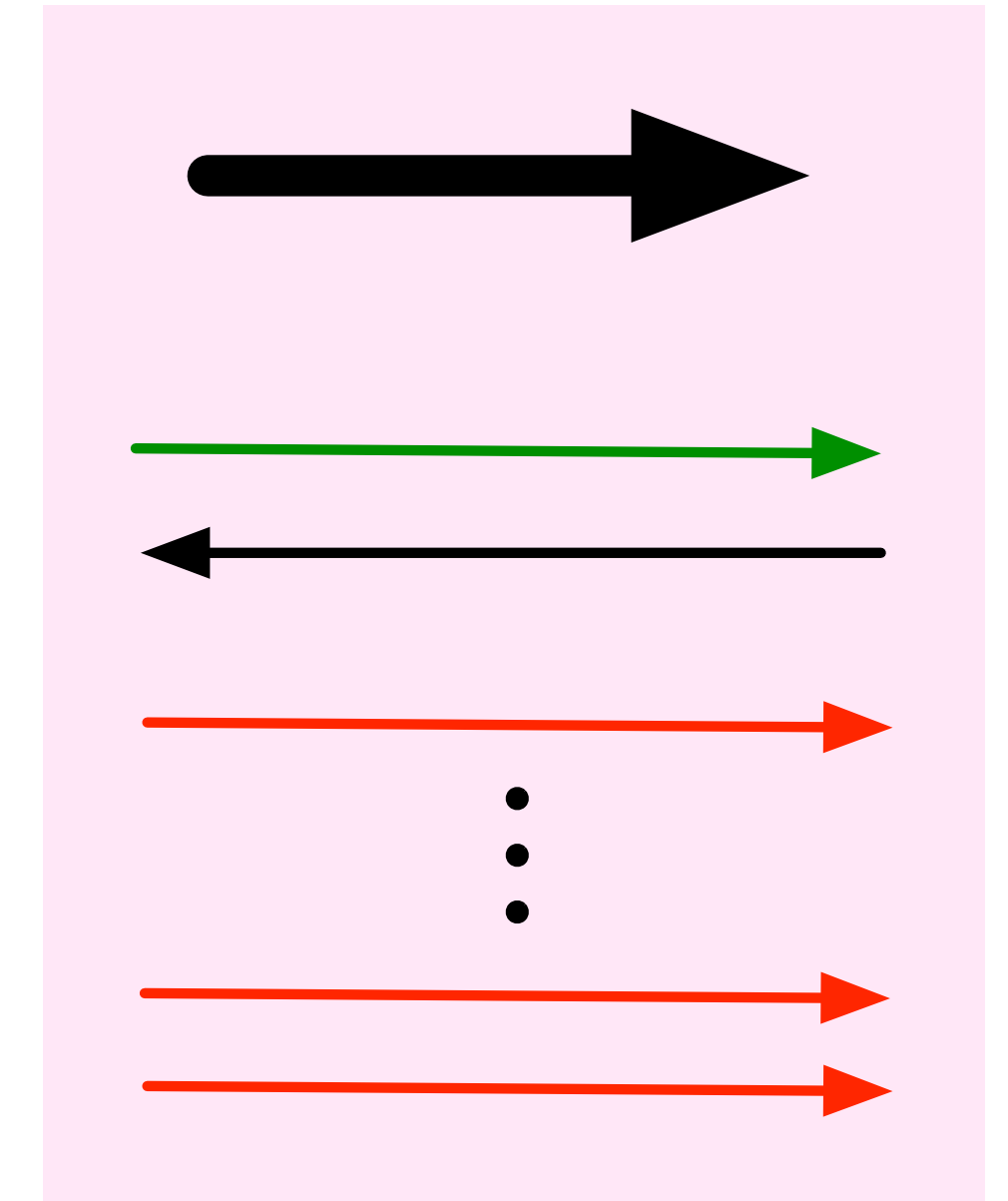 Encoding data: bundled data communication



- Protocol on request/acknowledge protocol can be **any** of the ones seen earlier!
 - ❖ Two wires (or one) for the control
 - ❖ N data wires for N-bit data communication
 - ❖ **Timing** requirement (“bundled data timing requirement”)

  Encoding data: delay-insensitive encoding



- Four-phase communication with dual-rail data encoding
 - ❖ Two wires for one bit
 - ❖ Four-phase handshake on (**data 0, acknowledge**) or (**data 1, acknowledge**)


Delay-insensitive encoding

- 1-of-N encoding
 - ❖ **N** wires to send **log(N)** bits of information
 - ❖ Common choices: N=2 or N=4
- k-of-N encoding
 - ❖ Maximum value occurs for $k = \text{floor}(N/2)$
 - ▶ Extra wires: $\sim O(\log(N))$
 - ▶ These are called Sperner codes
- Mix-and-match
 - ❖ N/2 copies of a 1-of-4 code (2N wires for N bits)


How do I know that data has arrived?

- 1-of-N encoding
 - ❖ **OR** gate
- k-of-N encoding
 - ❖ ... a bit more complicated!
- How do I check **all bits** have arrived?
 - ❖ Check each individual code
 - ❖ Combine checks using a **completion tree**



• Standard gate: **C-element**

 

a	b	x
0	0	0
0	1	hold state
1	0	hold state
1	1	1


 


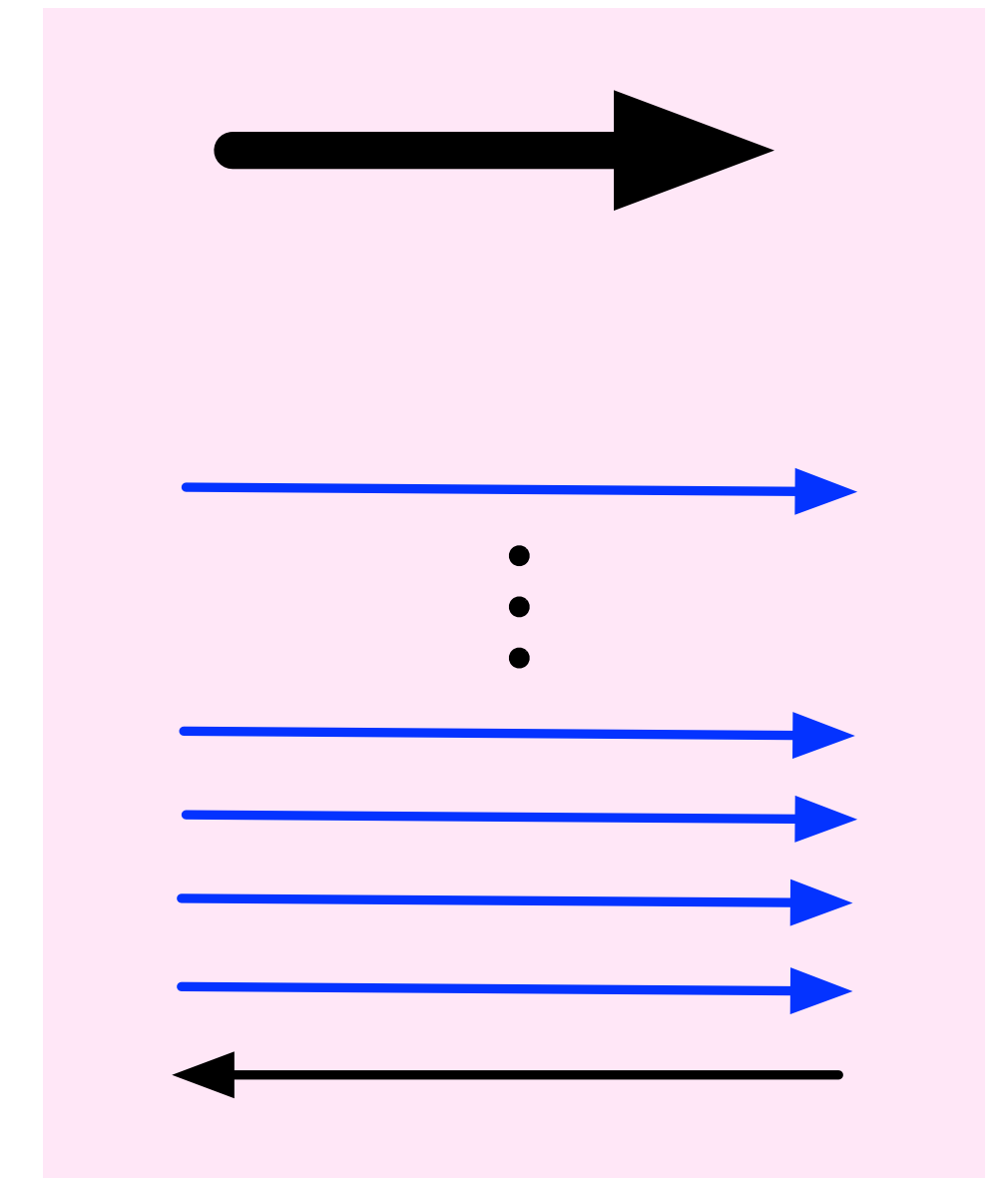 Multi-bit delay-insensitive communication



- In this example, the “request” is **embedded** in the data encoding
 - ❖ Data bits are valid is interpreted as a **phase** in the 2-phase/4-phase communication
 - ▶ Replaces request going high (or acknowledge going high), for example

  Encoding data: two-phase delay-insensitive encoding



- Two popular approaches
 - ❖ Toggle data wire to send the appropriate bit
 - ❖ Four-state encoding (popularly called level-encoded dual rail or LEDR)
 - ▶ One of the wires is the data bit
 - ▶ The second wire is toggled when next data bit is unchanged

Channels in ACT

- Example
 - ❖ Bundled-data four-phase channels
 - ❖ Defined in the ACT standard library

```
import std::channel;

/* This defines std::channel::bd<M>
   as an implementation of chan(int<M>)
*/
```

```
defproc alu(chan?(int<2>) cmd;
            chan?(int) X, Y; chan!(int) O)
{
  int x, y; // local state
  int<2> c;

  chp {
    *[ X?x, Y?y, cmd?c;
      [c=0 -> O!(x + y)
      [ ]c=1 -> O!(x - y)
      [ ]c=2 -> O!(x & y)
      [ ]c=3 -> O!(x | y)
    ]
  }
}
```