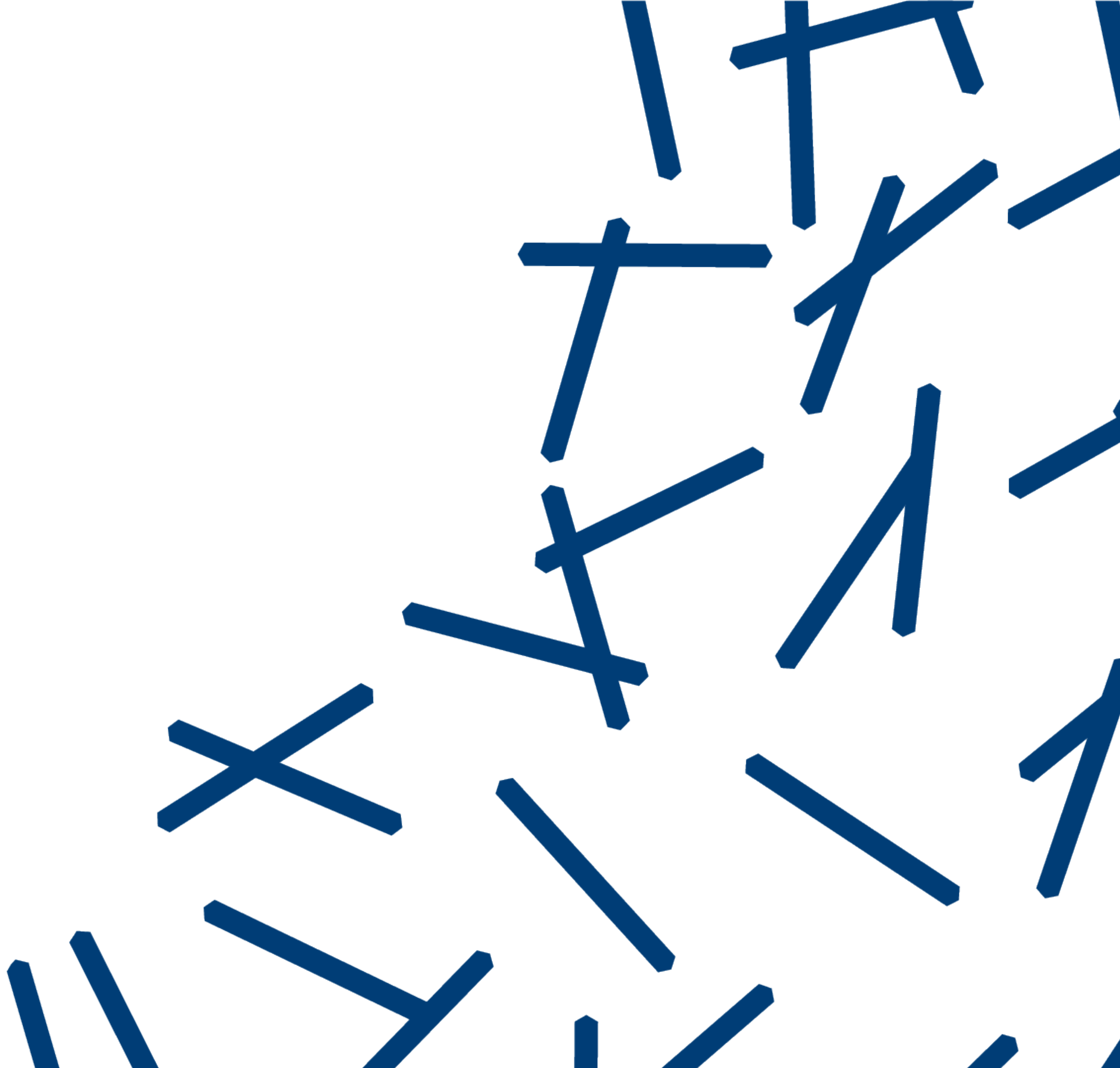


# Handshake protocols



# Message-passing abstraction

```
defproc buffer(chan?(int) L; chan!(int) R)
{
  int x; // local state

  chp {
    *[ L?x; R!x ]
  }
}
```

```
defproc gcd(chan?(int) X, Y; chan!(int) O)
{
  int x, y; // local state

  chp {
    *[ X?x, Y?y;
      *[ x > y -> x := x - y
        [] y > x -> y := y - x
      ];
      O!x
    ]
  }
}
```



```
defproc alu(chan?(int<2>) cmd;
           chan?(int) X, Y; chan!(int) O)
{
  int x, y; // local state
  int<2> c;

  chp {
    *[ X?x, Y?y, cmd?c;
      [c=0 -> O!(x + y)
        []c=1 -> O!(x - y)
        []c=2 -> O!(x & y)
        []c=3 -> O!(x | y)
      ]
    }
}
```

CHP = Communicating Hardware Processes
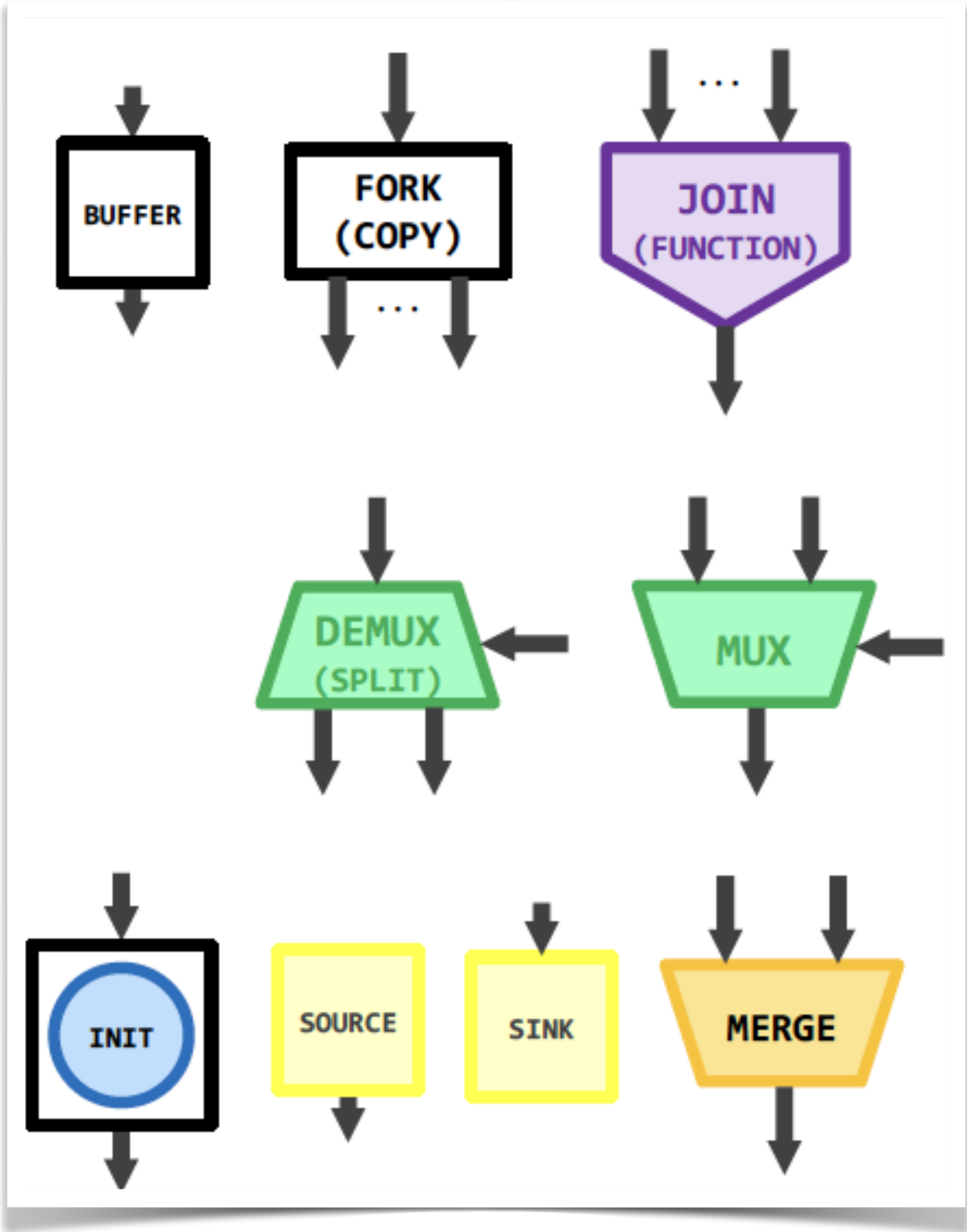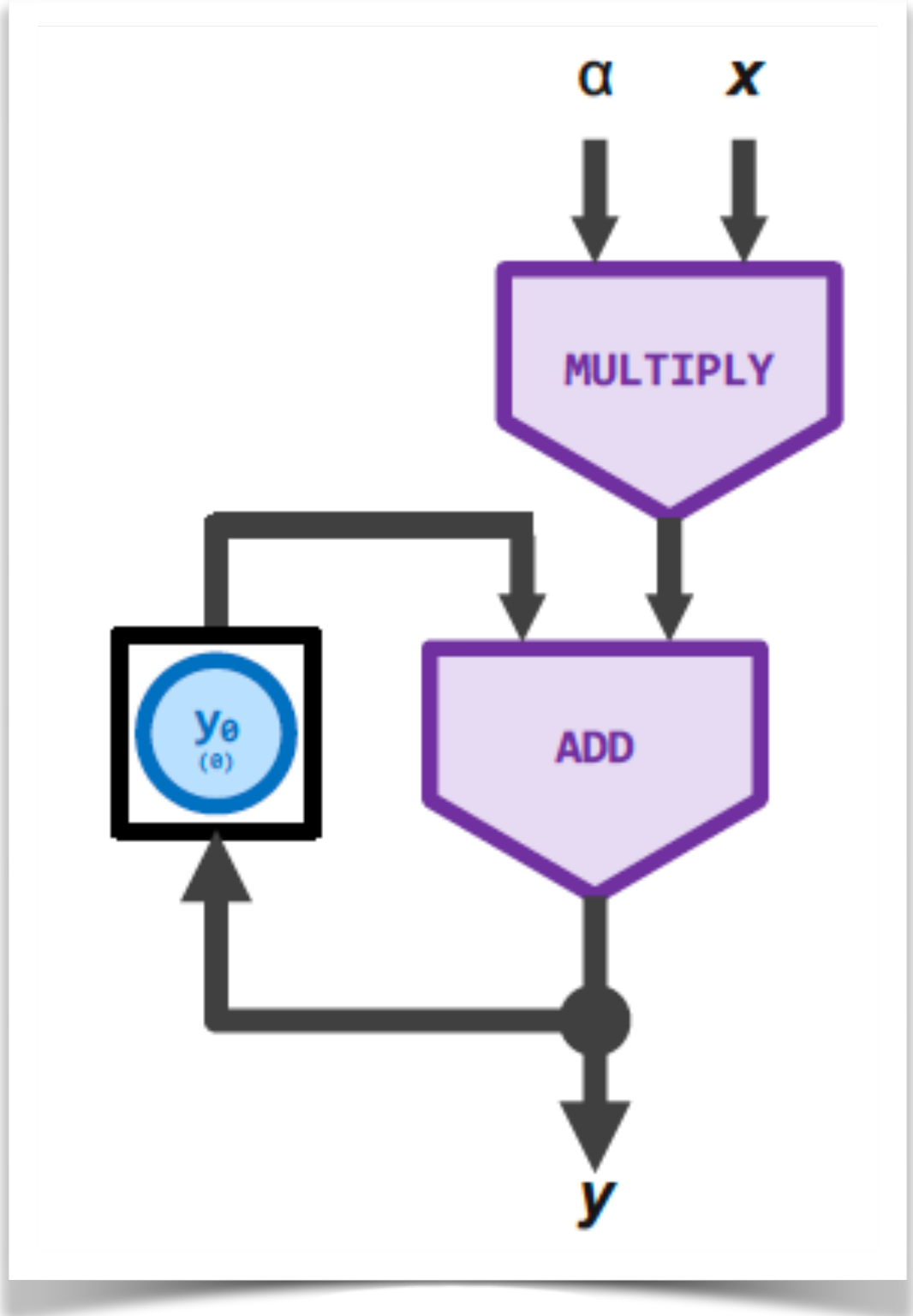
# Dataflow abstraction

- Dataflow model of computation
  - ▶ Tokens flowing through pipelines
  - ▶ Each component operates in parallel
- Each dataflow component can be written as a CHP program




# From message-passing to signals


- Variables
  - ❖ Integers can be implemented as an array of signals (`bool`)
- What about channels?

```
defproc alu(chan?(int<2>) cmd;  
           chan?(int) X, Y; chan!(int) O)  
{  
  int x, y; // local state  
  int<2> c;  
  
  chp {  
    *[ X?x, Y?y, cmd?c;  
      [c=0 -> O!(x + y)  
      [ ]c=1 -> O!(x - y)  
      [ ]c=2 -> O!(x & y)  
      [ ]c=3 -> O!(x | y)  
    ]  
  }  
}
```



# Channels

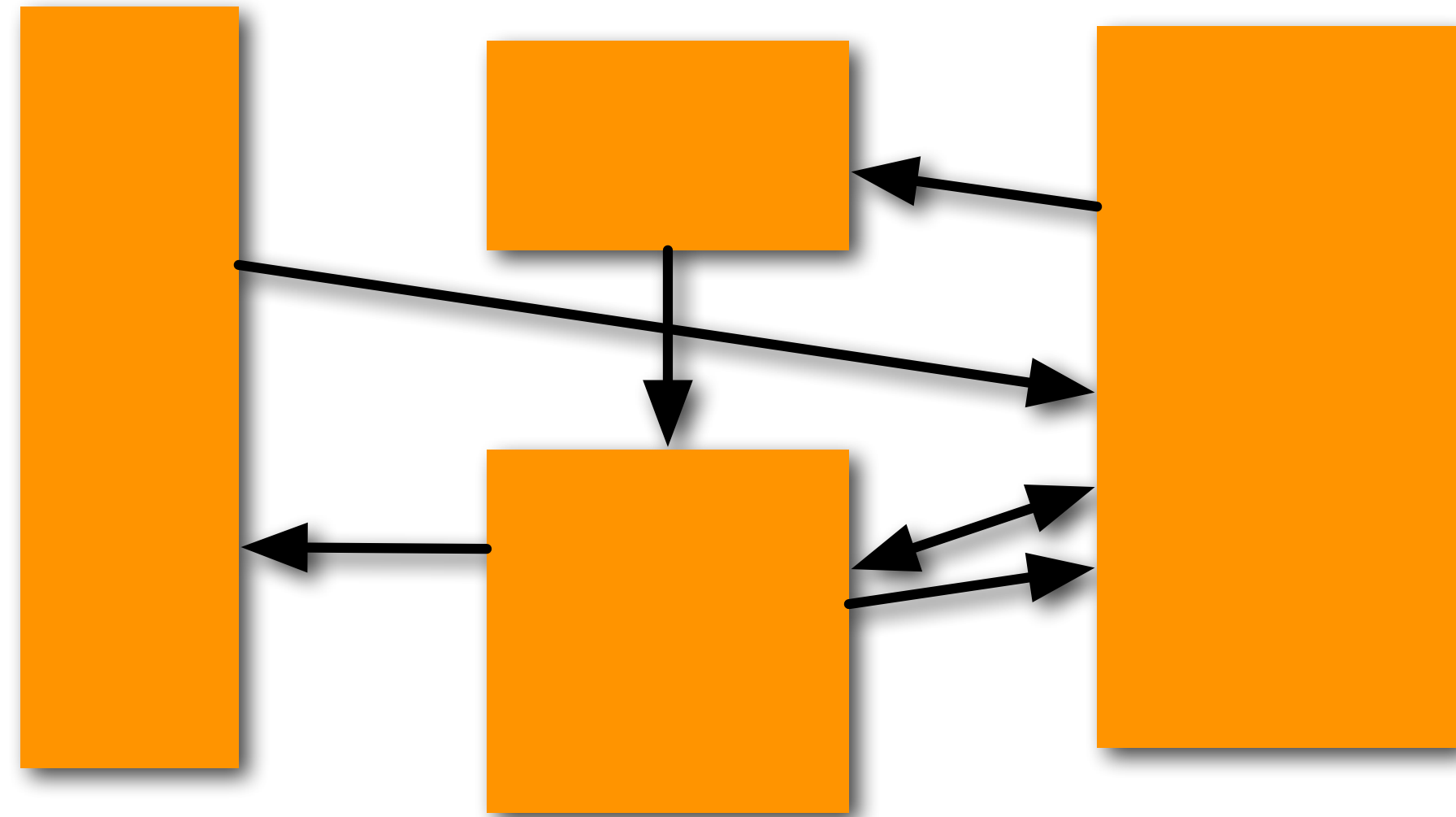

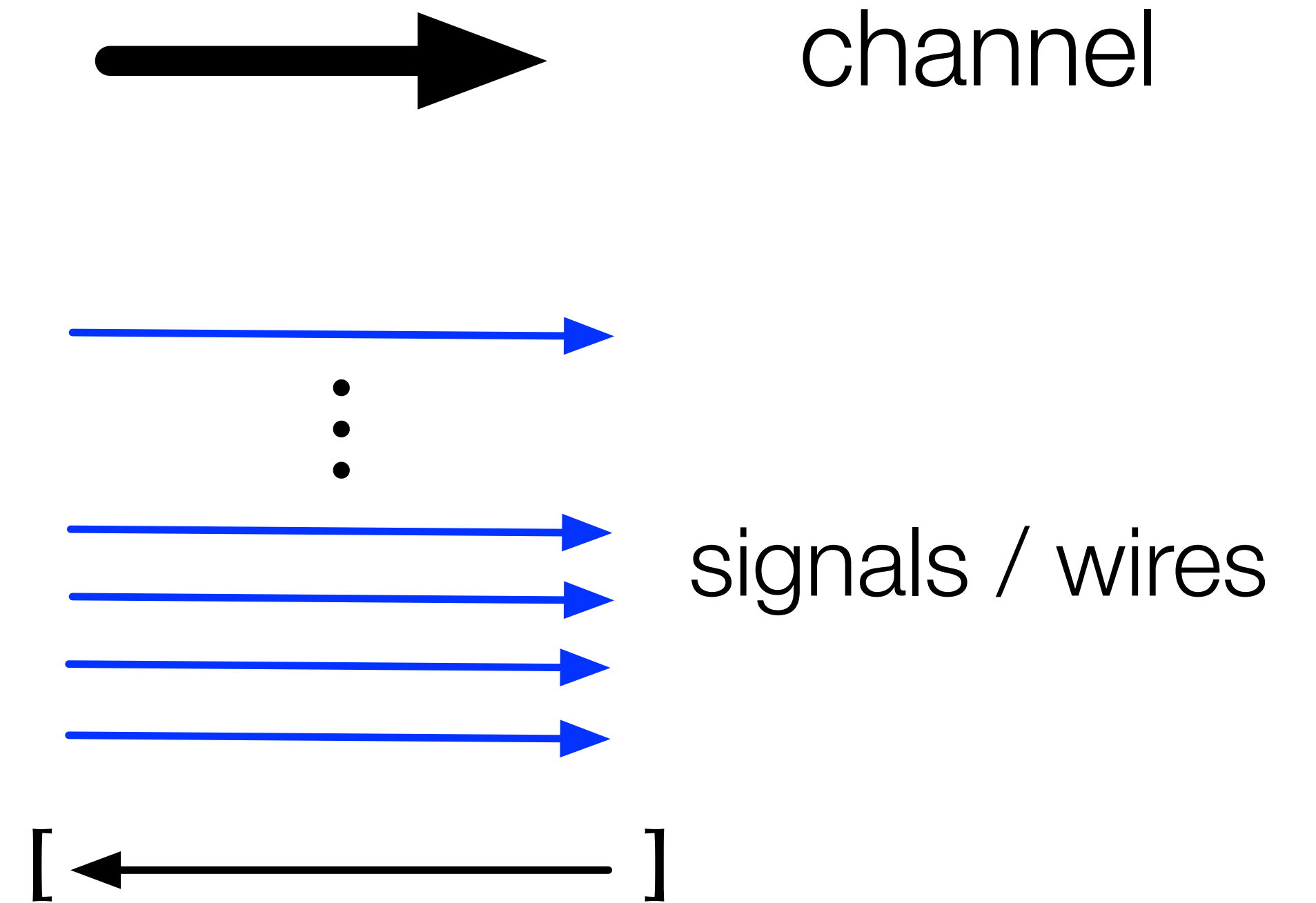- Channels can be implemented in a number of ways
  - ❖ Each channel requires a set of wires
  - ❖ Sender and receiver must follow a communication **protocol**





# Dataless channels: two-phase protocol

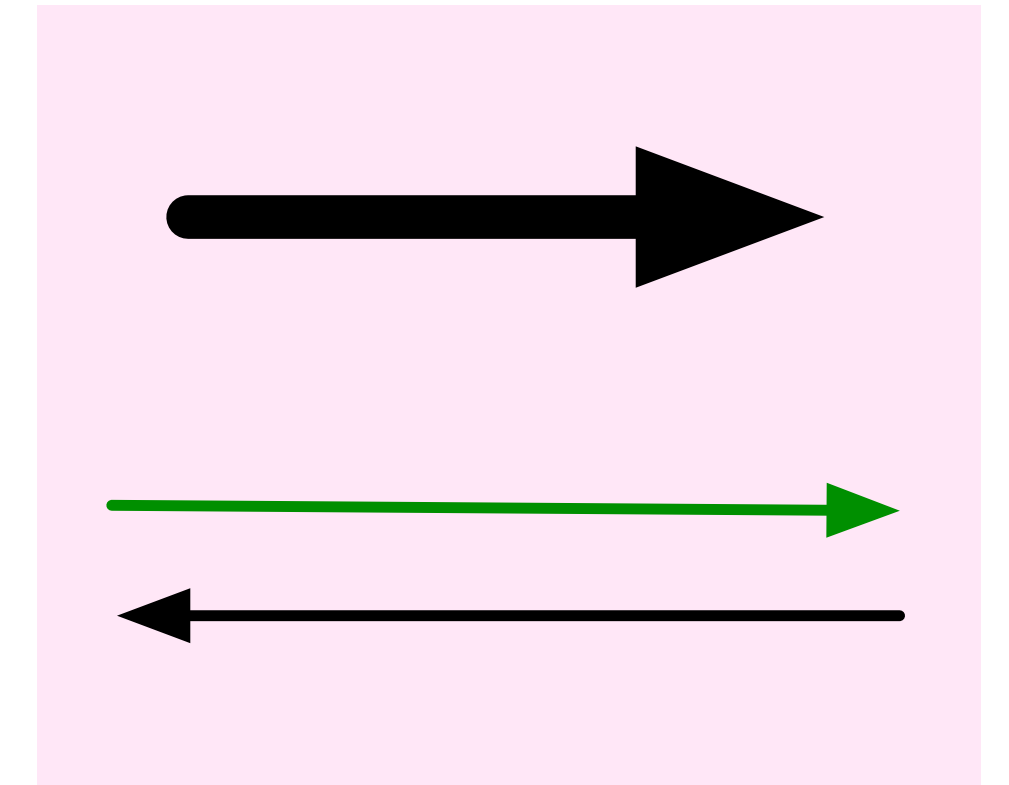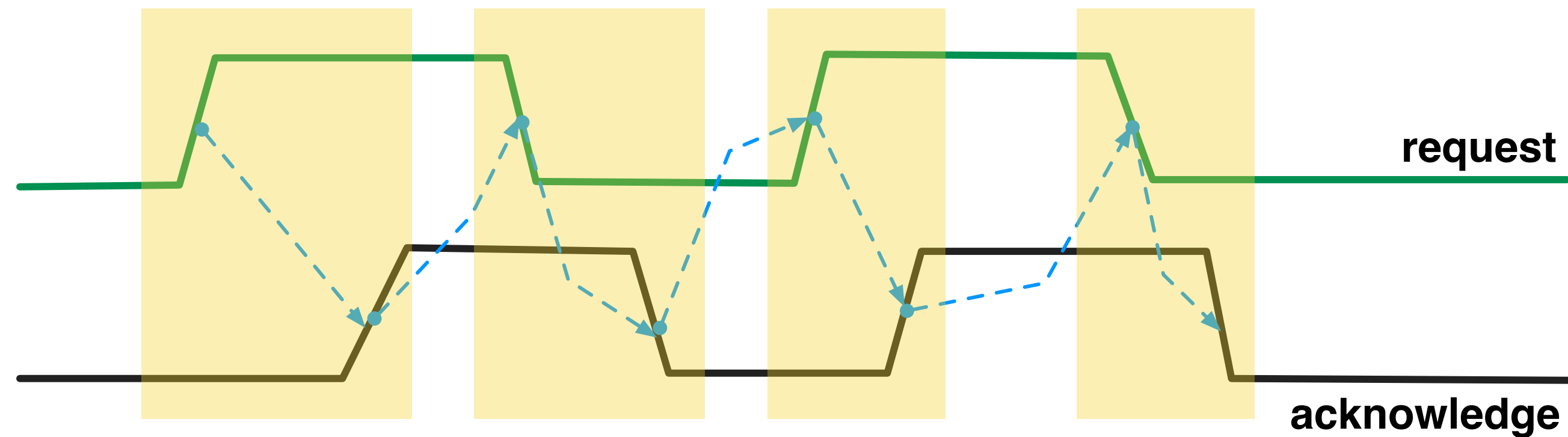

- Two-phase protocol
  - ❖ Also called *transition signaling* protocol
  - ❖ Two wires to implement channel
  - ❖ Two signal changes (“phases”) in sequence
- One end of the channel **initiates** the communication
  - ❖ Called the “**active**” end of the channel (other end is **passive**)

*Either end of the channel  
can initiate the communication!*

# Dataless channels: four-phase protocol

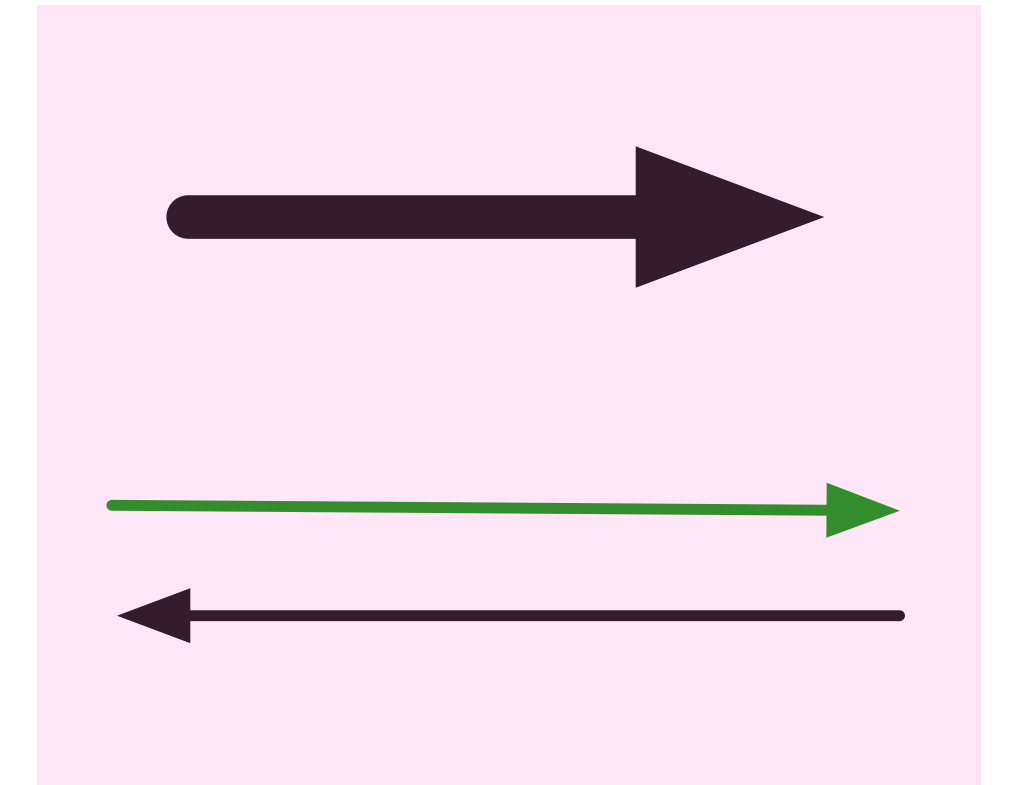
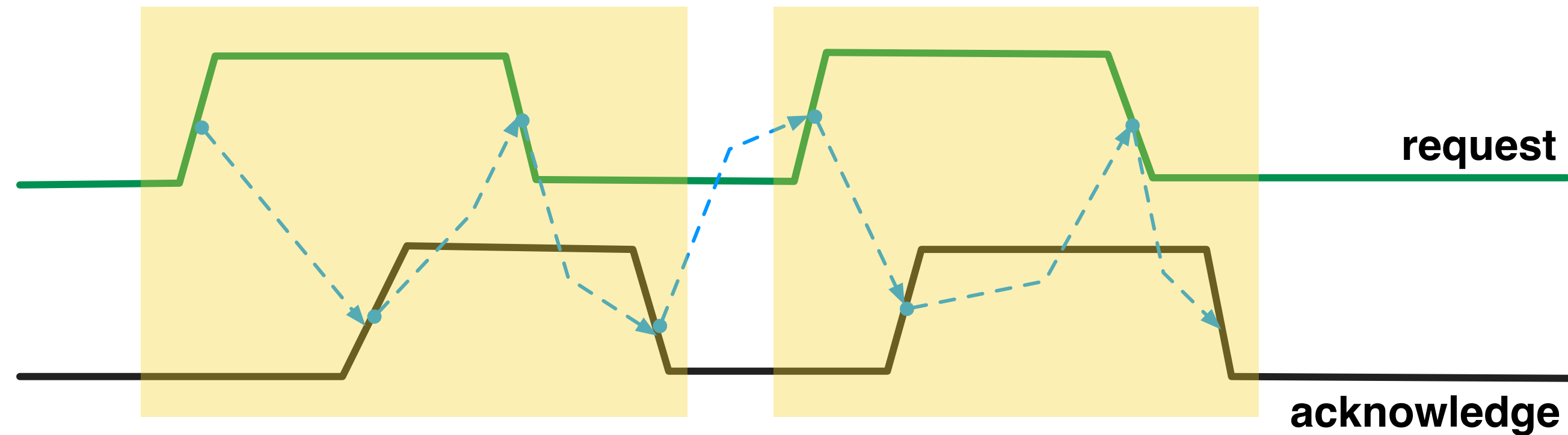


- Four-phase protocol
  - ❖ Two wires to implement channel
  - ❖ Four signal changes (“phases”) in sequence
  - ❖ Sometimes called “return to zero” protocol
- One end of the channel **initiates** the communication
  - ❖ Called the “**active**” end of the channel (other end is **passive**)

*Either end of the channel  
can initiate the communication!*

# Dataless channels: single track protocol



---

 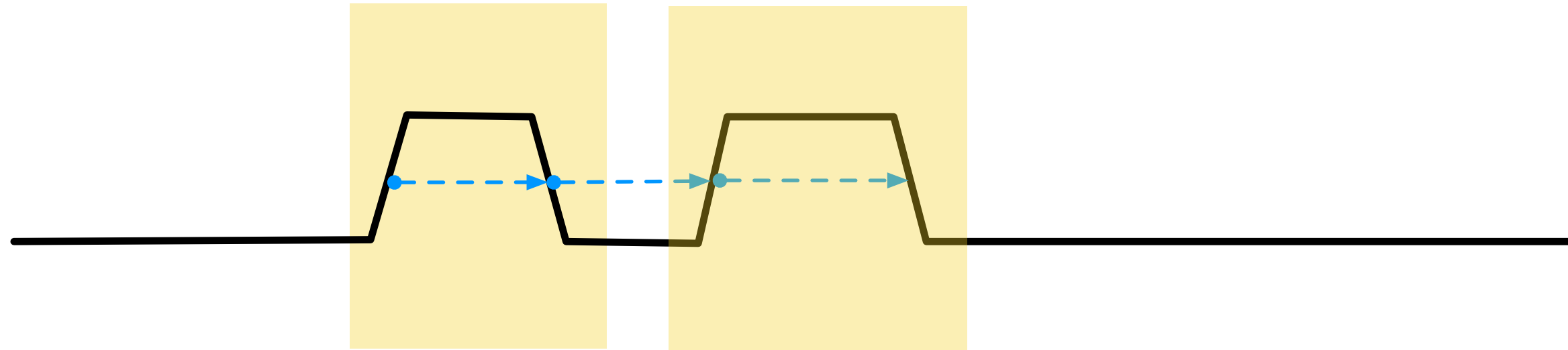

- Two-phase protocol
  - ❖ One wire to implement channel
  - ❖ Two signal changes (“phases”) in sequence
- One end of the channel **initiates** the communication
  - ❖ Called the “**active**” end of the channel (other end is **passive**)



*Either end of the channel  
can initiate the communication!*
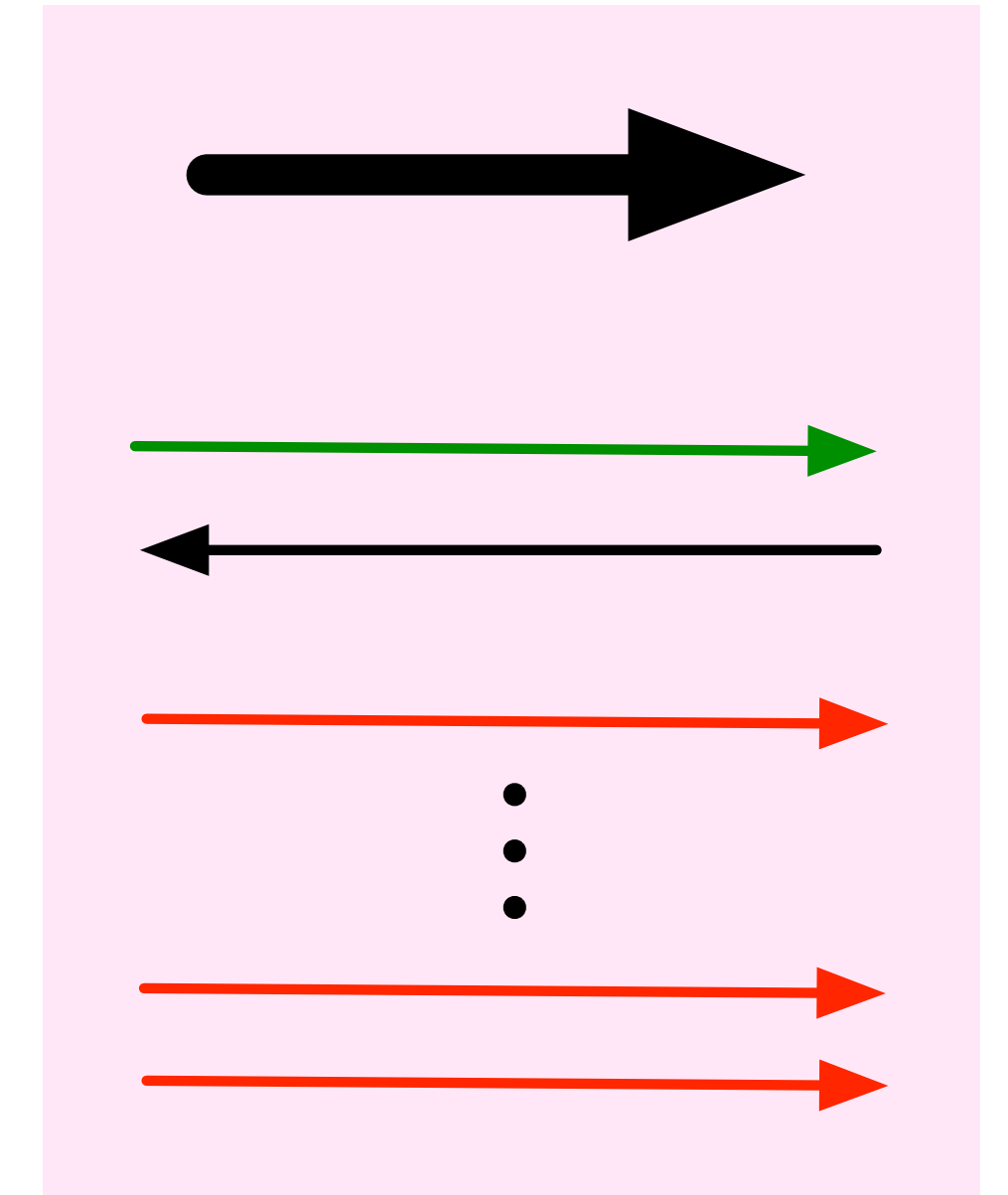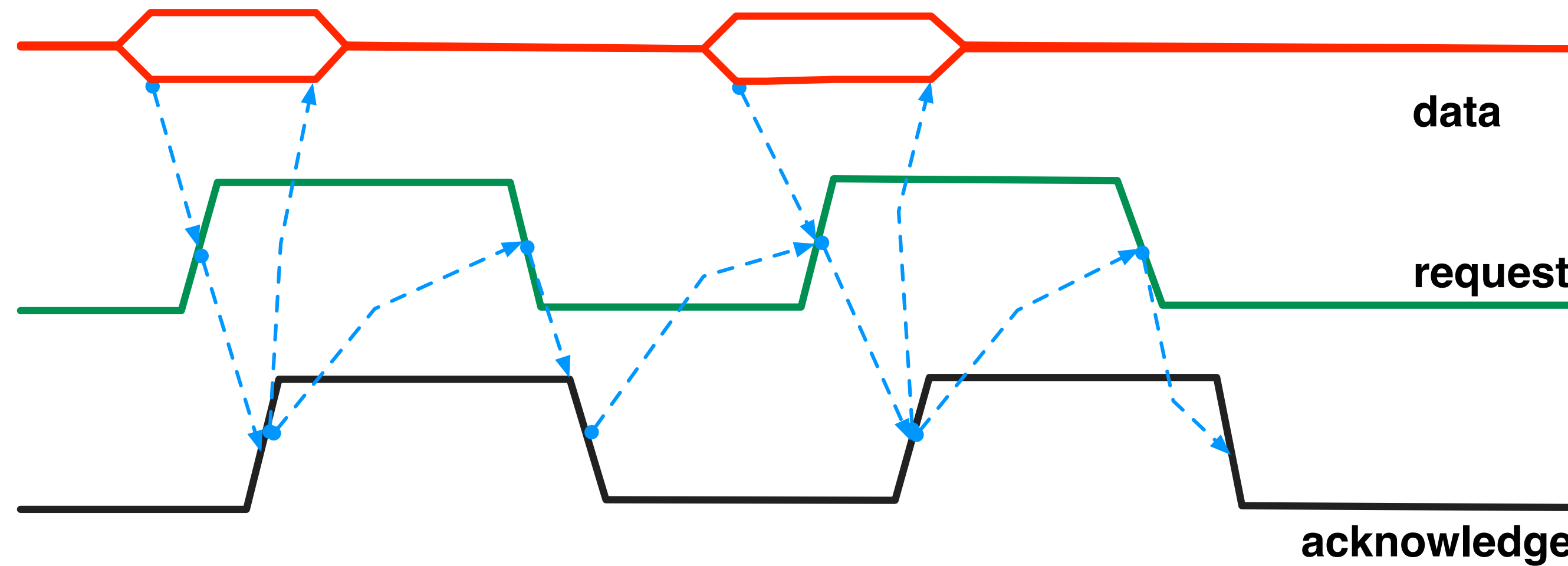
# Encoding data: bundled data communication





- Protocol on request/acknowledge protocol can be **any** of the ones seen earlier!
  - ❖ Two wires (or one) for the control
  - ❖ N data wires for N-bit data communication
  - ❖ **Timing** requirement (“bundled data timing requirement”)
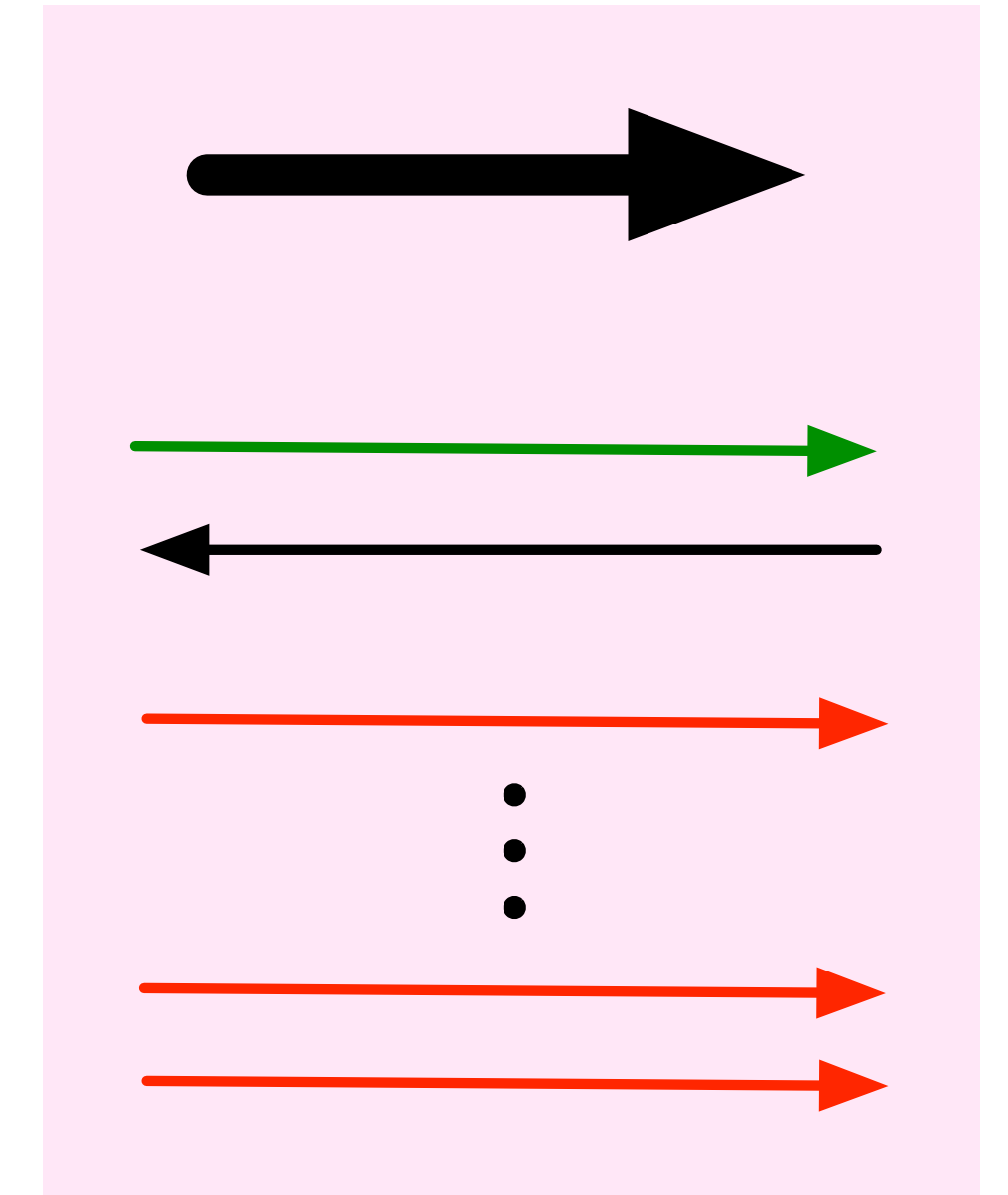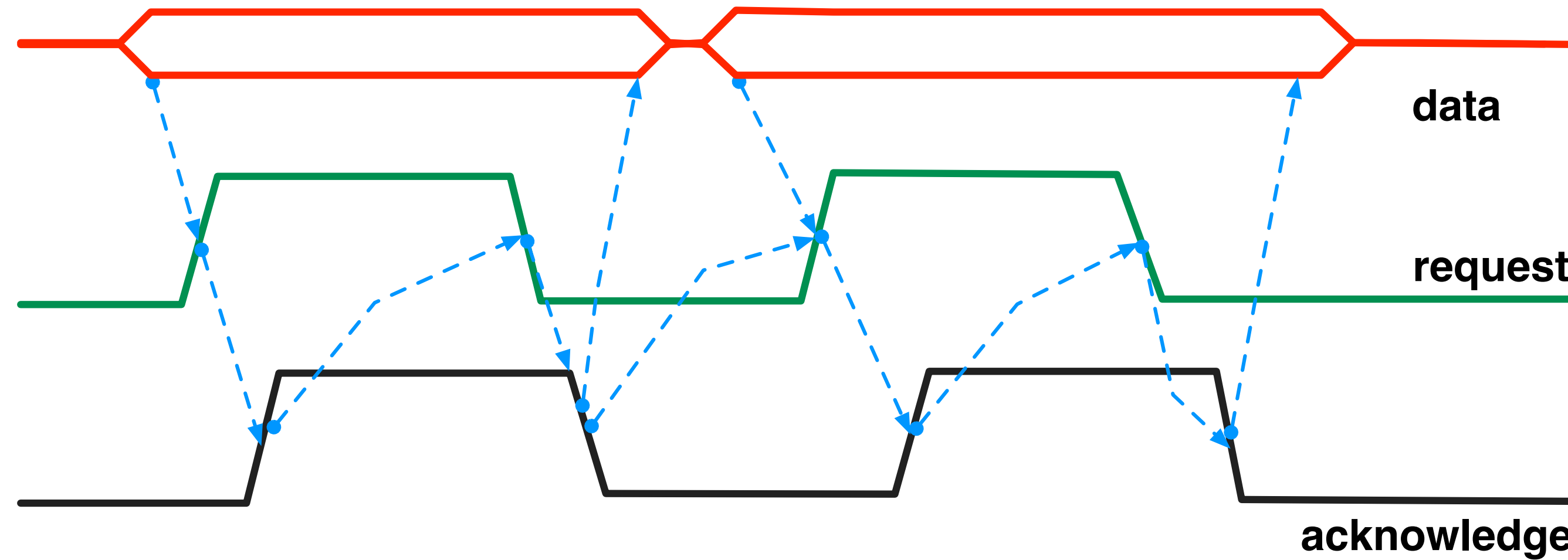
# Encoding data: bundled data communication



- Protocol on request/acknowledge protocol can be **any** of the ones seen earlier!
  - ❖ Two wires (or one) for the control
  - ❖ N data wires for N-bit data communication
  - ❖ **Timing** requirement (“bundled data timing requirement”)
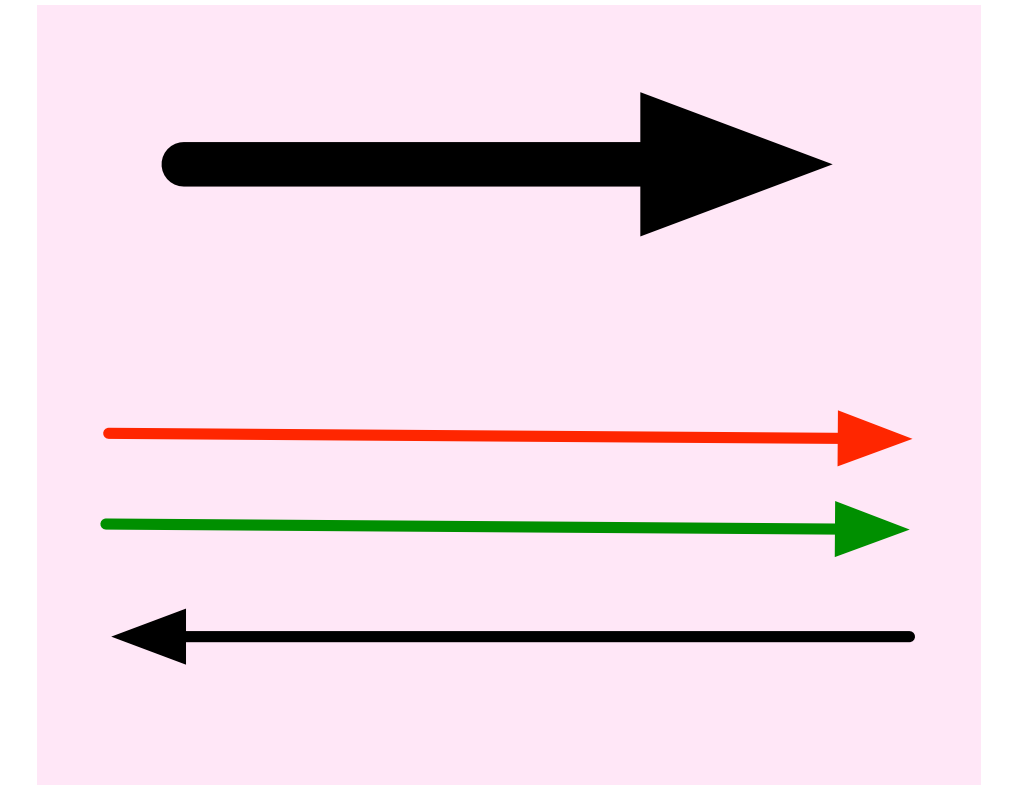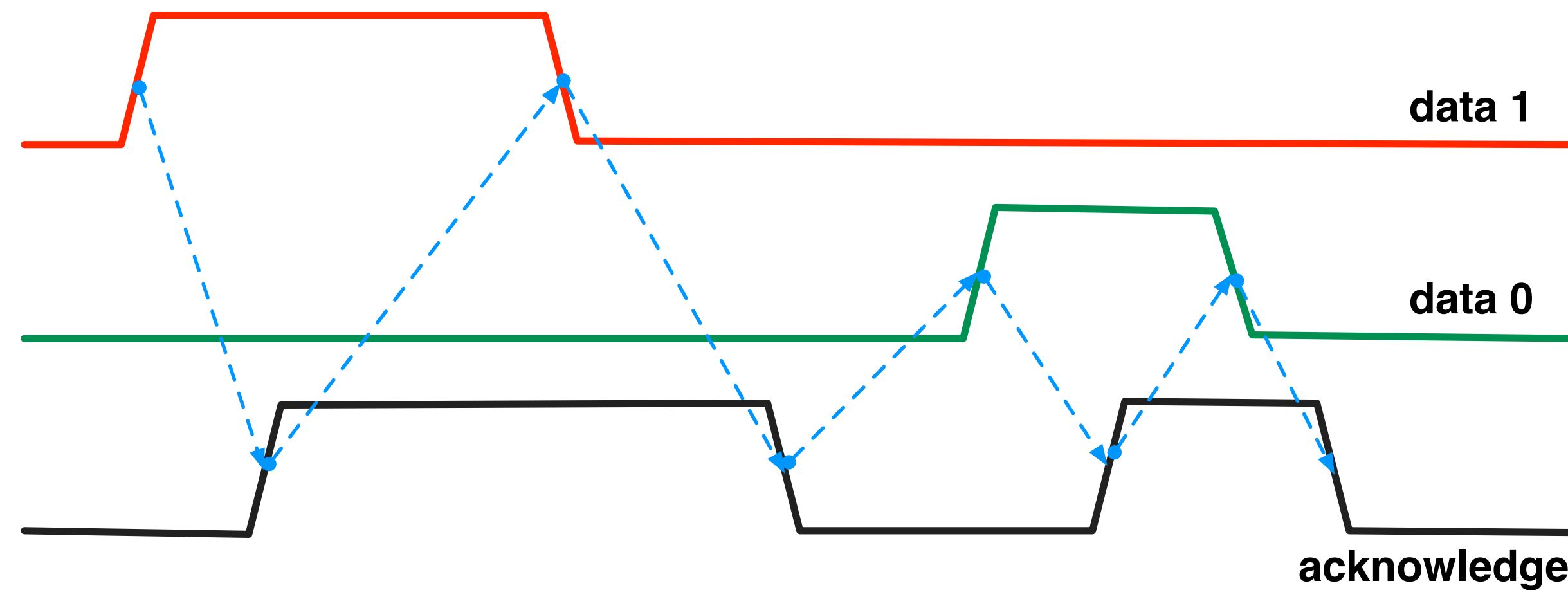
# Encoding data: delay-insensitive encoding



- Four-phase communication with dual-rail data encoding
  - ❖ Two wires for one bit
  - ❖ Four-phase handshake on (**data 0, acknowledge**) or (**data 1, acknowledge**)

# Delay-insensitive encoding


---

- 1-of-N encoding
  - ❖ **N** wires to send **log(N)** bits of information
  - ❖ Common choices: N=2 or N=4
- k-of-N encoding
  - ❖ Maximum value occurs for  $k = \text{floor}(N/2)$ 
    - ▶ Extra wires:  $\sim O(\log(N))$
    - ▶ These are called Sperner codes
- Mix-and-match
  - ❖ N/2 copies of a 1-of-4 code (2N wires for N bits)


# How do I know that data has arrived?

- 1-of-N encoding
  - ❖ **OR** gate
- k-of-N encoding
  - ❖ ... a bit more complicated!
- How do I check **all bits** have arrived?
  - ❖ Check each individual code
  - ❖ Combine checks using a **completion tree**



• Standard gate: **C-element**

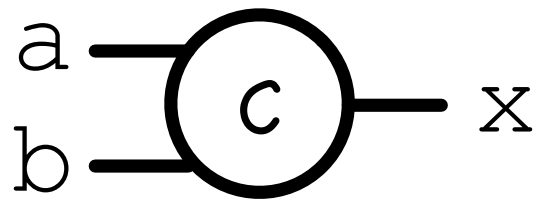

a	b	x
0	0	0
0	1	hold state
1	0	hold state
1	1	1


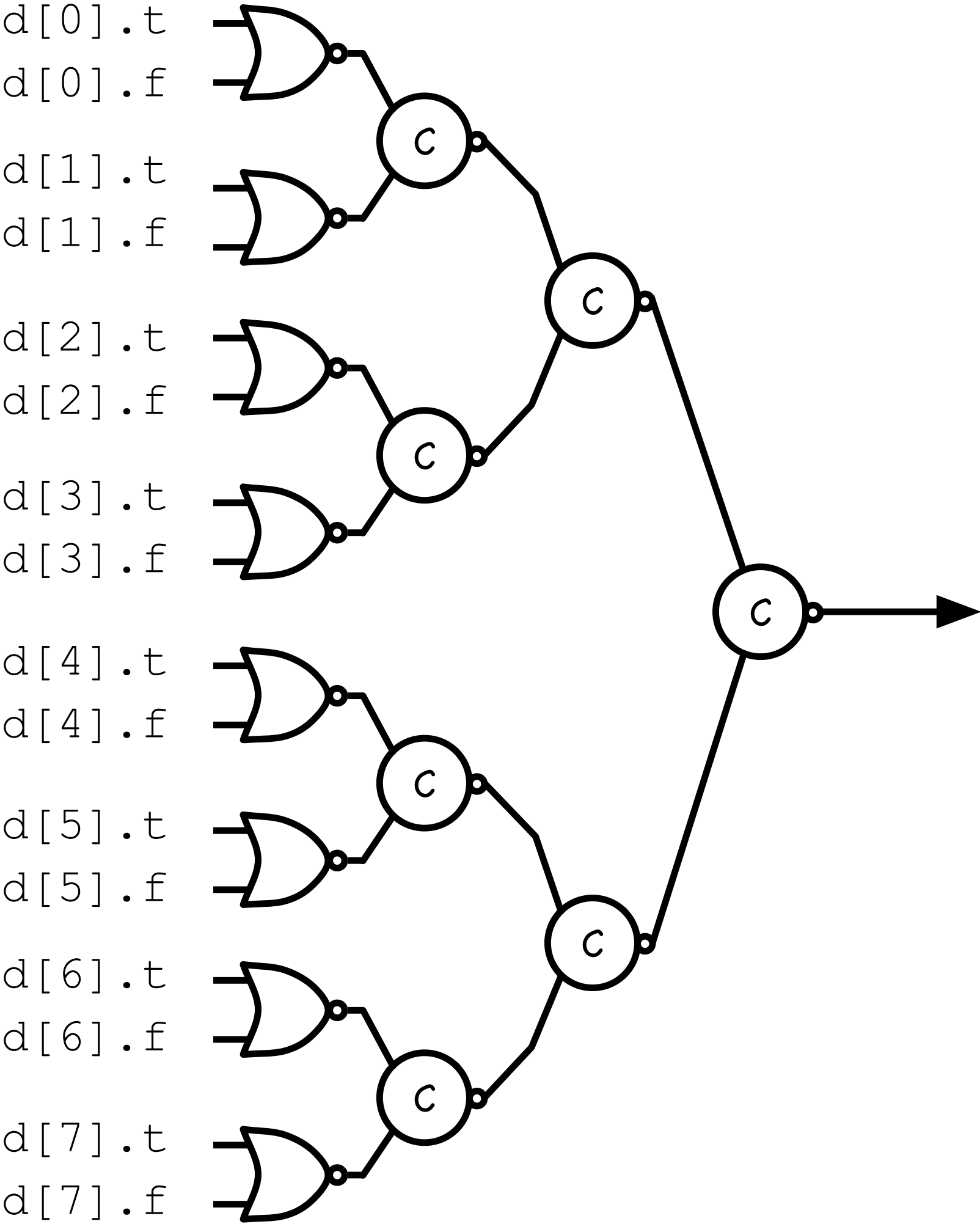

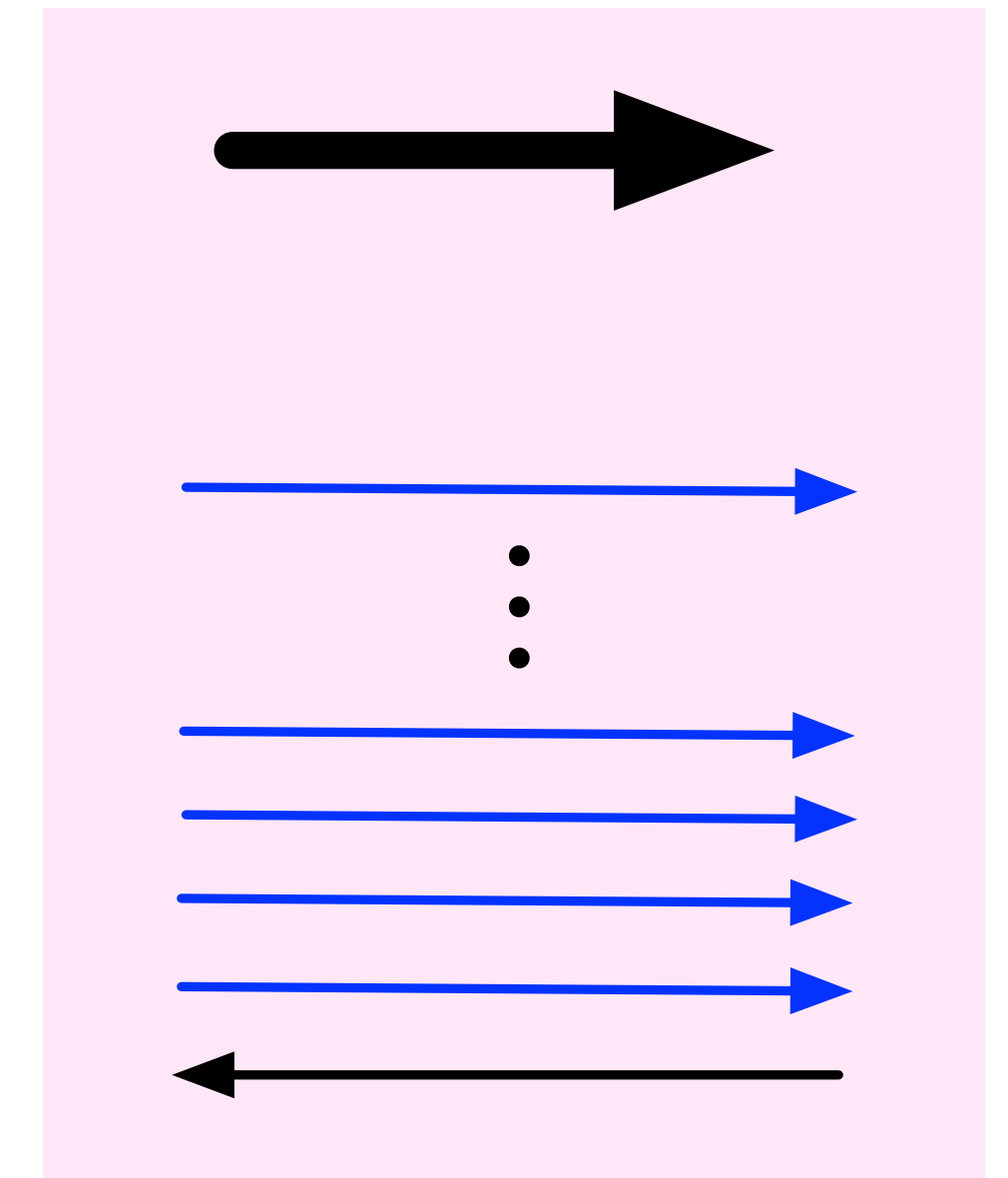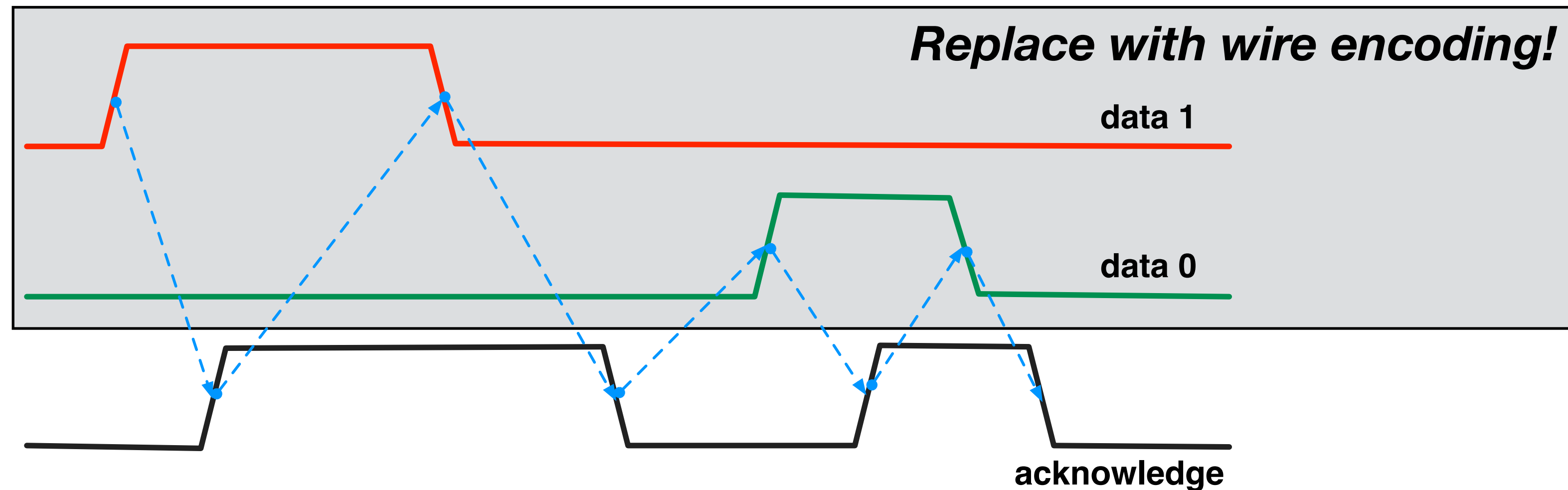
# Multi-bit delay-insensitive communication



- In this example, the “request” is **embedded** in the data encoding
  - ❖ Data bits are valid is interpreted as a **phase** in the 2-phase/4-phase communication
    - ▶ Replaces request going high (or acknowledge going high), for example
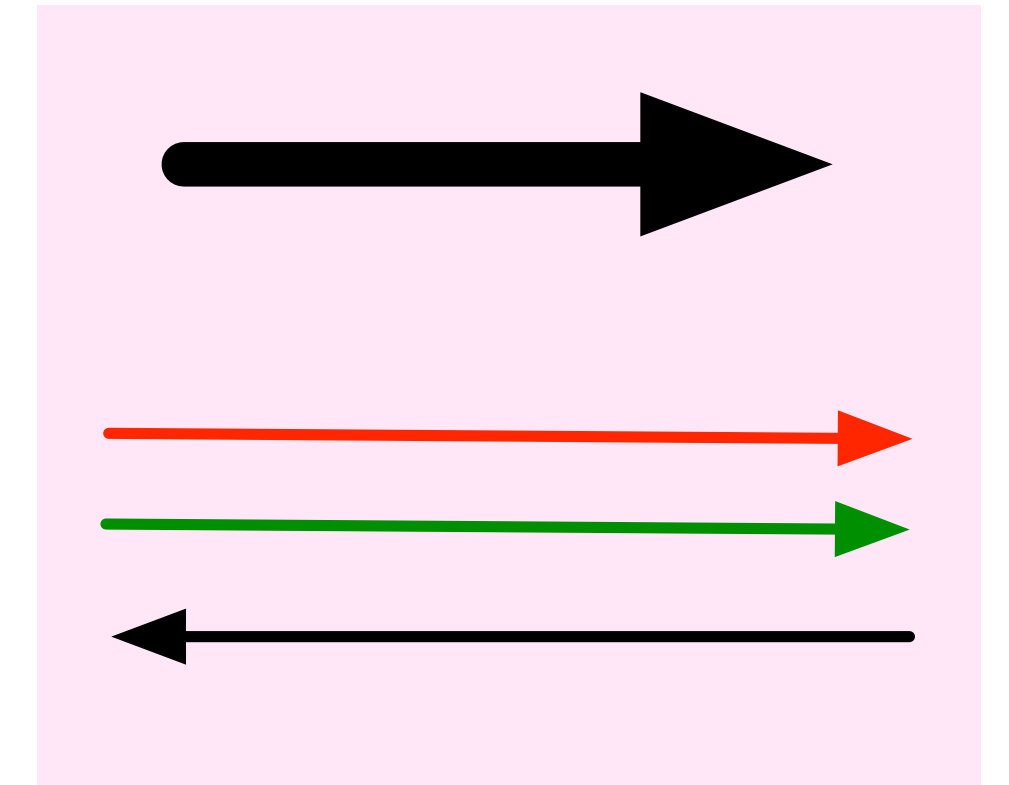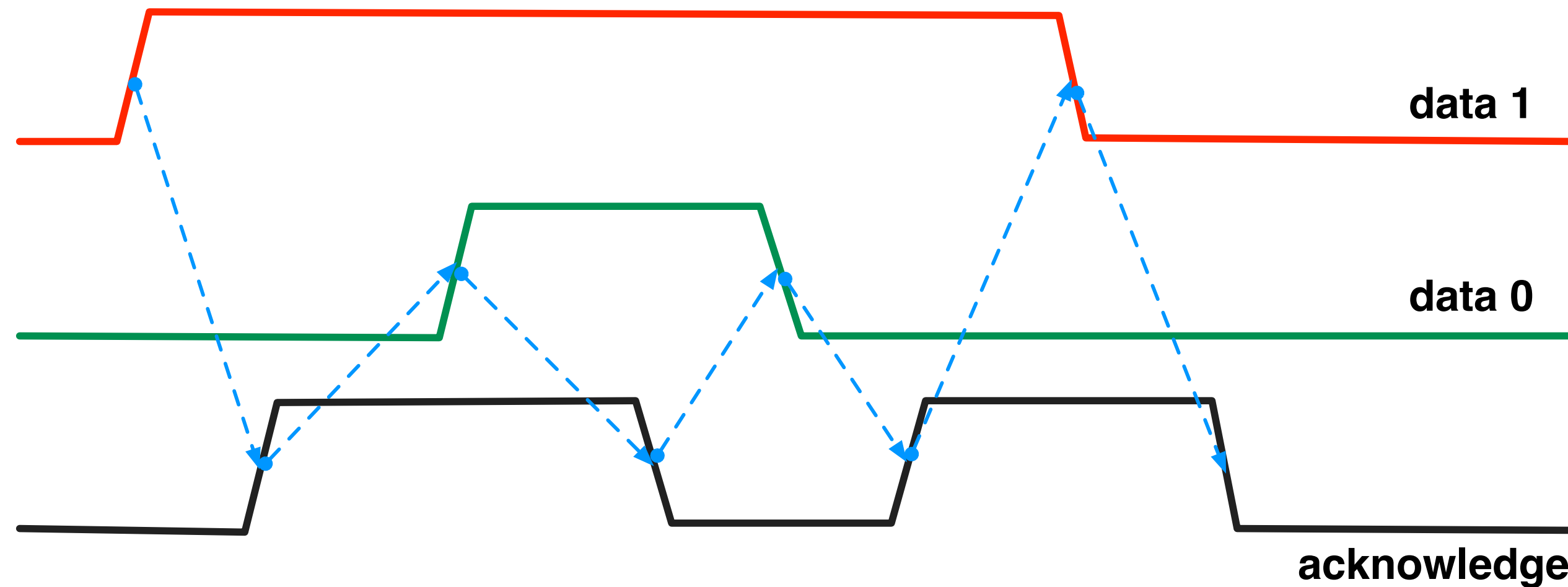
# Encoding data: two-phase delay-insensitive encoding



- Two popular approaches
  - ❖ Toggle data wire to send the appropriate bit
  - ❖ Four-state encoding (popularly called level-encoded dual rail or LEDR)
    - ▶ One of the wires is the data bit
    - ▶ The second wire is toggled when next data bit is unchanged

# Channels in ACT

- Example
  - ❖ Bundled-data four-phase channels
  - ❖ Defined in the ACT standard library

```
import std::channel;

/* This defines std::channel::bd<M>
   as an implementation of chan(int<M>)
*/
```

```
defproc alu(chan?(int<2>) cmd;
            chan?(int) X, Y; chan!(int) O)
{
  int x, y; // local state
  int<2> c;

  chp {
    *[ X?x, Y?y, cmd?c;
      [c=0 -> O!(x + y)
      [ ]c=1 -> O!(x - y)
      [ ]c=2 -> O!(x & y)
      [ ]c=3 -> O!(x | y)
    ]
  }
}
```