


# June 2 schedule

---



9:00 AM	Timing constraints	Rajit Manohar
9:30 AM	ASIC implementation flow I	Ole Richter
10:45 AM	Coffee break	
11:00 AM	ASIC implementation flow II	Rajit Manohar
12:10 PM	Lunch break	
1:10 PM	Petri net primer	Alex Yakovlev
2:00 PM	Controller design using Petri nets	Alex Yakovlev
3:00 PM	Coffee break	
3:30 PM	Custom circuit implementation	Rajit Manohar
 
# Timing

Rajit Manohar  
Computer Systems Lab  
Yale University


  
# Encoding data: bundled data communication



- Protocol on request/acknowledge protocol can be **any** of the ones seen earlier!
  - ❖ Two wires (or one) for the control
  - ❖ N data wires for N-bit data communication
  - ❖ **Timing** requirement (“bundled data timing requirement”)

# Why different circuit families?

---

DI control + datapath  
*No timing constraints!*

QDI control + datapath  
*Minimal timing constraints, robust operation*


QDI control + bundled-data datapath  
*Only bundled-data timing constraint*

Click elements  
*Repurpose clocked standard-cell library, flip-flop based*


GasP pipeline  
*high-speed pipeline, single track handshake*

MOUSETRAP pipeline  
*high-speed pipeline*

# Static timing analysis with cycles

 

Circuit

 

RER system

$$\langle x \uparrow, 0 \rangle \xrightarrow{2} \langle y \downarrow, 0 \rangle \xrightarrow{2} \langle z \uparrow, 0 \rangle \xrightarrow{2} \langle x \downarrow, 0 \rangle \xrightarrow{2} \langle y \uparrow, 0 \rangle \xrightarrow{2} \langle z \downarrow, 0 \rangle \xrightarrow{2} \langle x \uparrow, 1 \rangle \dots$$

- The **timing simulation** captures when events occur

$$\hat{t}(e) = \max\{\hat{t}(f) + \alpha \mid (f, e, \alpha) \in R\}$$

- “R” captures dependencies (“rules” or timing arcs)

# What can we say about timing?

- Theoretical result: there is an  $M$  such that for all  $i \geq N$

$$\hat{t}(x, i + M) - \hat{t}(x, i) = Mp^*$$

*critical cycle ratio*


- How do we calculate delays?

- ❖ Standard “non-linear delay model”

- ▶ delay is a function of (load, input slew)
- ▶ output slew is a function of (load, input slew)


- ❖ What is the slew rate?

*unfolding factor*

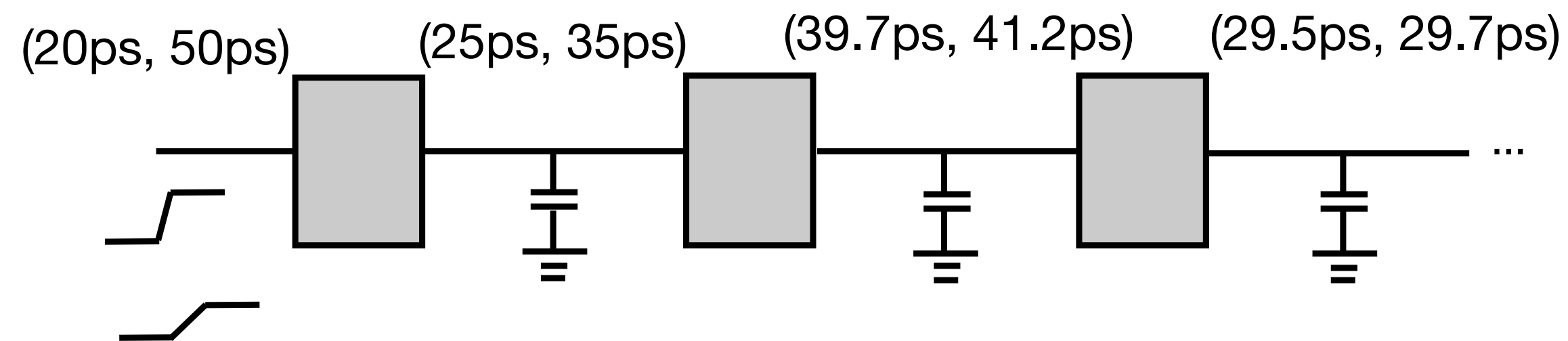

- ❖ Empirically, 3-4 stages suffices for convergence

# Timing constraints in ACT

 

- **maximum** delay from A to C < **minimum** delay from A to B

```
spec {  
    timing a+ : c+ < b-  
}
```

```
spec {  
    timing a+ : c+ < [4] b-  
}
```

# Timing constraints in ACT

---

- Example: bundled-data channel

```
template< pint M>
defchan bd (bool d[M]; bool r, a)
{
  spec {
    /* timing fork */
    timing a- : d* < r*+
  }
  ...
}
```

*The standard channel definitions in `std::channel` include timing constraints, so those will be automatically included.*

***actsim* checks constraints during simulation.**

# Where do you get the timing for gates?

---

- Cell library
  - ❖ Covers all the gates needed for the design
    - ▶ NAND2X1, INVX4, NOR2X2, ... etc
  - ❖ Any digital circuit component is mapped to a collection of cells
  - ❖ Cells + wiring = gate level design
- Cell library can then be *characterized*
  - ❖ Delays from input to output
    - ▶ ... under different operating conditions
    - ▶ ... under different loads
    - ▶ ... under different input conditions
  - ❖ ".lib" file