

**Jens Sparsø**


# **Dataflow Design**

**ASYNC 2026 Summer School  
June 1-2, 2026 @ DTU**

# Dataflow graphs and Dataflow computation

- Structural method of describing computations by specifying functions and their sequence of operations together graphically
- Intuitive way to convey design intent. Similar to an RTL-schematic
- Not necessarily asynchronous, though async has some nice advantages as a natural mapping of dataflow graphs
- Internal representation used in high-level synthesis tools.  
Source code -> data-flow graph representation -> optimizations/transformations -> circuit
- Jack Dennis, MIT (dataflow pioneer); *“I formed the Computation Structures Group [within CSAIL in 1963] and focused on architectural concepts that could narrow the acknowledged gap between programming concepts and the organization of computer hardware.”*
  - Related stuff: Single assignment code. Pure functional programming.  
Hardware parallelism. Self-timed circuits.
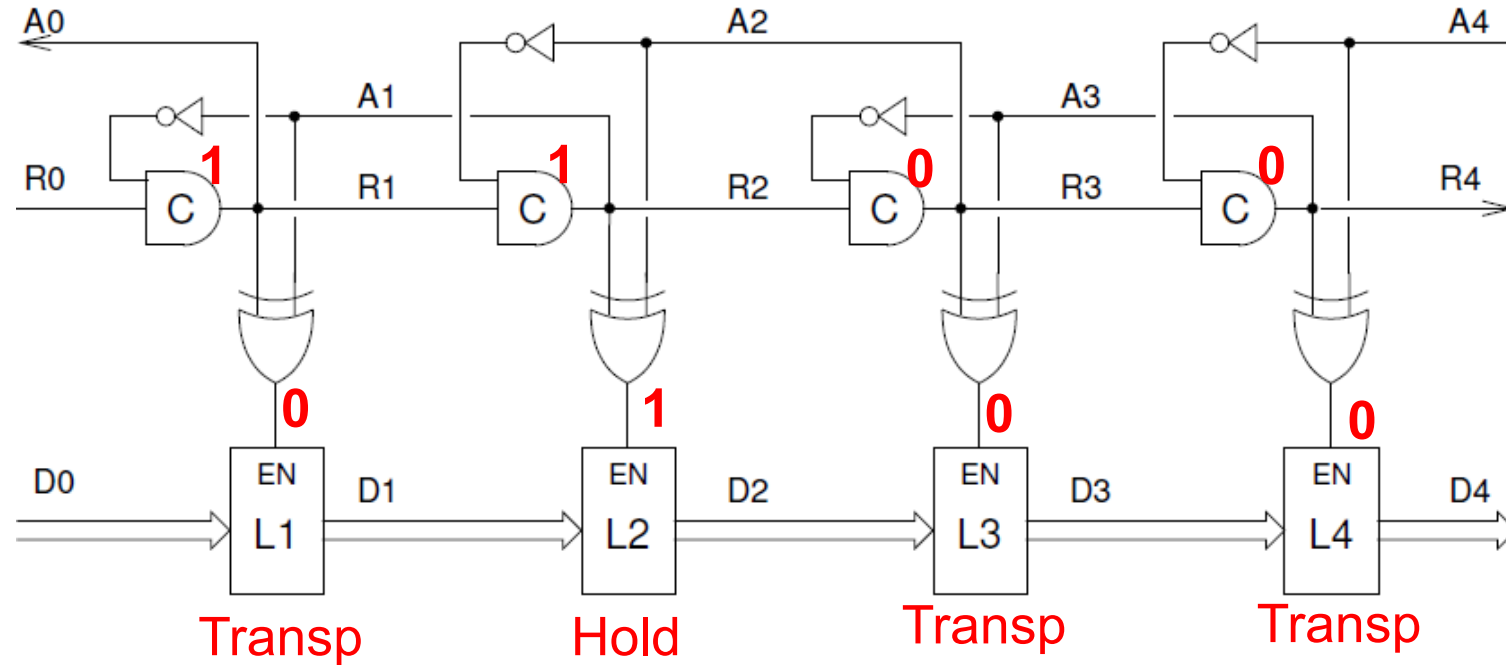
# Dataflow graphs and Data flow computation




- Snapshot of 2-phase bundled-data pipeline built from transparent latches controlled by a Muller pipeline.
- How do we understand, describe, and analyze its behavior? Timing diagram, hmm ☹️


I.E. Sutherland, "Micropipelines" Communications of the ACM 23(6), pp.720-738, 1989

# Dataflow (tokens and bubbles)


How?

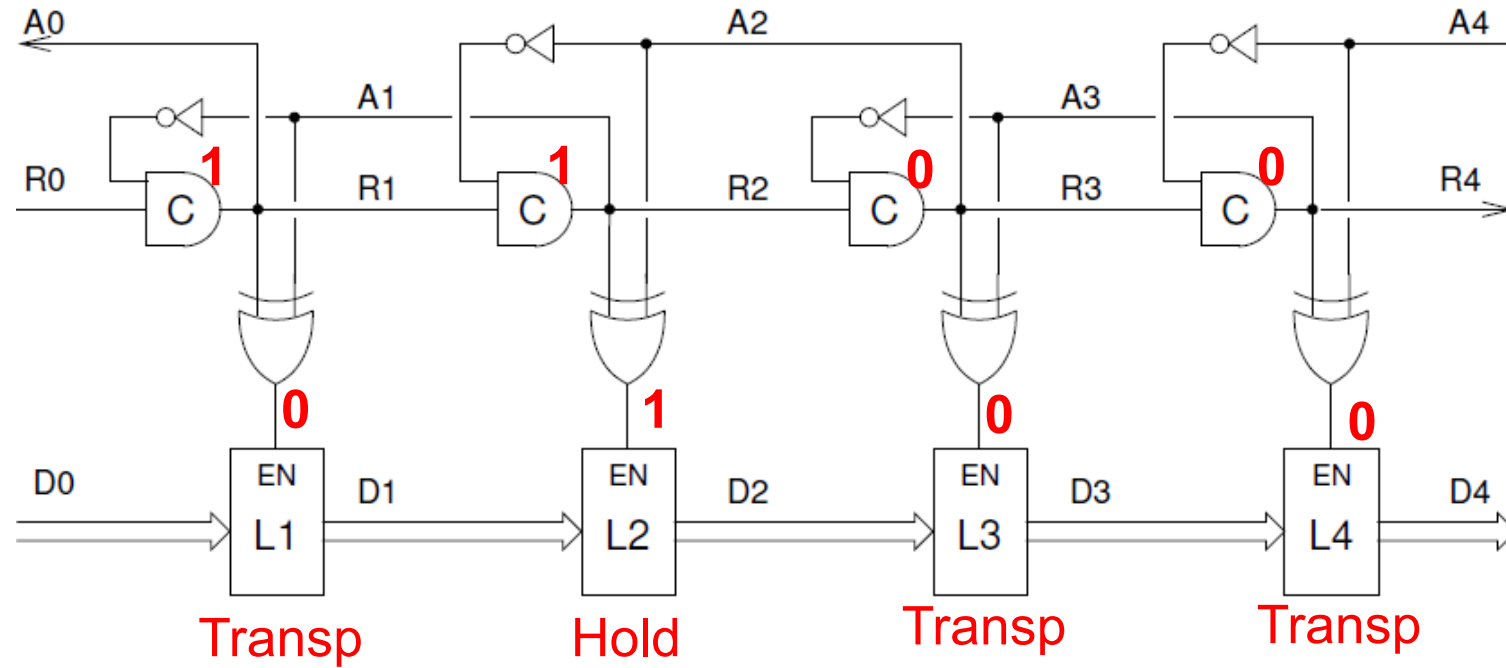


# Data-flow (tokens and bubbles)

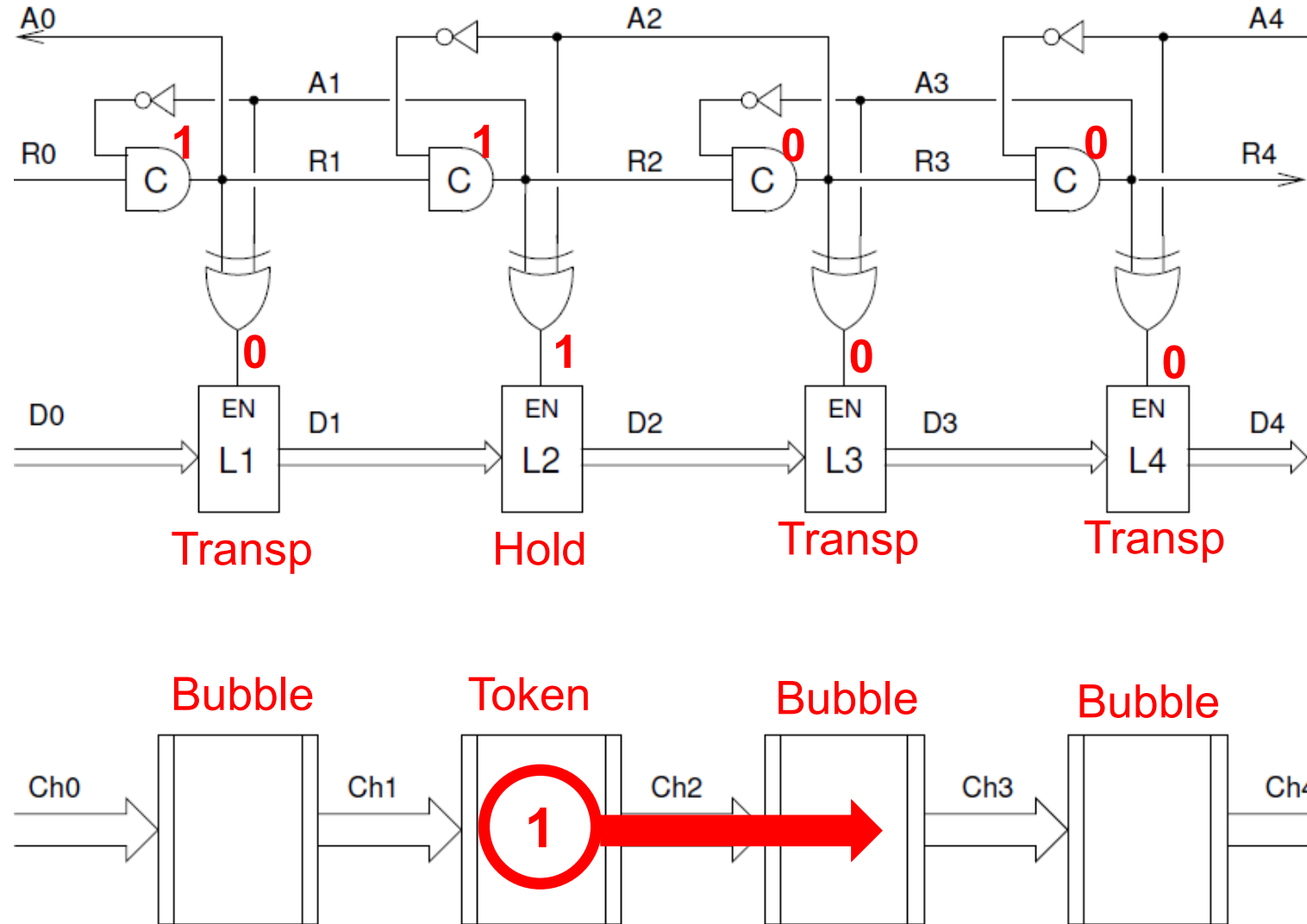

# Dataflow (tokens and bubbles)

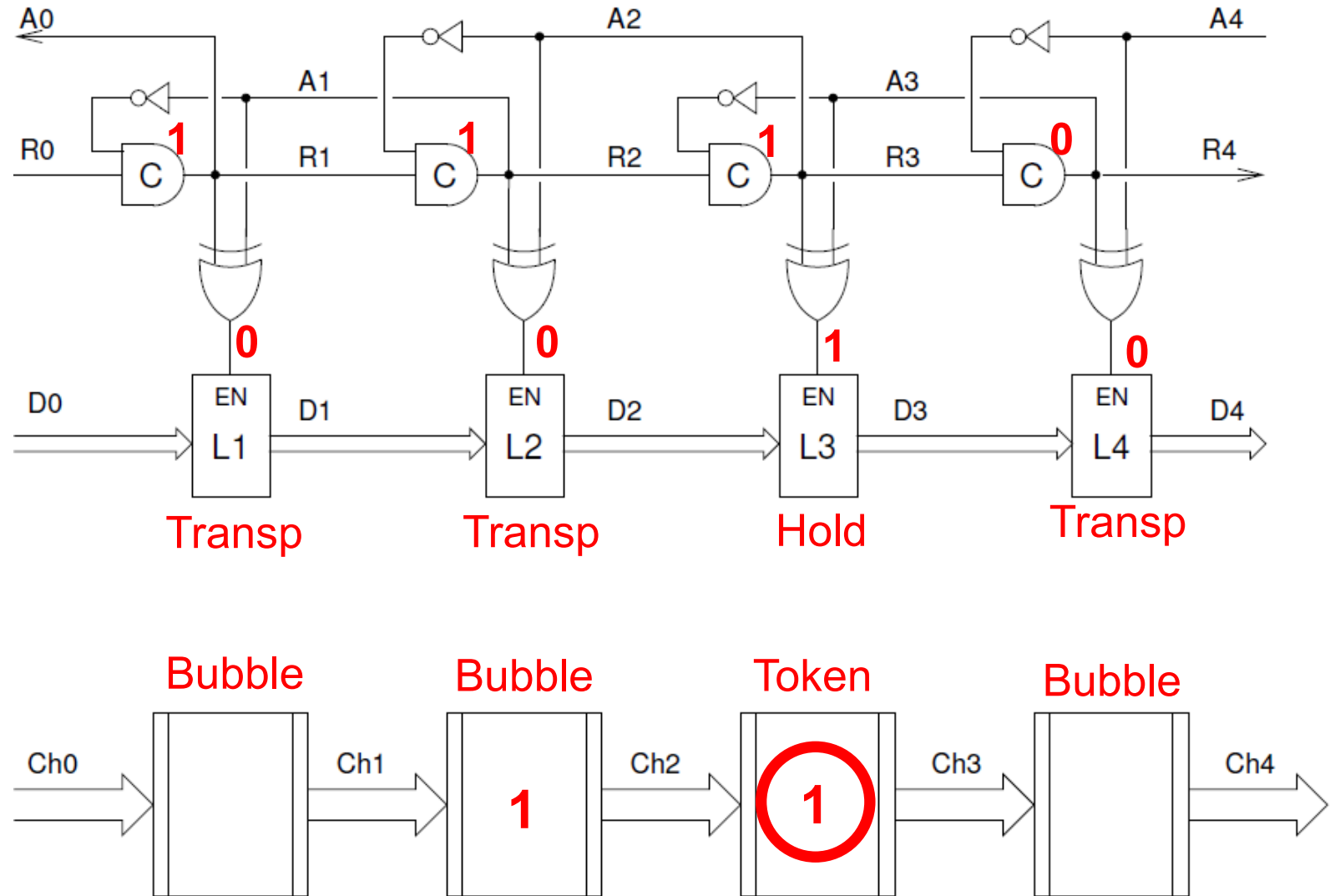


# Dataflow (tokens and bubbles)

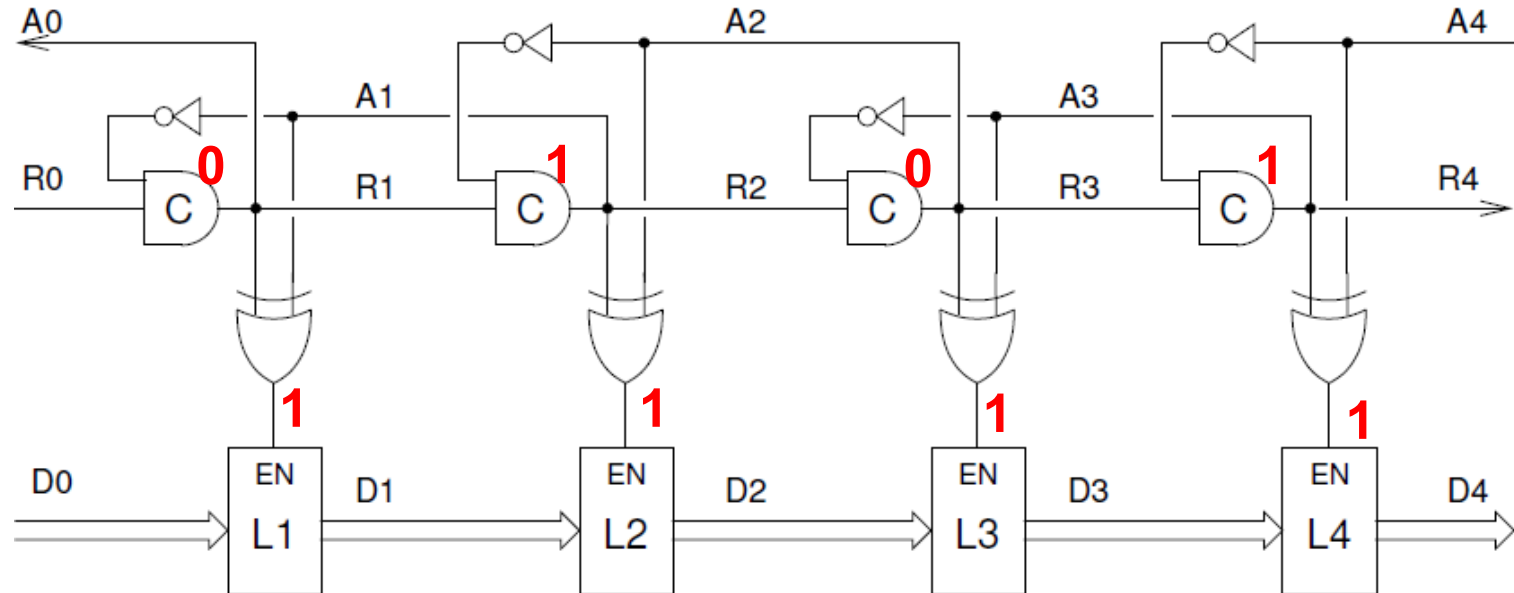


The pipeline may fill

 The circuit is both a pipeline and an elastic ripple FIFO



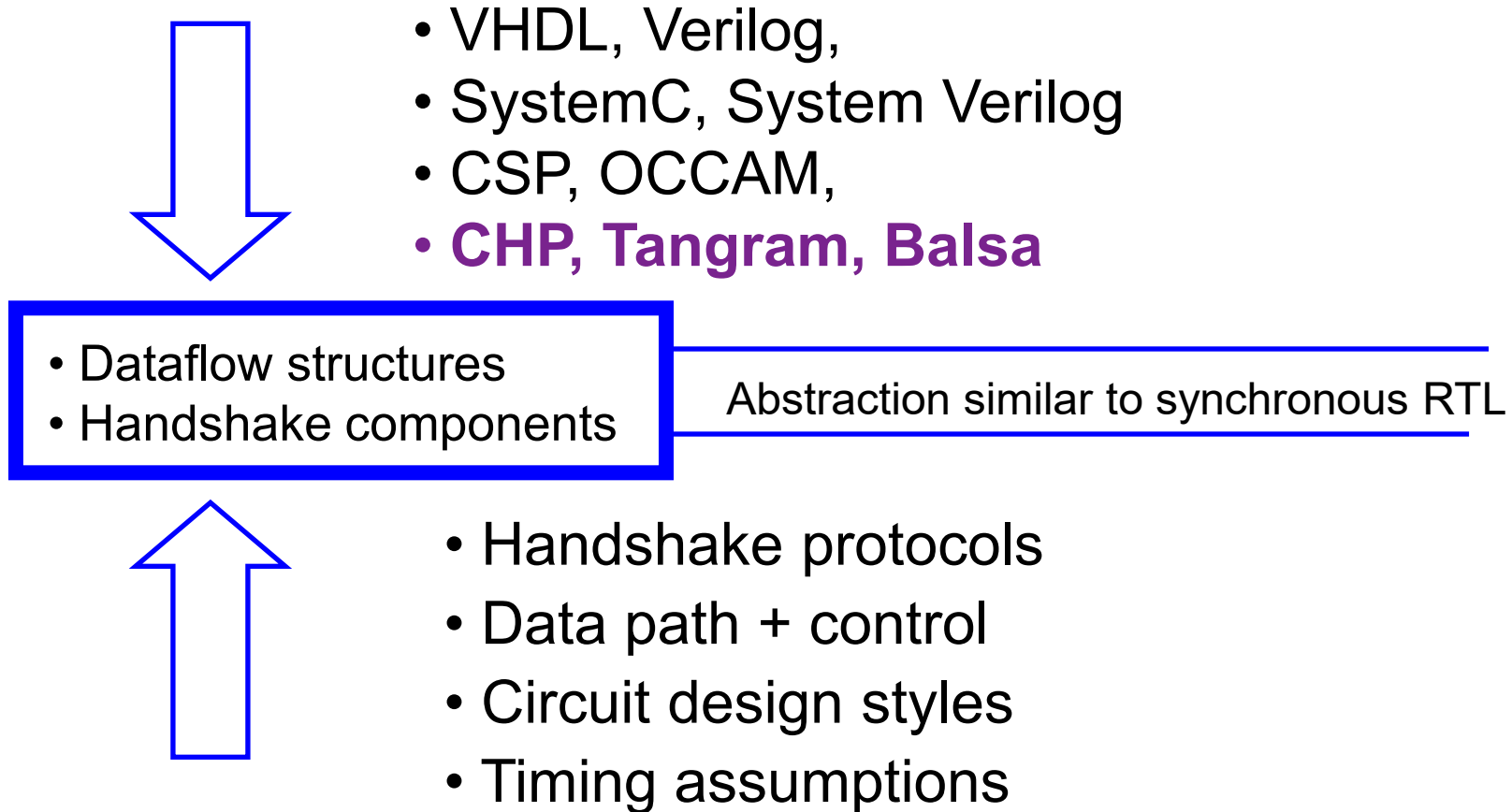
# Dataflow and asynchronous circuit design



 
# Building Blocks (data-flow components)



Active handshake components (handshake latches aka. buffers):




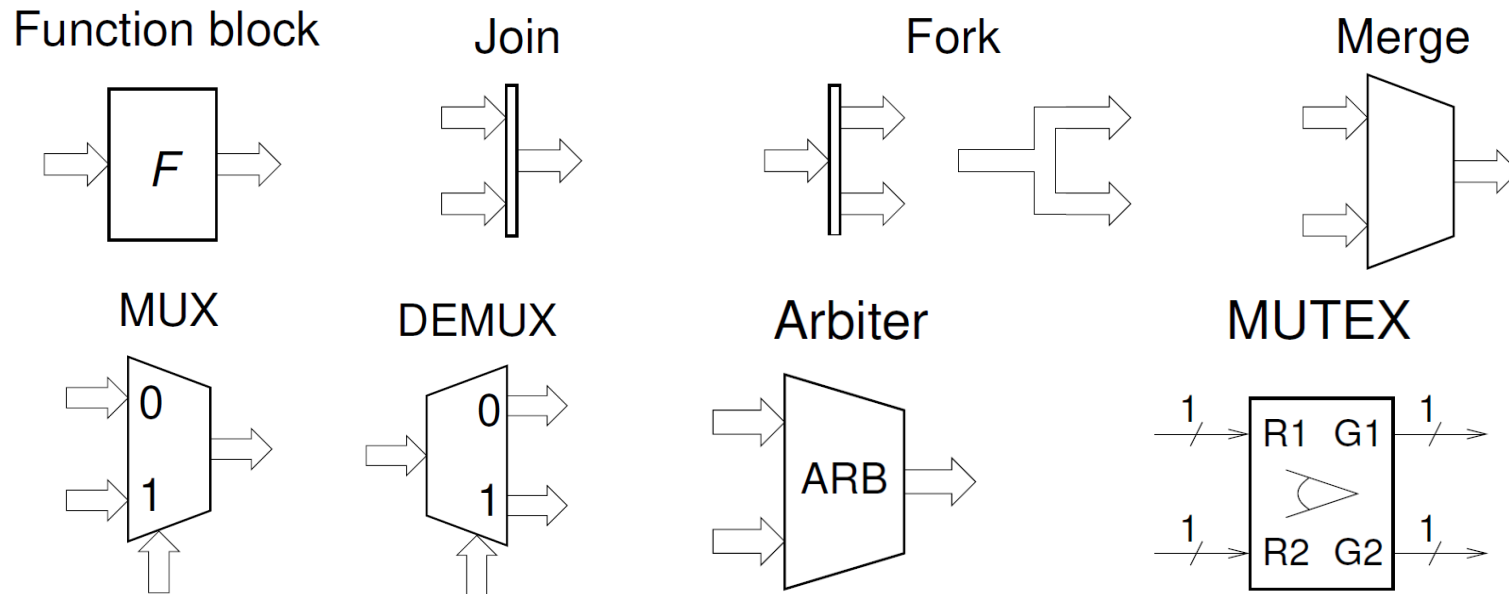
Passive handshake components (all other). Transparent to handshaking:




# Fork

  

# Join

  

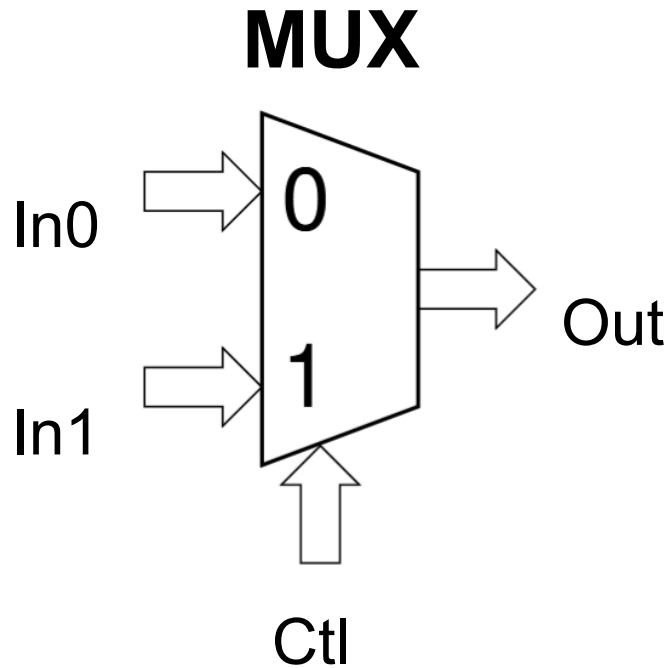

- When token on Ctl and selected input, propagate selected input to output
- A possible token on the other input is ignored
- Also known as: controlled merge, conditional join

A handshake-transparent implementation should:


- Join Ctl-Req and the selected Inx-Req and produce Out-Req
- Relay/propagate Inx-data to Out-data
- Propagate Out-Ack to Ctl-Ack and Inx-Ack

CHP-code from the 2022 summer school

```
*[Ctl?c;
  [ c=0 -> In0?x
  [] c=1 -> In1?x];
Out!x]
```


Note: does this perhaps describe a circuit with latch/buffer in Ctl and Out ports?

# MERGE

 

- Handshakes on In0 and In1 are mutually exclusive
- Active In-handshake relayed to output
- Also known as: MIXER, JOIN


# DEMUX

 


- When token on Ctl and In, propagate In-token to selected output channel
- Also known as: SPLIT

# Structures of handshake components

# IF statement

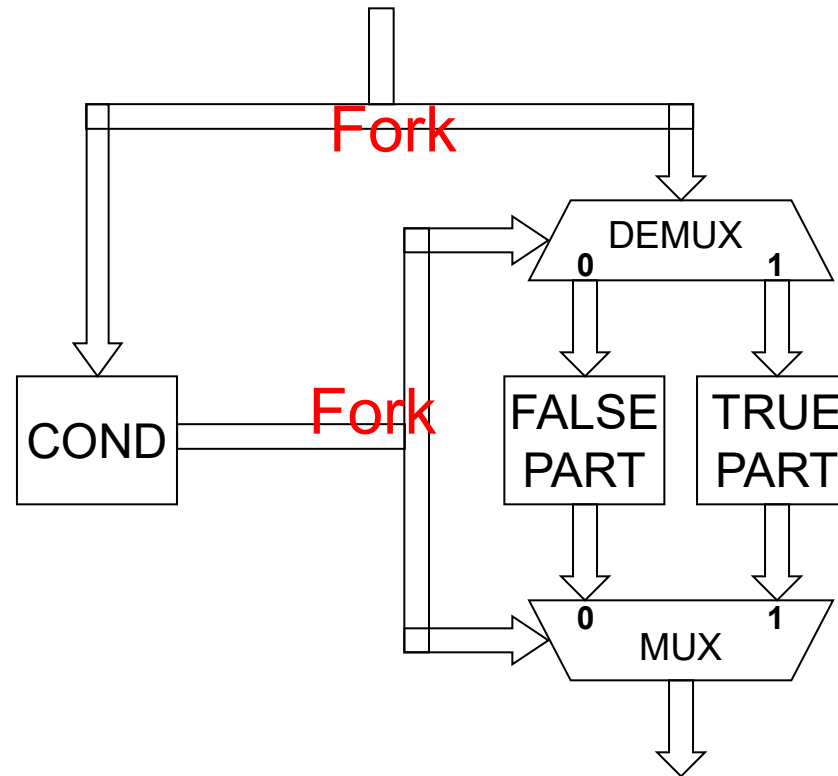


# IF statement

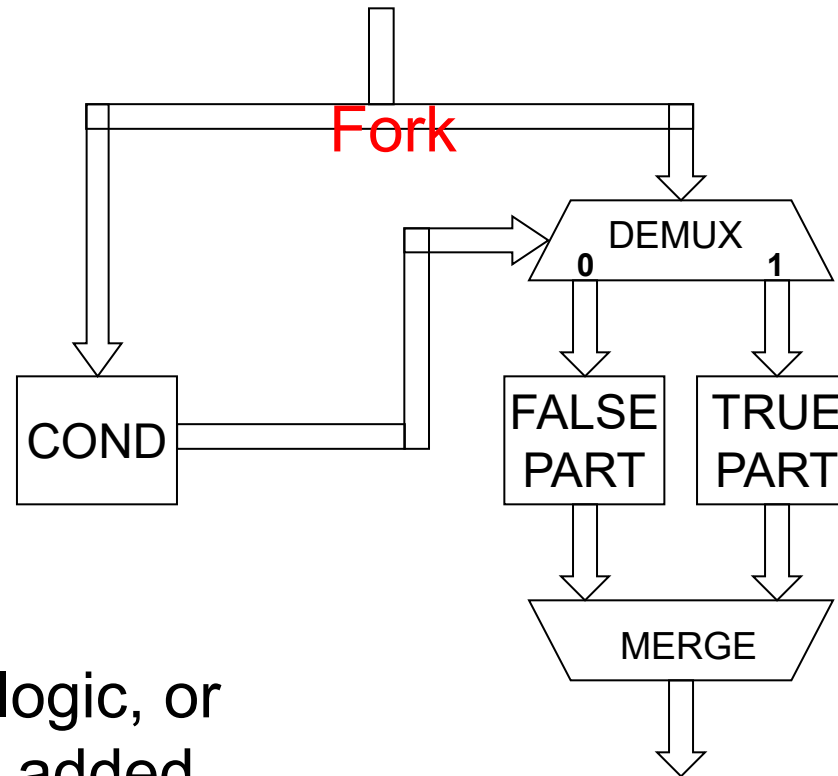

Combinational logic, or  
latches may be added

# WHILE statement


```
while <COND> do <BODY>
```

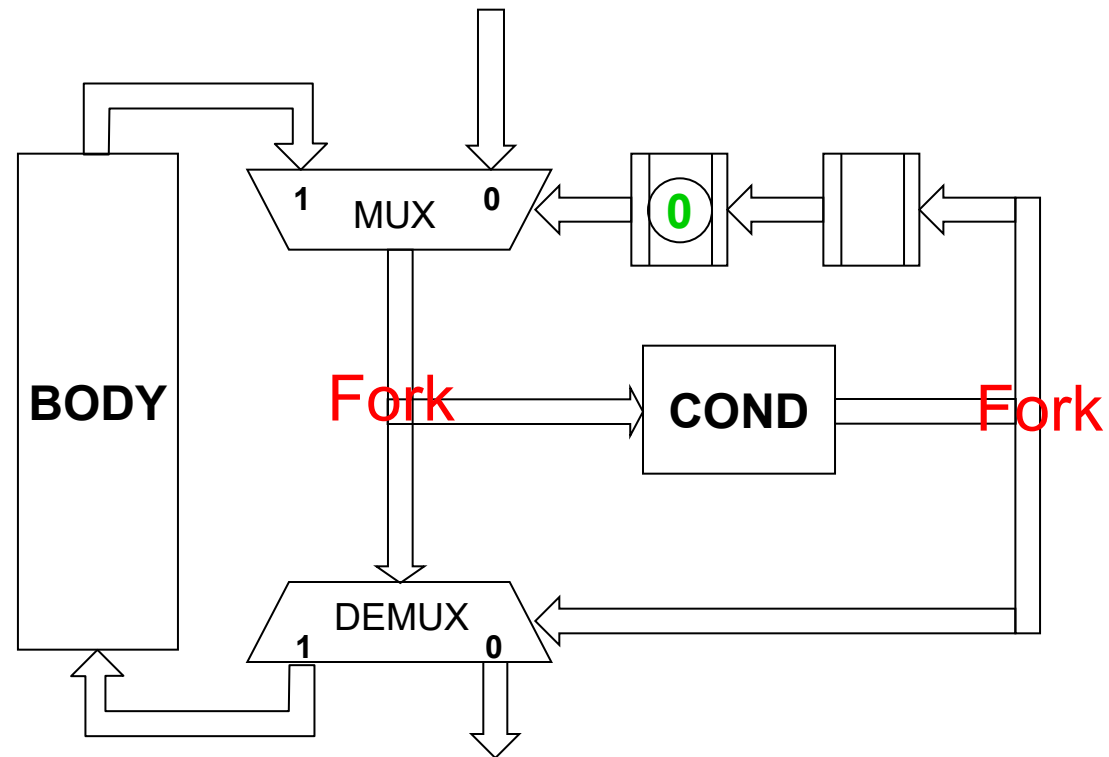



# WHILE statement

`while <COND> do <BODY>`

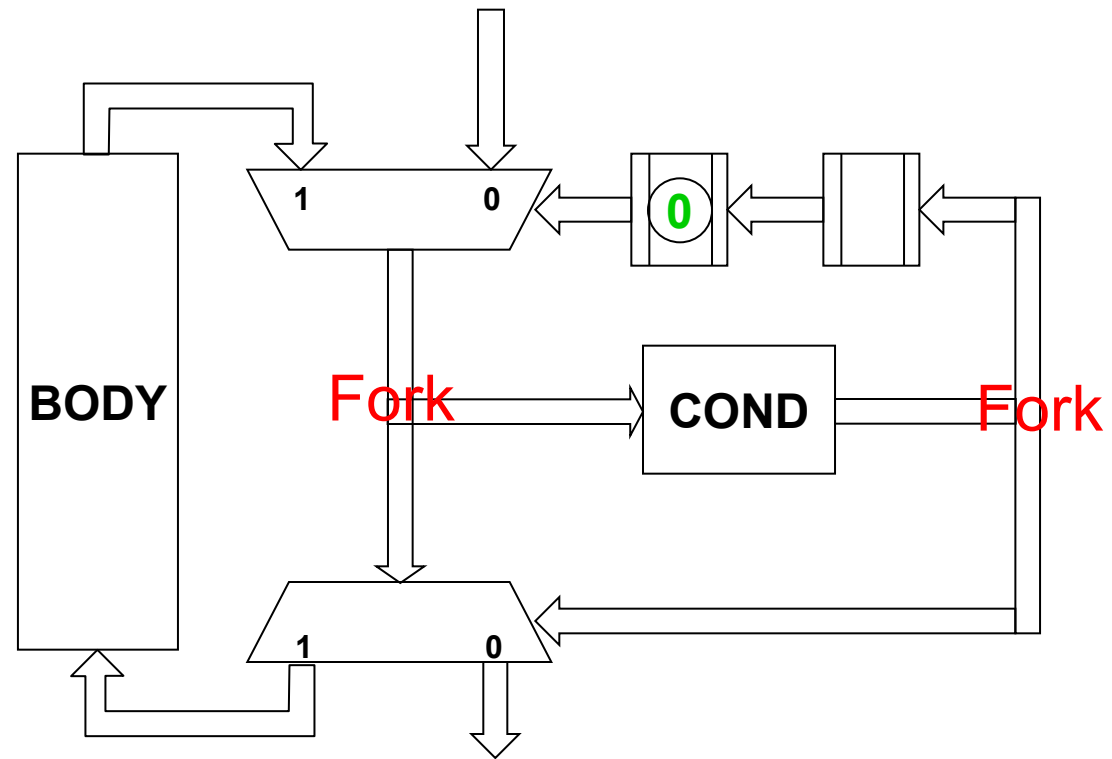



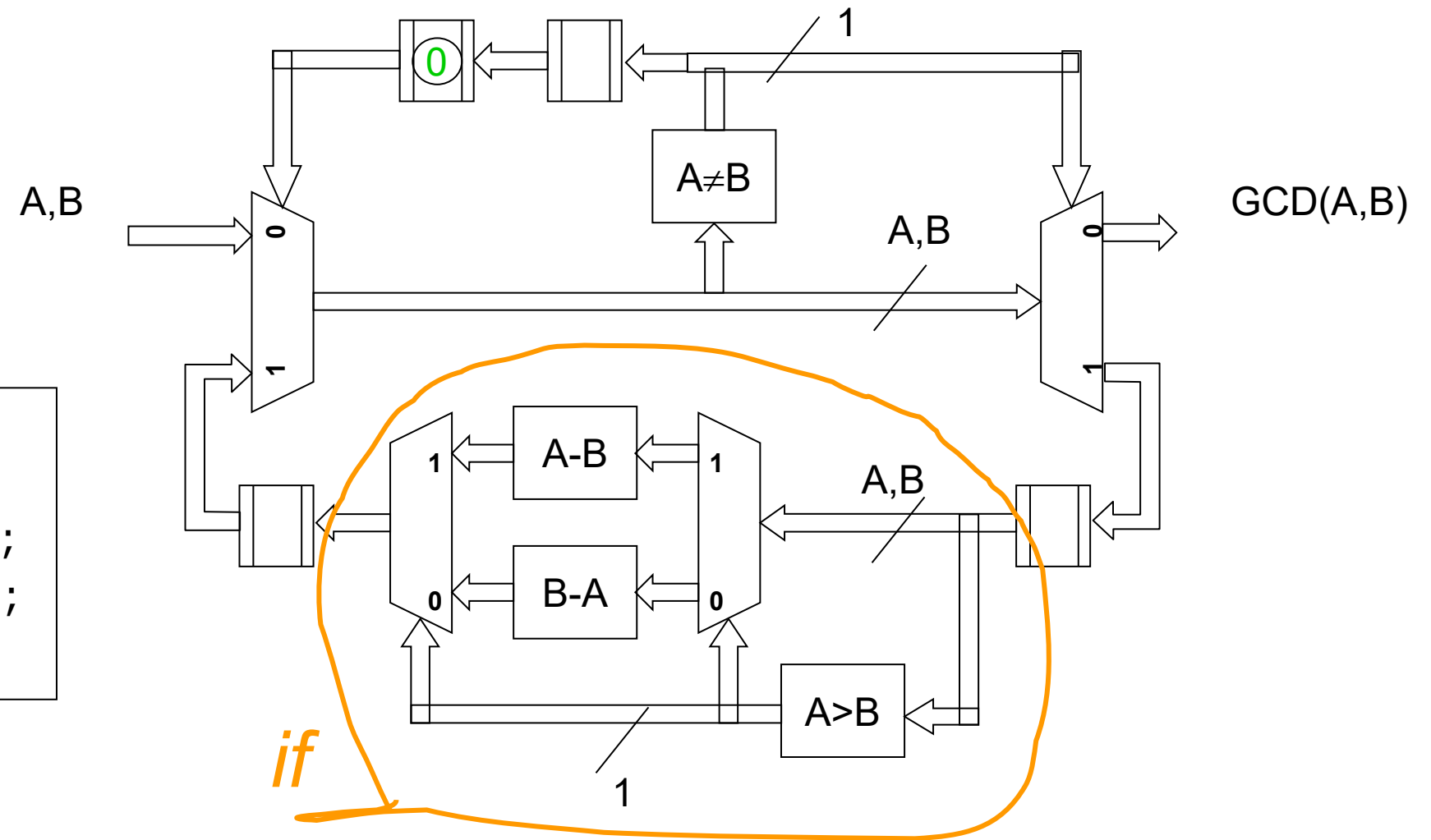
# Asynchronous GCD


```

input (a, b);
while a ≠ b do
  if a > b then a ← a-b ;
  else b ← b-a ;
output (a);
  
```



# Asynchronous processor (DTU's ARISC)
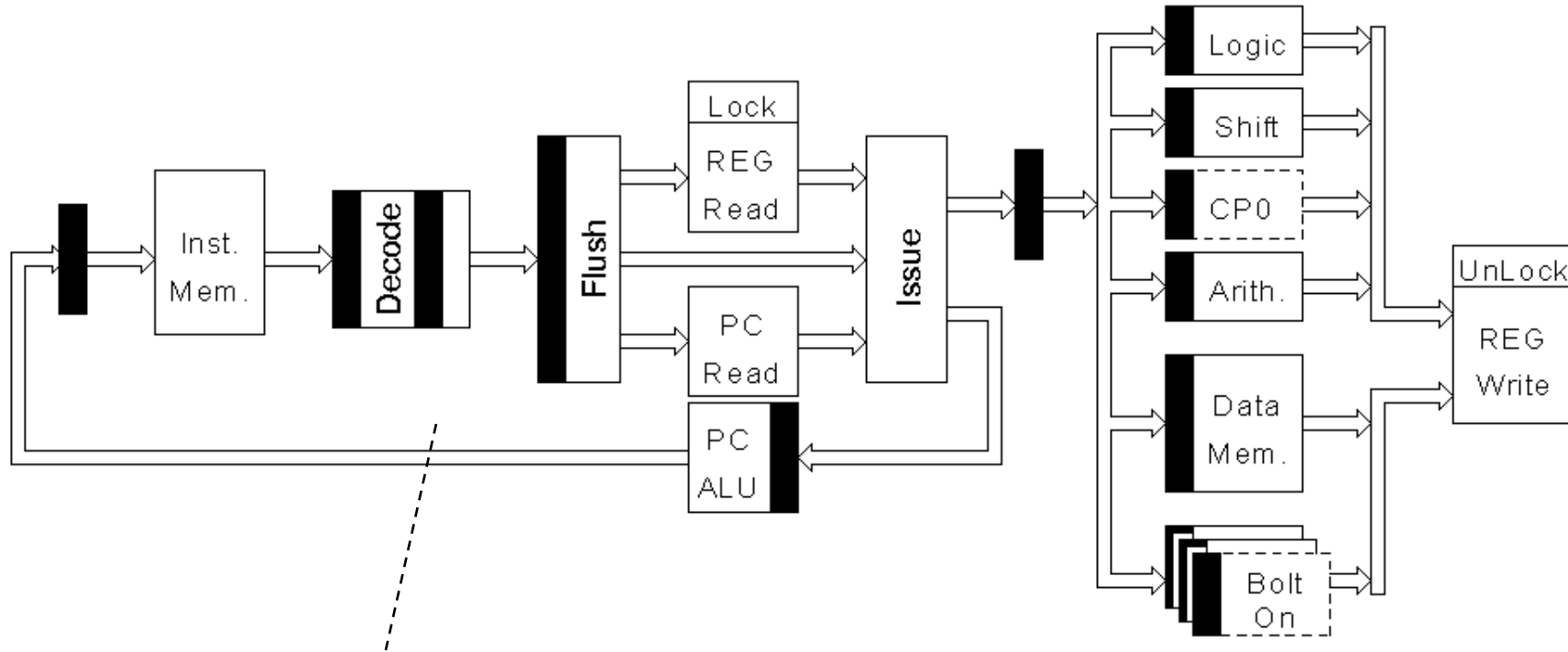
## LSI Logic TinyRISC (MIPS + MIPS16 isa):




Fetch-decode-issue ring  
with 2 tokens (=prefetch depth)


K. Christensen, P. Jensen, P. Korger and J. Sparsø,  
"The design of an asynchronous TinyRISC microprocessor core,"  
Proc. ASYNC'98, IEEE, 1998, pp. 108-119.

# Fibonacci circuit





Synchronous

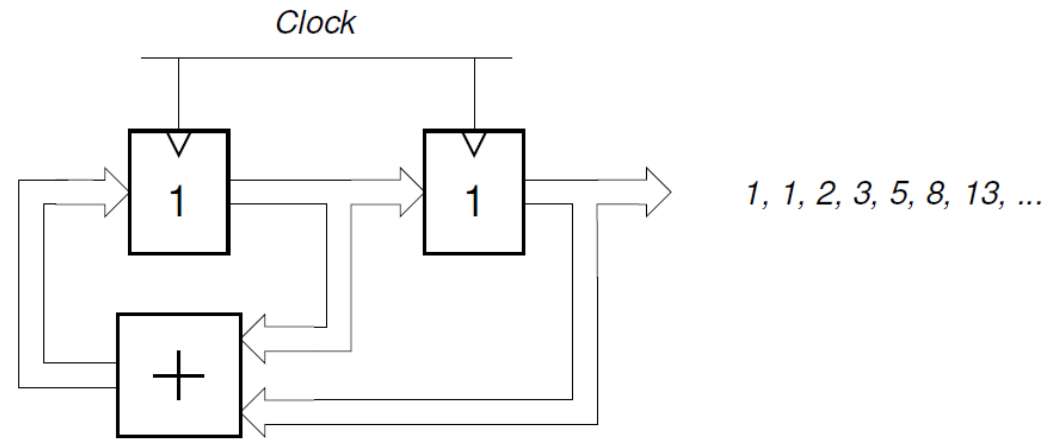

Asynchronous

 


# Asynchronous Fibonacci circuit

 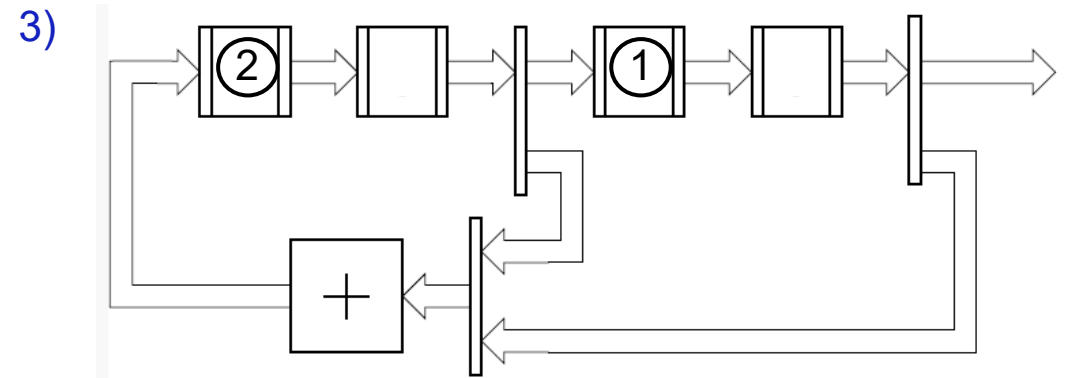  

# Performance; mostly qualitative


- Dynamic behavior
  - Example 1: A shift register  $\approx$  a ring
  - Example 2: A FIFO
- Performance parameters
  - dynamic wavelength (dynamic wavelength forward latency, reverse latency, and cycle time).

## Example: A shift register

 


- An N stage FIFO or pipeline whose environment alternately accepts and produces tokens
- Assume the FIFO is full
- Same as N+1 stage ring with N tokens and 1 bubble
- After initialization, the number of tokens is *invariant*

# Shift register (ring) performance

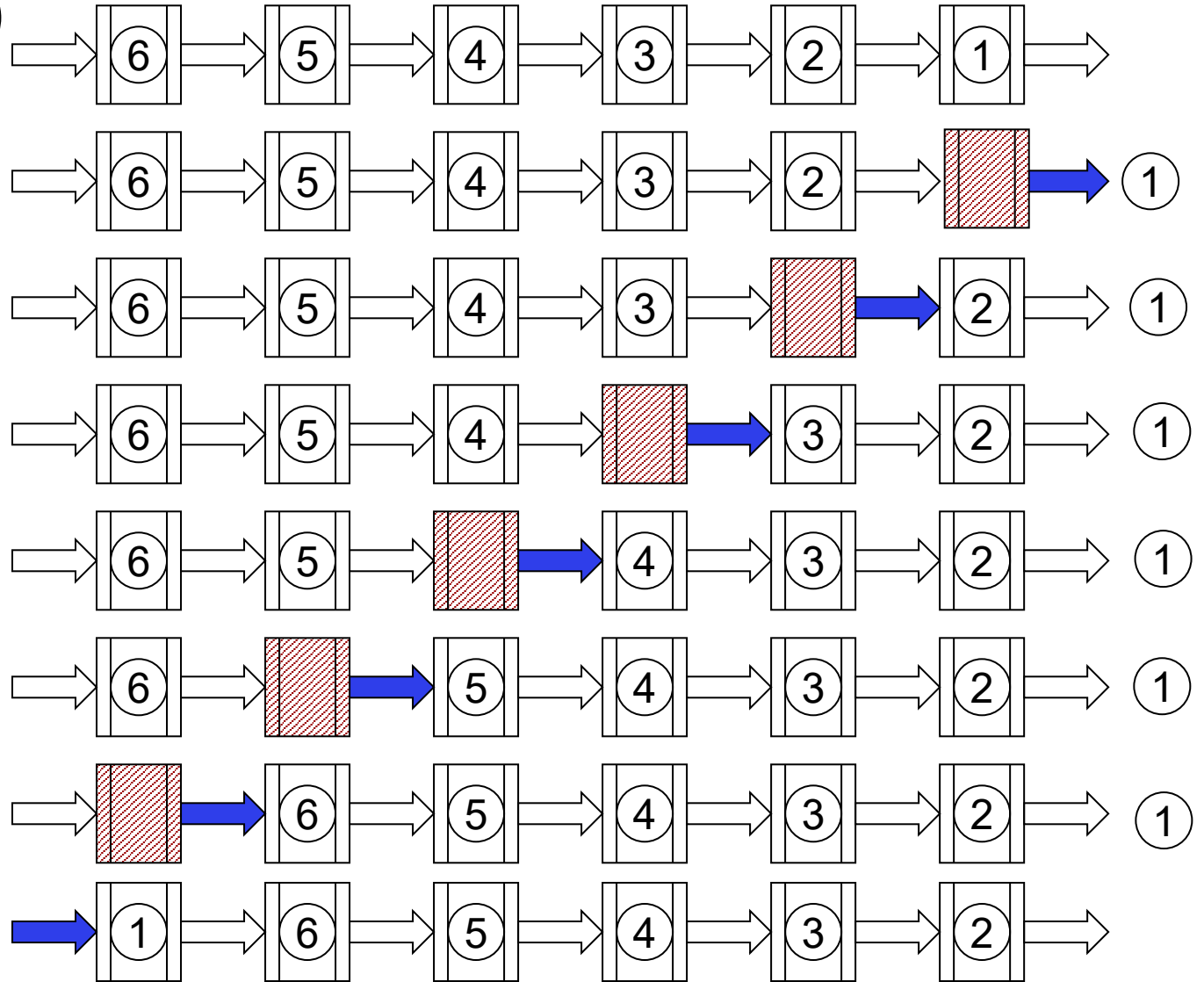

Only one bubble  
Ripples backward

## Example: Pipeline / FIFO

 


- Same circuit and same initialization (N stages, N tokens, no bubbles)
- Fast and independent producer and consumer.
- Start the circuit and observe its behavior

# FIFO / Pipeline performance


Reaches a steady-state where the time separation between successive tokens passing through a channel is minimum

The distance between successive tokens (measured as a number of latch stages) is the **dynamic Wavelength**

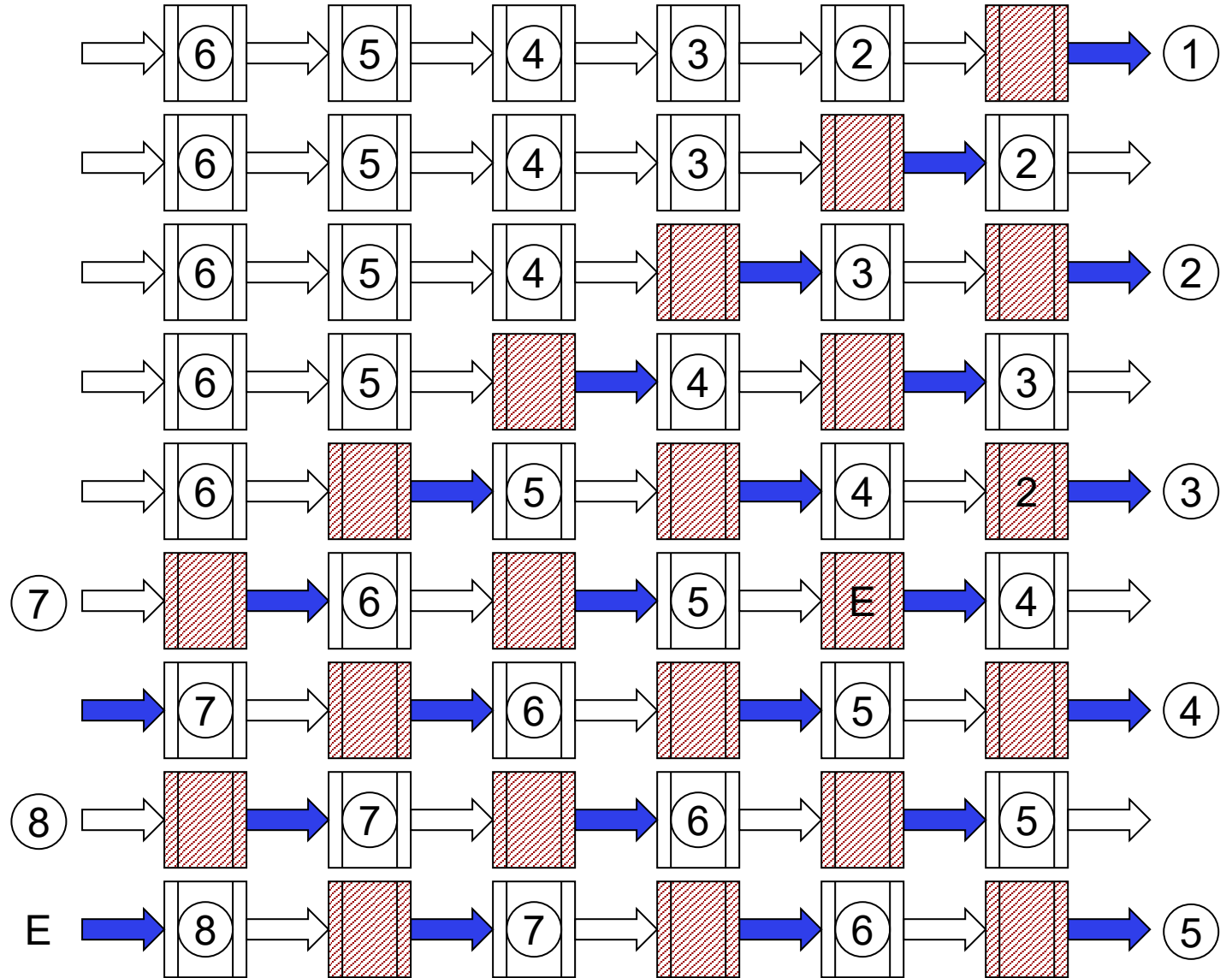Here  $W_d = 2$ , but in an actual circuit Implementation it can be any rational number.




# Dynamic wavelength

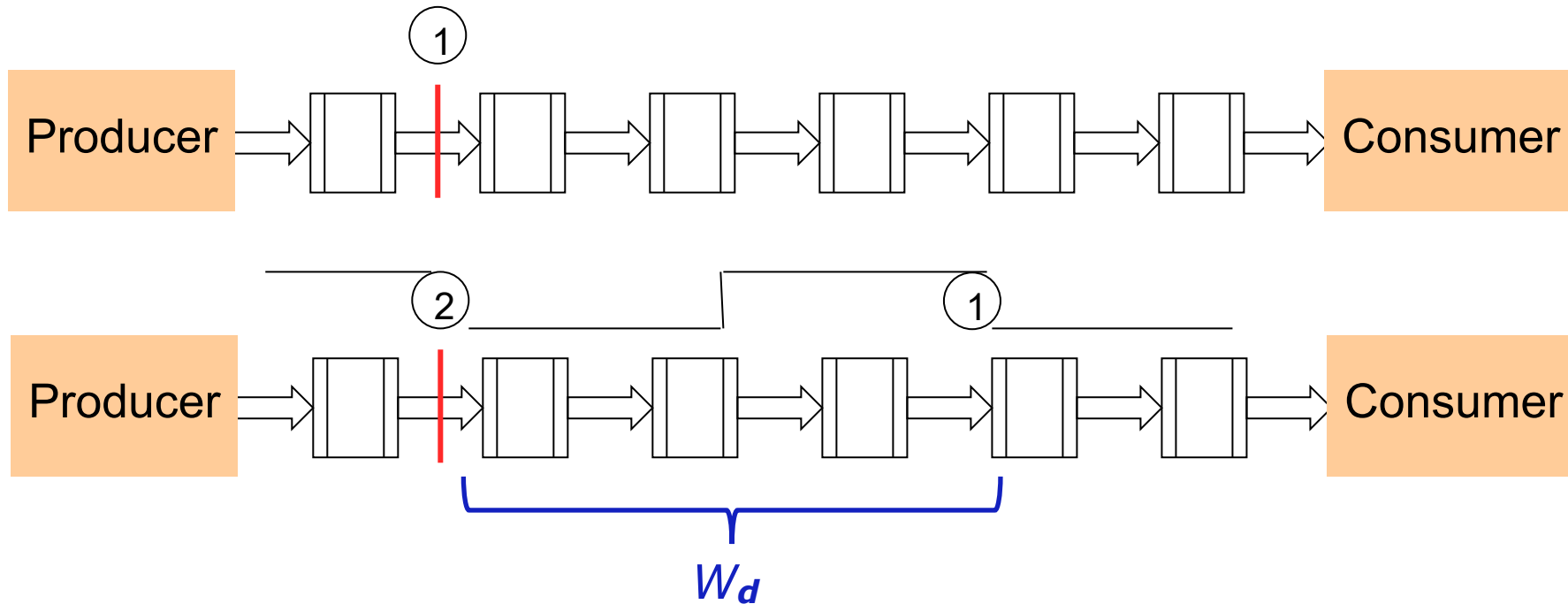

- $T_{cycle}$  is time from one token to the next
- During  $T_{cycle}$  the first token propagates through  $W_d$  stages  
(Think of a token as the front of a wave)

# Dynamic wavelength

 


Time for a handshake  
on a given channel

$$T_{cycle} \geq L_f + L_r$$

During time  $T_{cycle}$ , a token  
propagates forward  
through  $W_d$  stages

Best performance if  
 $W_d$  stages per token

# Dynamic wavelength

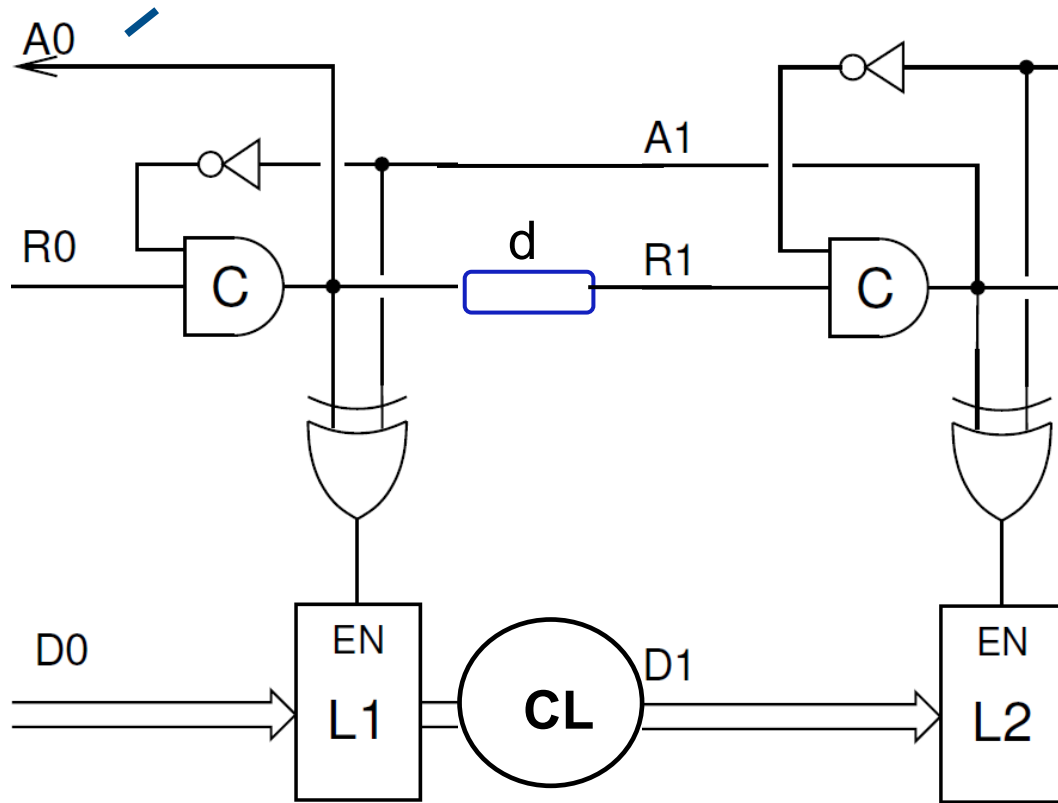


Time for a handshake  
on a given channel

$$T_{cycle} \geq L_f + L_r$$

During time  $T_{cycle}$ , a token  
propagates forward  
through  $W_d$  stages

Best performance if  
 $W_d$  stages per token

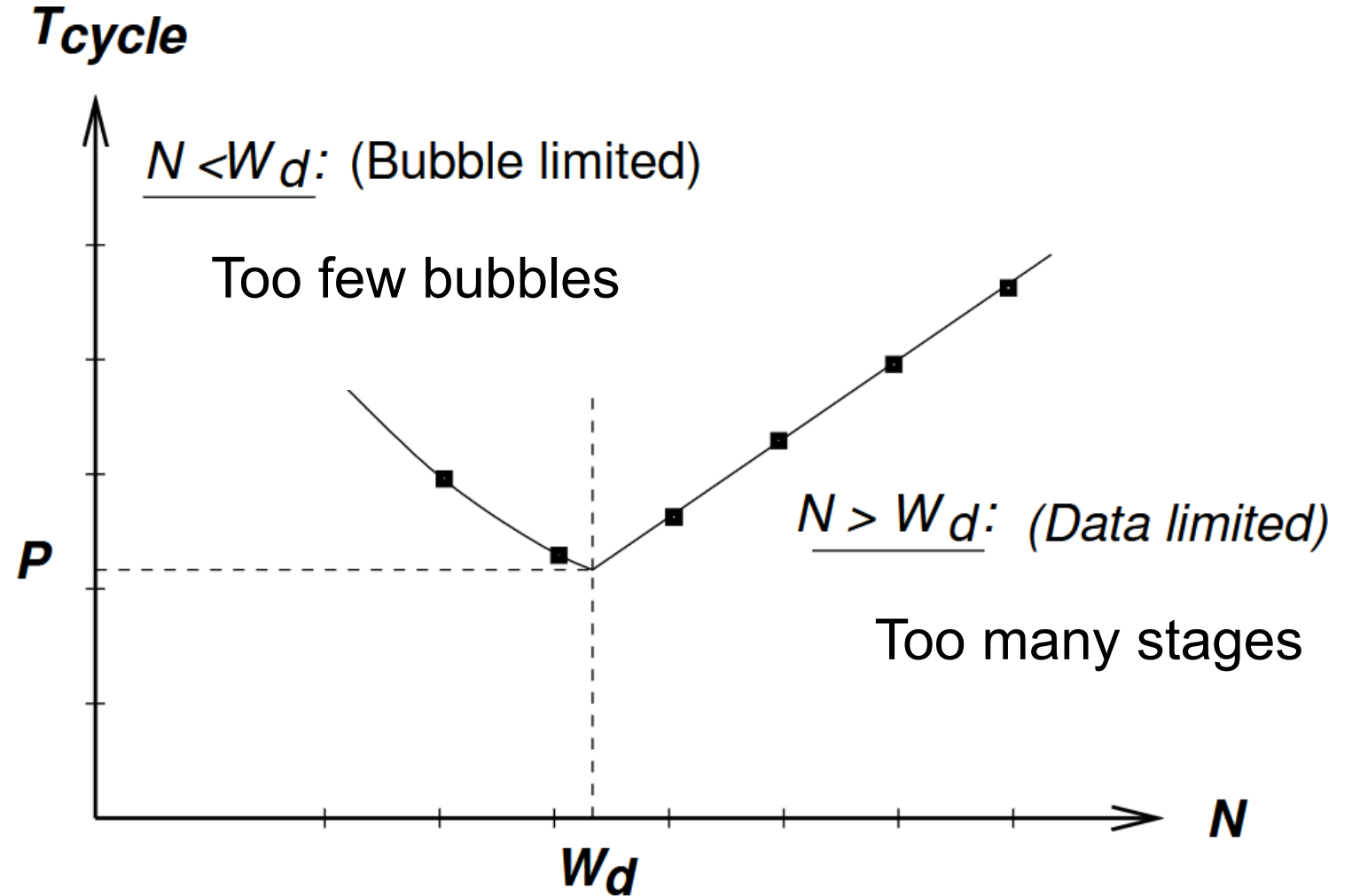
# Cycle time for N-stage ring with 1 token (time for the token to make one roundtrip)



# Conclusion

- Dataflow is an intuitive paradigm for describing asynchronous circuits.
- Handshake components:
  - Actively handshaking: Source, sink, (handshake) latch/buffer
  - Transparent to handshaking: fork, join, mux, demux. Merge, arbiter
  - (Data) tokens and bubbles
- Flow of tokens determines the function of the circuit,
- Adding or removing handshake latches initialized to bubbles affects performance, but does not change functionality
- Some example circuits (if-then-else, while, for, FIB, GCD, processor)
- A qualitative view on the performance of pipelines and rings
  - Balancing the number of tokens and bubbles (aka. Slack matching)
  - Dynamic wavelength.

# Reading

 

- Jens Sparsø,  
*Introduction to Asynchronous Circuit Design*  
DTU Compute, Technical University of Denmark  
2020. (273 pages)
- Download free version by following the link given on my homepage <https://people.compute.dtu.dk/jspa/>
- Or buy the paperback book from Amazon for just 11 USD

