

# From Dataflow to Circuits (Mousetrap Circuit Style)

---

Montek Singh  
UNC Chapel Hill

ASYNC 2026 Summer School  
Day 1: June 1

# Outline

- \* Circuit implementation style
  - MOUSETRAP
- \* Design example
  - Greatest-Common Divisor (GCD)

# Implementation of asynchronous pipelines

---

MOUSETRAP Circuit Style

# MOUSETRAP Pipelines

[Singh/Nowick, ICCD 2001 & TVLSI 2007]

Simple asynchronous implementation style, uses...

- *transparent D-latches + standard combinational function logic*
- *simple control:* 1 gate/pipeline stage

Uses a “capture protocol”: Latches are ...

- normally transparent while waiting for data
- become opaque after data arrives


Control Signaling: *transition-signaling (2-phase) + bundled data*

Goals:

- fast cycle time
- simple inter-stage communication
- standard cell implementation
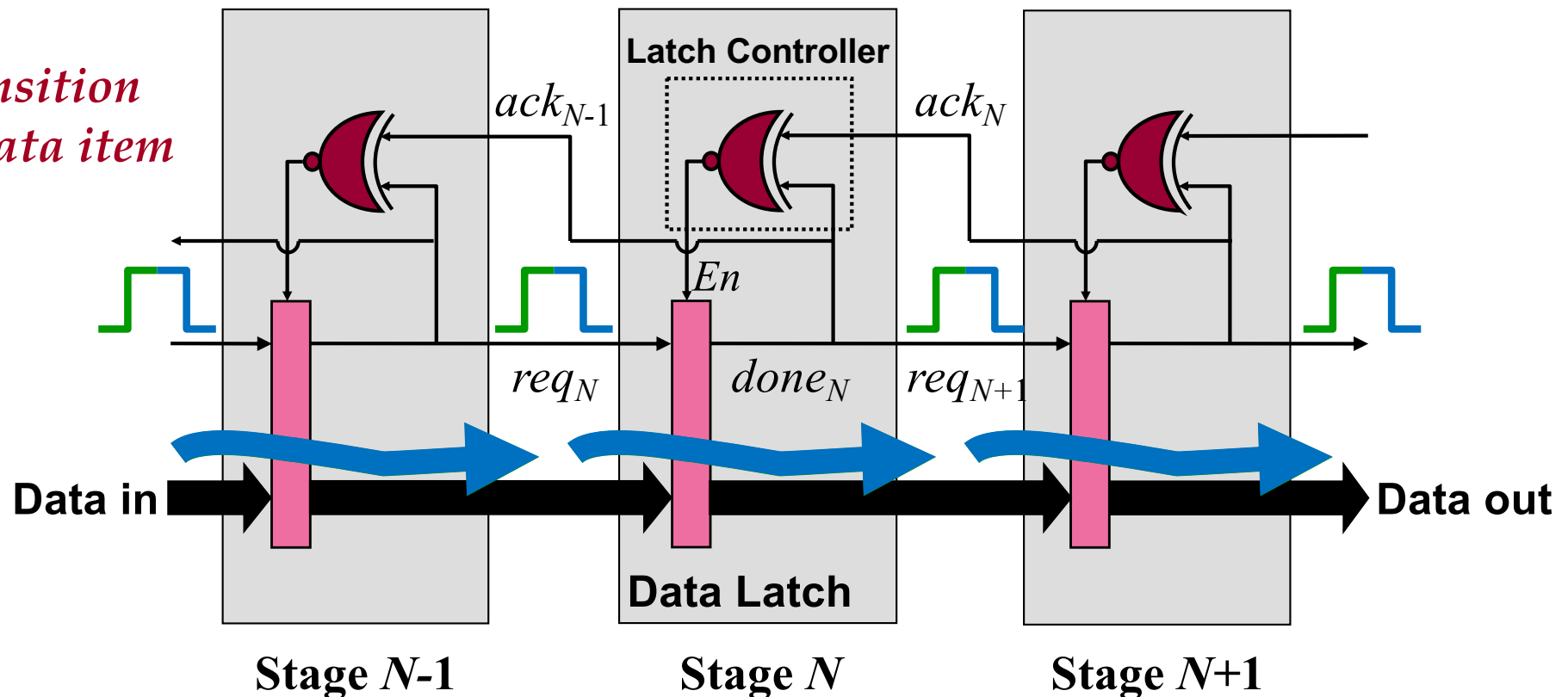
# MOUSETRAP: A Basic FIFO



Stages communicate using *transition-signaling*:



2<sup>nd</sup> data item flowing through the pipeline




# MOUSETRAP: FIFO Cycle Time

 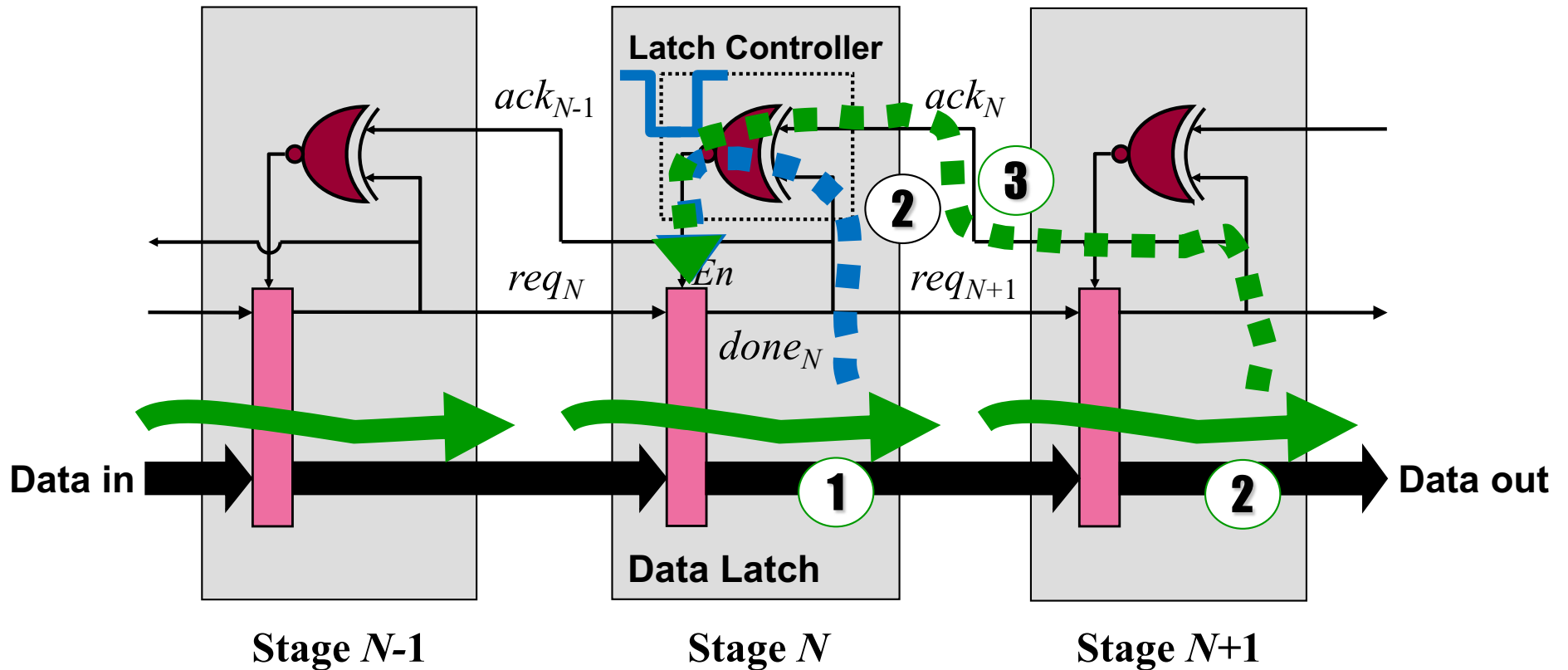
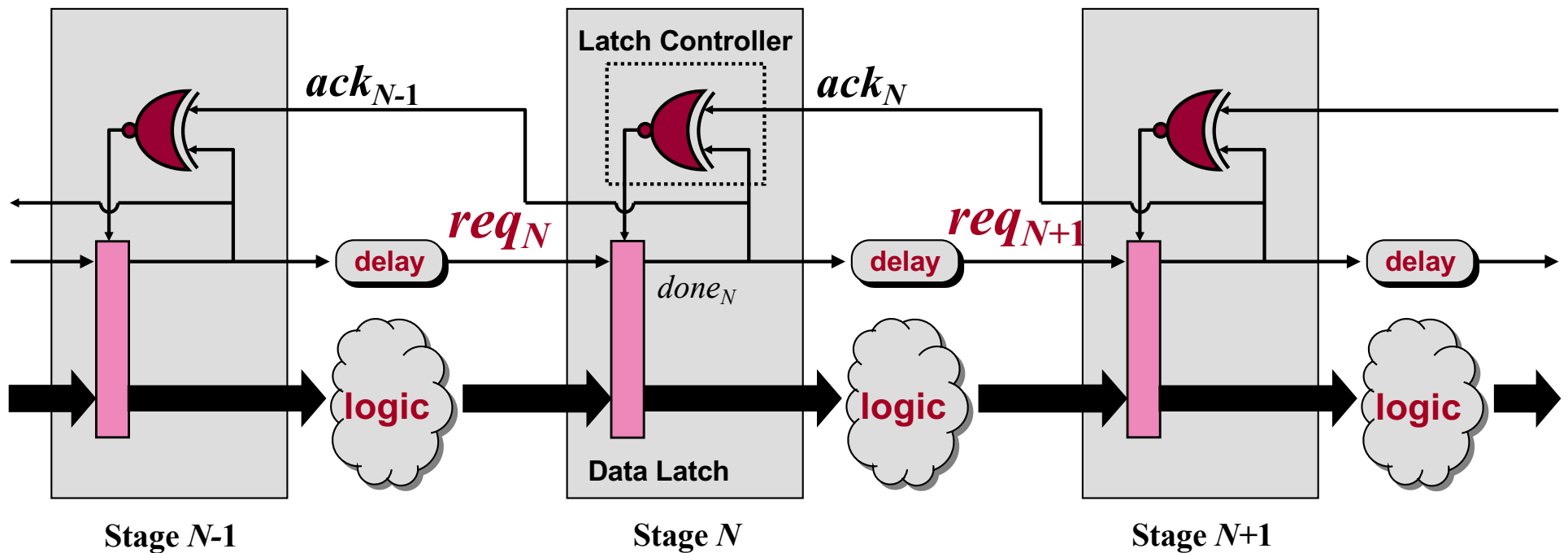
# MOUSETRAP: Pipeline With Logic

Simple Extension to FIFO:

insert *logic block* + *matching delay* in each stage




"Bundled Data" Requirement:

- each *req* must arrive *after* data inputs valid and stable



 
# Fork

- \* A fork stage has two (or more) successors
  - same data and req sent to all
  - wait for ack from all



**Fork Stage**

# Fork

  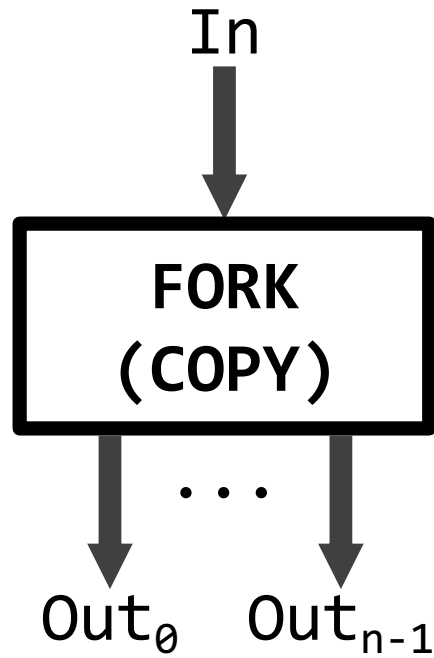


**Fork Stage**

\*[In?x; Out<sub>0</sub>!x, ..., Out<sub>n-1</sub>!x]



 
# Join

\* A join stage has two (or more) predecessors

- wait for data from all
- same ack sent to all




# Join

   

```
*[ In0?arg0, In1?arg1, ... , Inn-1?argn-1;  
  Out!func(arg0,arg1,...,argn-1)  
]
```
 
# Arbitration Stage

- \* Two input channels, two output channels
- \* Only one input read
  - whichever arrives first
  - ... goes out on the corresponding output
- \* Seitz' Mutex is the core
  - [from Brunvand's thesis]
  - surrounding logic adapts it to transition signals




# Merge without (or after) Arbitration

\* A merge stage has two (or more) predecessors

- data is taken from whichever input channel has a new request

\* Assumption:

 - no arbitration needed
- input channels are mutually exclusive




**Merge w/o arbitration**



# Merge without (or after) Arbitration
 
## \* Datapath

- mux controlled by change detectors on input channels


  
```
*[ [ #In_0 -> In_0?x
  [] #In_1 -> In_1?x
  ];
  Out!x
]
```



# Conditional Select (or event mux)

## \* Two data inputs and one select


- first read select

- then:


- based on select, read one of the inputs
- do not read the other input

- datapath

- mux + latch

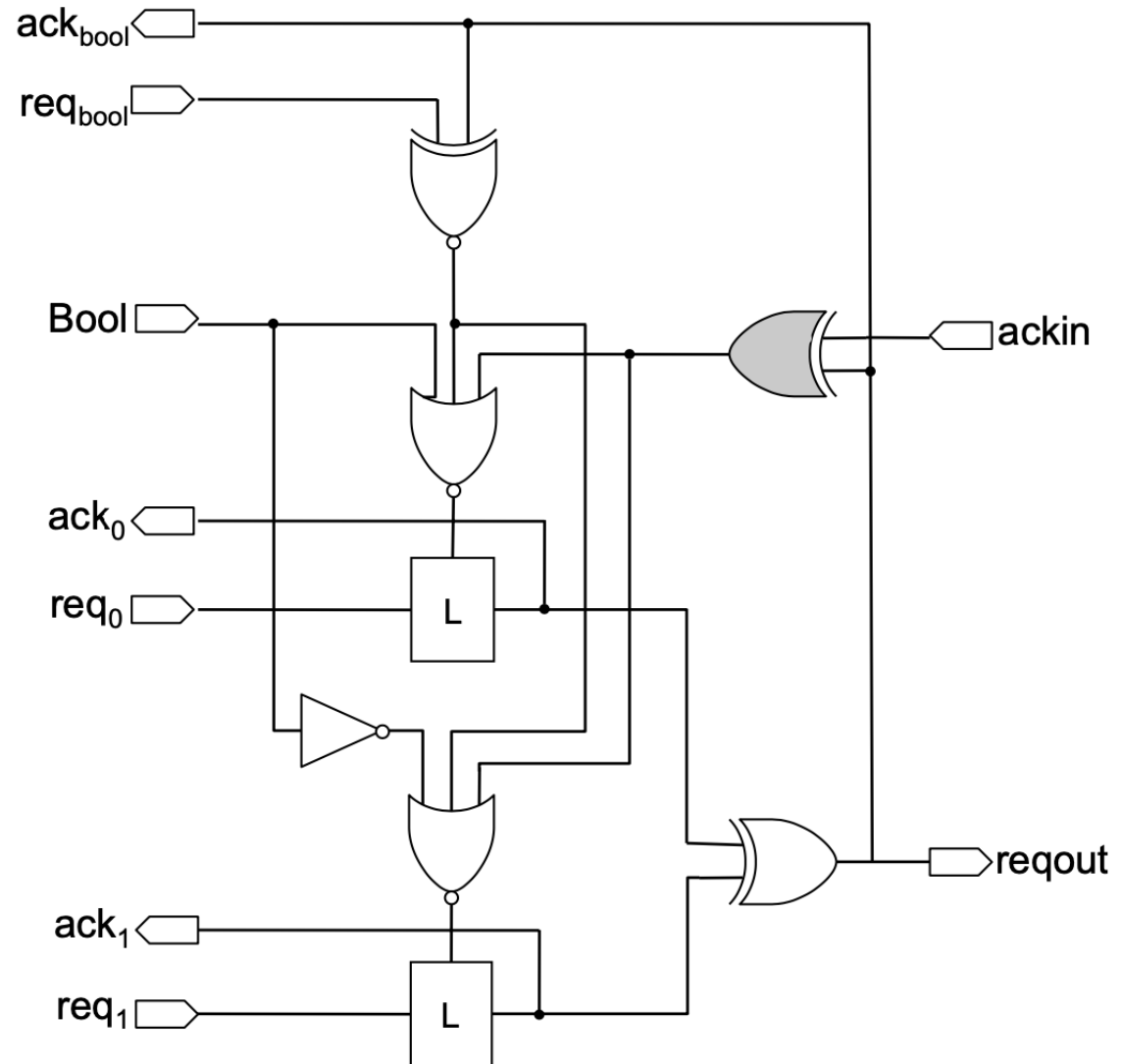


# Conditional Select (or event mux)

 

```

 
*[C?c;
 [ c=0 -> In_0?x
 [] c=1 -> In_1?x
 ];
 Out!x
 ]
    
```




# Conditional Split (or router)
 
## \* One data input and one select


- first read data + select
- then:
  - based on select, send data along one output channel



# Conditional Split (or router)

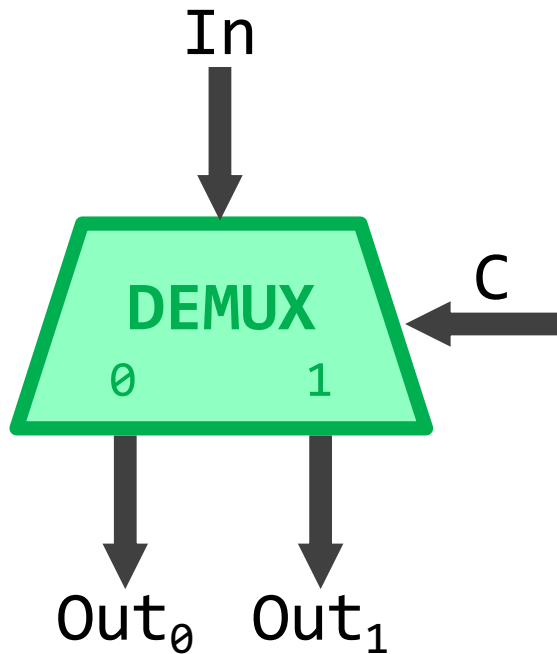
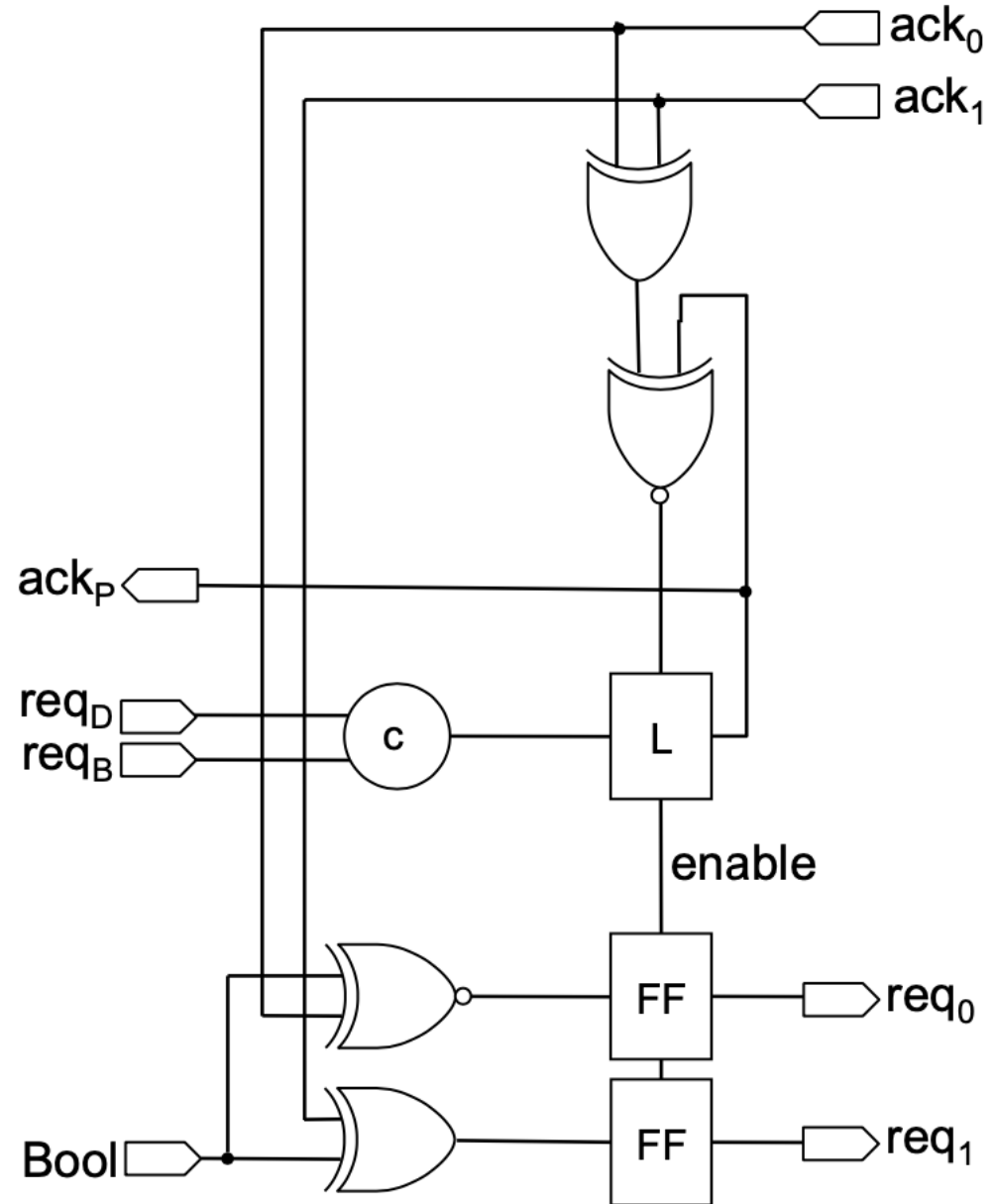
```
*[In?x, C?c;  
  [ c=0 -> Out0!x  
  [ ] c=1 -> Out1!x  
  ]  
]
```





# Example: Greatest Common Divider

---

# Euclid's GCD algorithm

```
gcd(a, b)
  while (b != 0)
    if(a>b)
      a = a - b
    else
      b = b - a
  return a
```

## \* Example

- gcd(42, 28)
- (14, 28)
- (14, 14)
- (14, 0)
- → 14

# Euclid's GCD algorithm

`gcd(a, b)`

`while (b != 0)`


`if(a>b)`

`a = a - b`

`else`

`b = b - a`

`return a`

 

# Better area version

`gcd(a, b)`


`while (b != 0)`

```
s = a-b
if(s<0)
    swap(a,b)
else
    a = s
```

`return a`

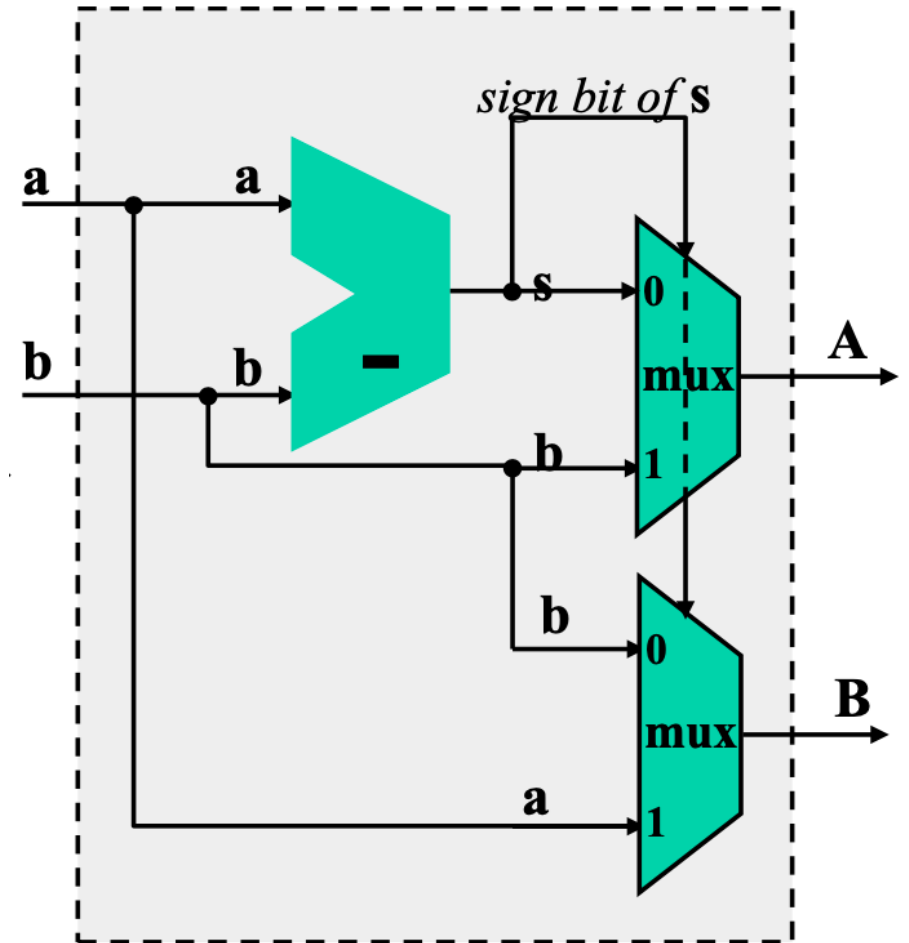
## \* Example

- `gcd(42, 28)`
- `(14, 28)`
- `(28, 14)`
- `(14, 14)`
- `(0, 14)`
- `(14, 0)`
- `→ 14`



 
# Dataflow: WHILE loop structure

```
while (b != 0)
  s = a-b
  if(s<0)
    swap(a,b)
  else
    a = s
return a
```


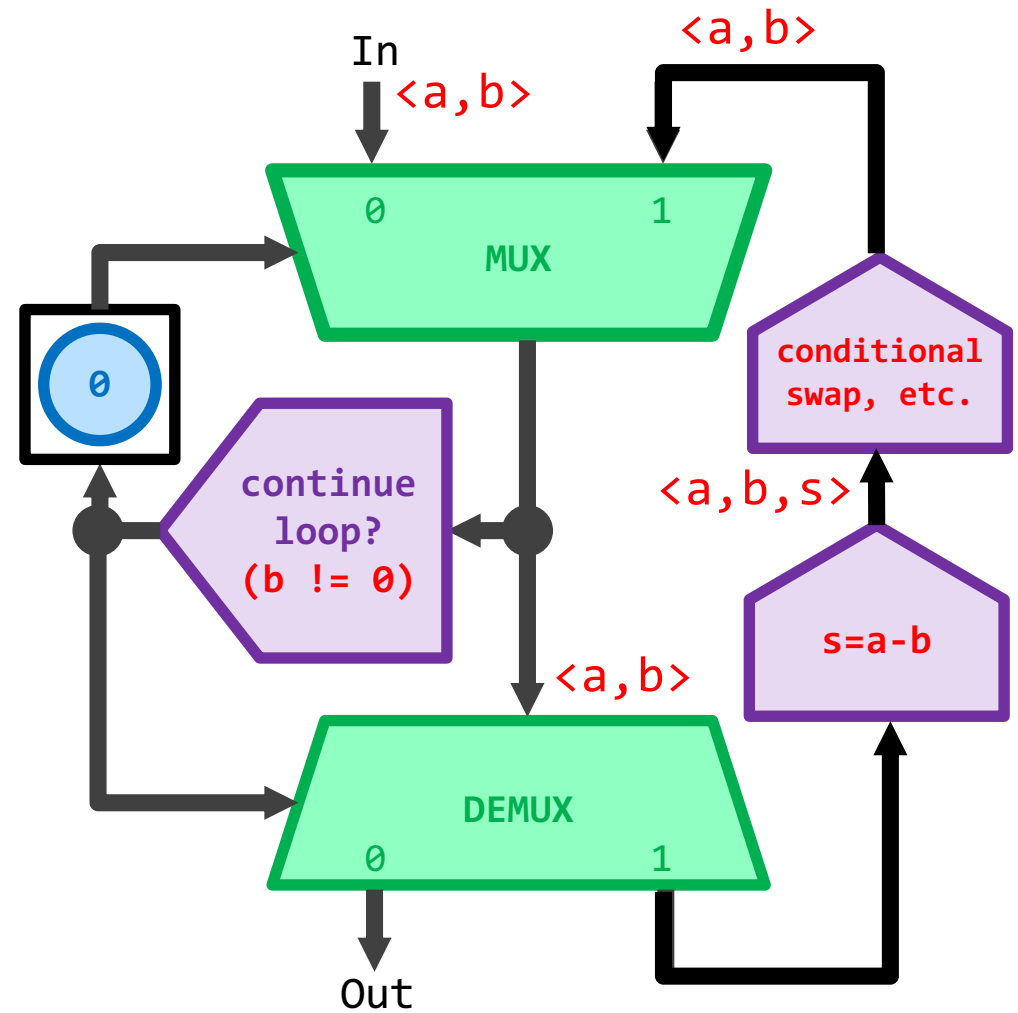
# GCD implementation

```
while (b != 0)
  s = a-b
  if(s<0)
    swap(a,b)
  else
    a = s
return a
```



# GCD implementation

```
while (b != 0)
```


```
  s = a-b  
  if(s<0)  
    swap(a,b)  
  else  
    a = s
```

```
return a
```

Unroll 8 times!

Pipeline subtract  
into 8 stages

Pipeline swap  
into 4 stage


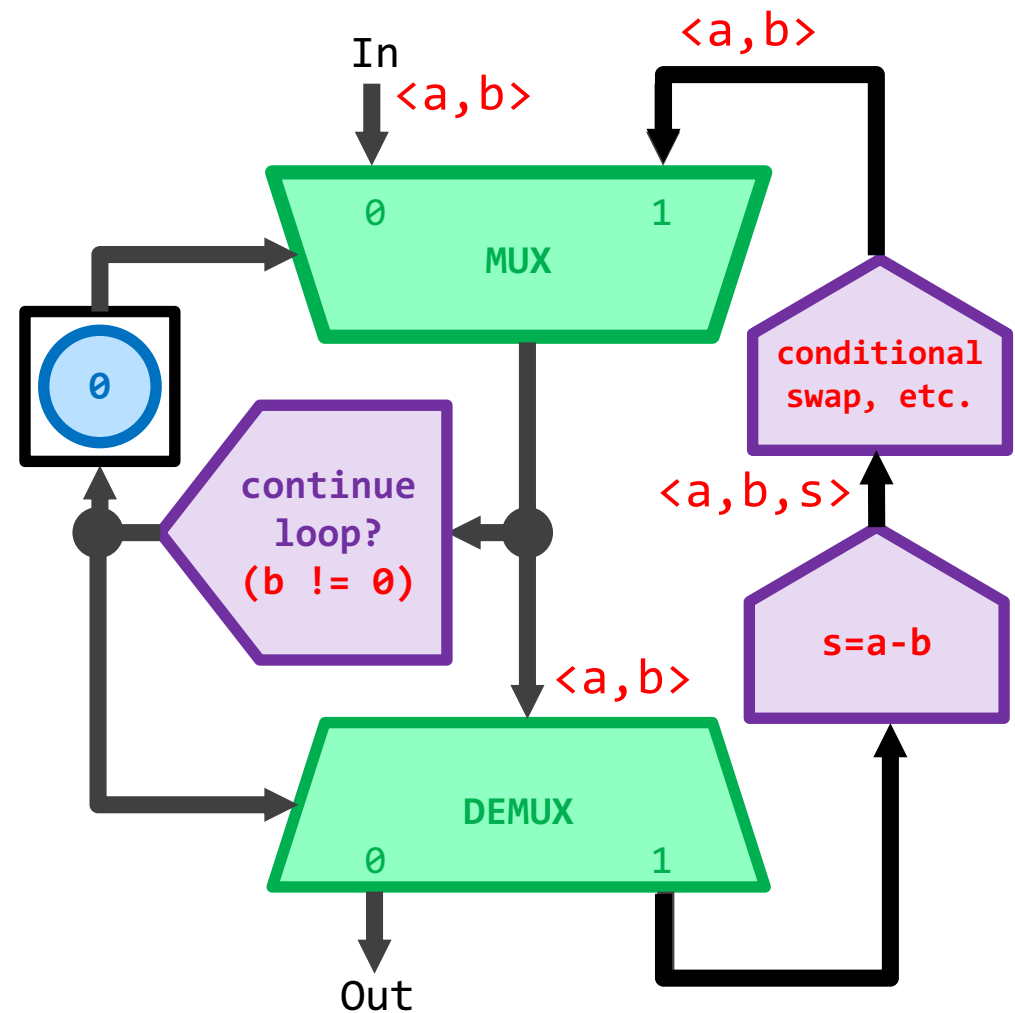


# GCD implementation

```
while (b != 0)
```

```
  s = a-b  
  if(s<0)  
    swap(a,b)  
  else  
    a = s
```



```
return a
```

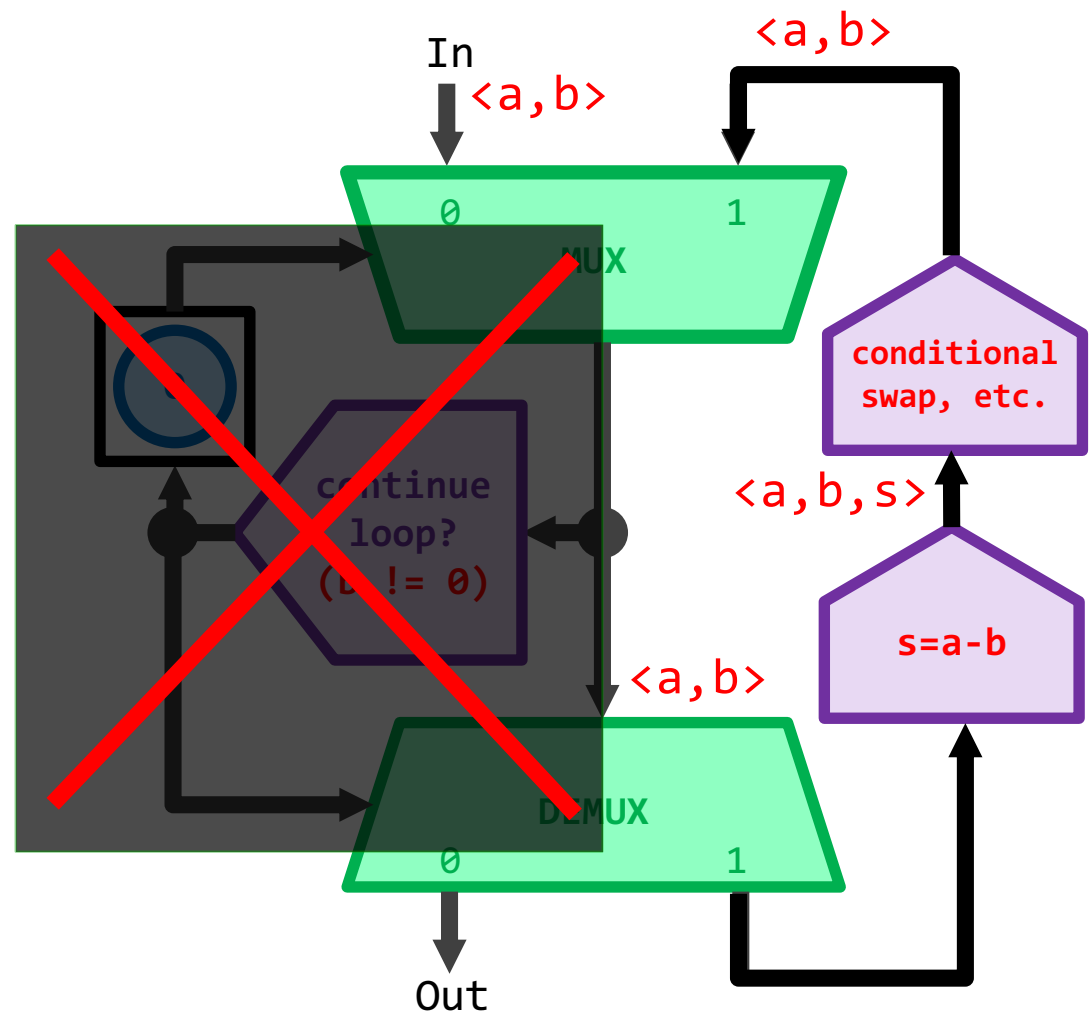 

# GCD chip

## \* Layout and fab:

- 0.13um, standard cell

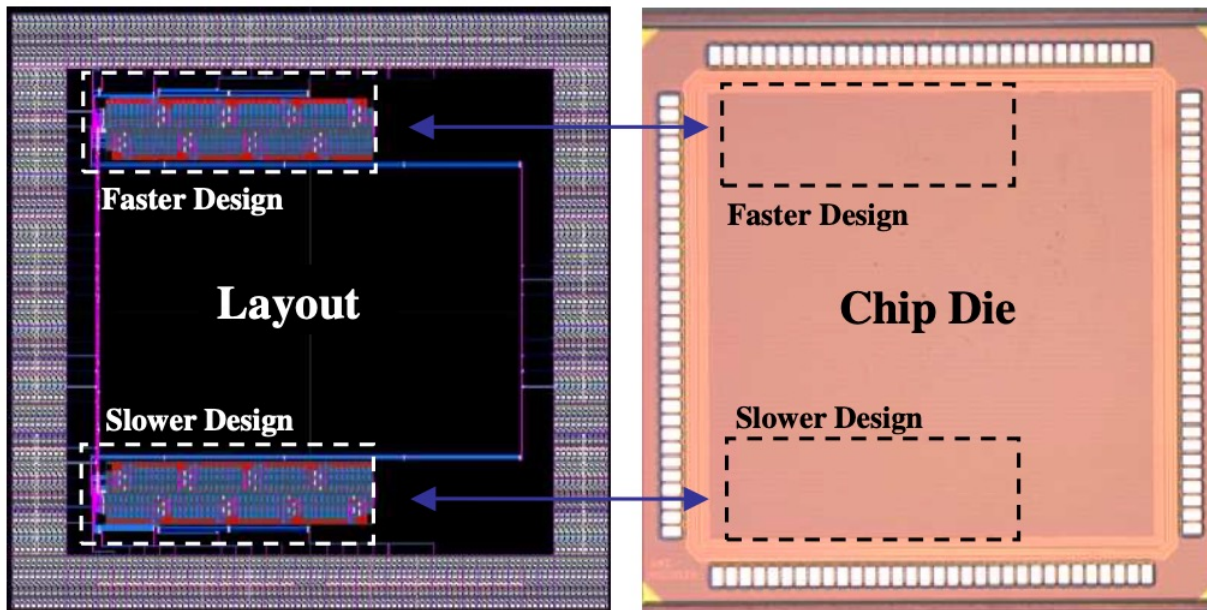 


# GCD chip


## \* Testing:

- Full scan for latches
- Combinational test patterns generated (Shi 2005) gave 98% coverage
- Functional tests for timing violations (Gill 2006)

## \* Evaluation:

 


# GCD chip: Results

 

 
# GCD chip: Results

\* Operates correctly over a wide voltage range



 
# GCD chip: Results

\* Impact of voltage variation on power consumption



# GCD chip: Results

\* Impact of temperature performance

 

# References

- \* Feng Shi, Yiorgos Makris, Steven M. Nowick, and Montek Singh. *"Test generation for ultra-high-speed asynchronous pipelines."* ITC 2005.
- \* Gennette Gill. *Analysis and Optimization for Pipelined Asynchronous Systems.* PhD thesis. UNC Chapel Hill. 2010.
- \* Gennette Gill, A. Agiwal, M. Singh, F. Shi, Y. Makris, *"Low-Overhead Testing of Delay Faults in High-Speed Asynchronous Pipelines."* ASYNC 2006.
- \* Montek Singh and Steven Nowick. *"MOUSETRAP: Ultra-High-Speed Transition-Signaling Asynchronous Pipelines."* ICCD 2001.
- \* Montek Singh and Steven Nowick. *"MOUSETRAP: High-Speed Transition-Signaling Asynchronous Pipelines."* TVLSI 2007.
- \* Gennette Gill, J. Hansen, A. Agiwal, L. Vicci and M, Singh. *"A High-Speed GCD Chip: A Case Study in Asynchronous Design."* ISVLSI 2009.