

# EENG 426/CPSC 459/ENAS 876 Silicon Compilation

## Well plugs. Pads

Computer Systems Lab  
<http://csl.yale.edu/~rajit>

Fall 2018

Yale

AVLSI

Manohar


EENG 426: Silicon Compilation

Fall 2018

1 / 9

## Wells

### CMOS latchup

 

Well contacts prevent this pair from turning on.

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

2 / 9

## Wells

- magic generates wells automatically
  - ... by bloating the diffusion region
- Try `:cif see CWP` or `:cif see CWN`
- *p*-type transistors in *n*-type well (connected to *V*<sub>dd</sub>)
- *n*-type transistors in *p*-type well (connected to GND)
- Use *substrate* (*well*) contacts
  - Contacts: `psc`, `nsc`

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

3 / 9

## Chip I/O

To get signals on and off a chip:

- *Pads*: big metal “sandwich”
- Input/output pins on the chip are bonded to pads
- Wires from layout connected to pads
- Pad design rules don’t scale (bonding machines constrain them)

### Organization:

- Periphery of chip
- Multiple layers
- Array pads

Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

4 / 9

## Pads

### Multiple types:

- Input pads
- Output pads
- Bidirectional pads
- Tristate pads

### Others:

- Power supply pads
- Level shifting pads
- Analog (bare) pads
- LVDS pads, etc etc.

Yale

AVLSI

Manohar


EENG 426: Silicon Compilation

Fall 2018

5 / 9
 
## Input pads

What do we know about the inputs from off-chip?



Yale

AVLSI

Manohar


EENG 426: Silicon Compilation

Fall 2018

6 / 9

## Bidirectional and tristate pads

Why do we use this particular structure?

 

Yale

AVLSI

Manohar


EENG 426: Silicon Compilation

Fall 2018

7 / 9
 
## Guard rings

Used to isolate sensitive parts of the circuit from "noisy" parts.



Yale

AVLSI

Manohar

EENG 426: Silicon Compilation

Fall 2018

8 / 9

# Pad frame

