

EENG 4250/ENAS 8750 Introduction to VLSI System Design

Rajit Manohar

Computer Systems Lab
<http://cs1.yale.edu/~rajit>

Fall 2025

Yale

AVLSI

Manohar

EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

1 / 13

Inverting logic

CMOS is said to be “inverting.”

Given a one-stage circuit $\mathcal{C}$ computing

$$y = \mathcal{C}(\mathbf{x})$$

where $\mathbf{x}$ is a Boolean vector of inputs, we know that if any component of $\mathbf{x}$ changes from *false* to *true*, the output changes from *true* to *false* or remains unchanged.

Why?

Yale

AVLSI


Manohar

EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

2 / 13

Ratioless logic

 

$$R_{on} \approx 10^4 \Omega$$

$$R_{off} \approx 10^9 \Omega$$

Yale

AVLSI


Manohar

EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

3 / 13

Switches

 

Switch is controlled by $V(c)$.

$$c \Rightarrow (a = b)$$

Yale

AVLSI

Manohar

EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

4 / 13

Computing with switches

Use the switches to set nodes to specific voltages.

The voltage could come from:

- Power supply
- Another node

Restoring logic switches power supplies.

Pass gate logic switches other nodes.

Yale




Manohar

EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

5 / 13

Switches in CMOS

 

A restoring inverter using switches?

NAND? NOR?

Yale



Manohar

EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

6 / 13

Pass gates

Pros and Cons:

- Can reduce transistor count
- Can reduce logic stages (non-inverting logic)
- Does not restore signals!
- Unintended “sneak” paths

Yale



Manohar


EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

7 / 13

Multiplexer

A 2-input MUX:

 

Terrible!

Yale




Manohar

EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

8 / 13

Restoring multiplexer

 

$$(\neg x \wedge c) \vee (\neg y \wedge \neg c) \mapsto z \uparrow$$

$$(x \wedge c) \vee (y \wedge \neg c) \mapsto z \downarrow$$

Yale

AVLSI


Manohar

EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

9 / 13

Pass gate MUX

 

Simple and fast, but it doesn't restore the quality of the logic signals.

Yale

AVLSI

Manohar


EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

10 / 13

Pass gate MUX

To restore the pass gate MUX signals:

 

Can we simplify this?

Yale

AVLSI

Manohar

EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

11 / 13

Simple functions: static CMOS

If we want to compute the Boolean function $f(\mathbf{x})$:

- Pull-up switching network: $f(\mathbf{x})$
- Pull-down switching network: $\neg f(\mathbf{x})$

The net result: the output is *a/ways* connected to a power supply.

$$f(\mathbf{x}) \mapsto z \uparrow$$

$$\neg f(\mathbf{x}) \mapsto z \downarrow$$

Yale

AVLSI

Manohar

EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

12 / 13

Dynamic logic

We can implement arbitrary switching networks for pull-ups and pull-downs.

$$B^+ \mapsto z \uparrow$$

$$B^- \mapsto z \downarrow$$

(called *production rules*)

We require: $\neg(B^+ \wedge B^-)$ **non-interference**

If $\neg(\neg B^+ \wedge \neg B^-)$ **combinational** or **static**

If $B^+ \neq \neg B^-$ **state-holding** or **dynamic**