

# EENG 4250/ENAS 8750 Introduction to VLSI System Design

Rajit Manohar

Computer Systems Lab  
<http://csl.yale.edu/~rajit>

Fall 2025

Yale

AVLSI

Manohar


EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

1 / 5

## Single phase clocking

Simple pipeline:

 

Clock input:



Timing constraints for correctness? (race-through)

Yale

AVLSI

Manohar

EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

2 / 5

## Single phase clocking

Better pipeline structure:



Clock input:



Timing constraints for correctness?

Yale

AVLSI

Manohar


EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

3 / 5

## Single phase clocking

Special case:

 

Clock input:



Timing constraints for correctness?

Yale

AVLSI

Manohar


EENG 4250/ENAS 8750: VLSI Systems

Fall 2025

4 / 5

## Two phase non-overlapping clocks

Safe pipeline structure:

 

Clock input:

